

Total No. of printed pages = 3

ECE-3203/IE/6th Sem/2013/M

INDUSTRIAL ELECTRONICS

Full Marks – 100

Pass Marks – 30

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

1. (a) Discuss the effect of reverse recovery time in diodes. 8
- (b) Write short notes on : 4×3=12
 - (i) General purpose diode
 - (ii) Fast recovery diode
 - (iii) Schottkey diode.
2. (a) Explain how a BJT can be used as a switch as well as an amplifier. 7
- (b) Explain the working of an N-channel enhancement mode MOSFET. 8

[Turn over

- (c) What are the advantages of IGBT over BJT and MOSFET ? 5
3. (a) Explain the two transistor analogy of a thyristor. 7
- (b) How thyristor can be turned off and on ? 6
- (c) Explain the firing of a thyristor using UJT. 7
4. (a) Explain the working of a three phase full wave rectifier. 8
- (b) What is a chopper circuit ? Explain the working of a basic chopper circuit. 7
- (c) Explain the working of a buck-boost regulator. 5
5. (a) Explain the working of a basic inverter. 8
- (b) How a solid state relay works ? 5
- (c) How a 555 timer can be used as an astable multivibrator ? 7

6. (a) What is a transducer ? What are the different types of transducers ? Give applications of each type of transducers. 8
- (b) Explain the working of a PLC. 8
- (c) What are the differences between a microprocessor and a microcontroller ? 4
7. Write short notes on : 10×2=20
- (a) 8051 microcontroller
- (b) SIT.