

Total number of printed pages-7

53 (EE 201) BEEN

2012 C

2013

(May)

## BASIC ELECTRICAL ENGINEERING

Paper : EE 201

Full Marks : 100

Pass Marks : 30

Time : Three hours

*The figures in the margin indicate full marks  
for the questions.*


*Answer any five questions.*

- (a) State Superposition theorem and Maximum Power transfer theorem. 2.5+2.5=5

(b) What is linear circuit element? 3


*Contd.*

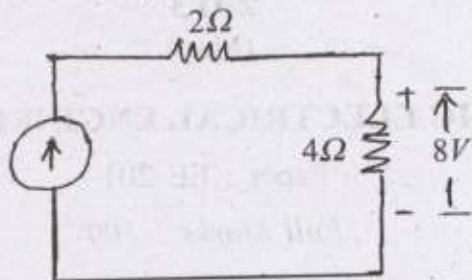- (c) In the following circuit, find the value of the current and terminal voltage of the current source. Also determine the power that is dissipated in the  $2\Omega$  resistor. 6



- (d) A resistor  $R$  is connected in series with a parallel circuit comprising two resistances of  $12\Omega$  and  $8\Omega$  respectively. The total power dissipated in the circuit is  $70W$  when the applied voltage is  $20V$ . Calculate  $R$ . 6

2. (a)

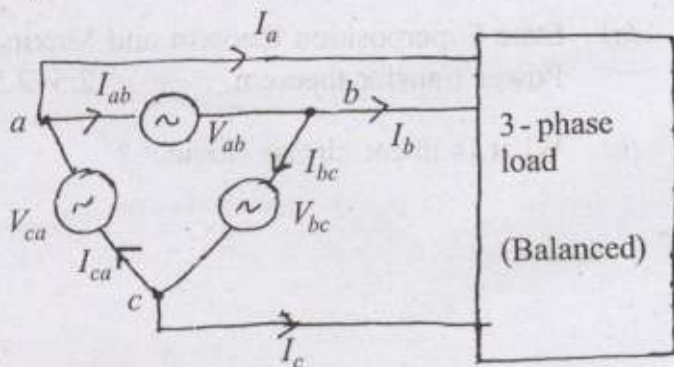


For the above 3-phase circuit, three voltage sources have same amplitude and frequency but phase displacement from one another by  $120^\circ$ . Derive the relationship between phase current and line current. Also draw the phasor diagram. 10

- (b) A three phase  $440V$  power supply has a load of power factor  $0.6$ . Two wattmeters are connected to measure the power. If the input be  $15KW$ , find the reading of each wattmeter. 10

3. (a) State Ampere's law and comment about the motion of lines of forces. 5

(b) What is magnetomotive force? How does it differ from electromotive force? How is it similar? 5

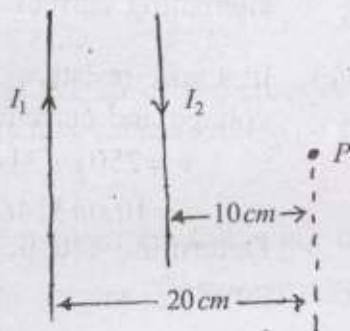(c) In the following figure, the current  $I_1$  has a value of  $40A$ . Find the value of  $I_2$  that causes the magnetic field intensity at point  $P$  to disappear. 5



(d) Show that the flux density produced by an infinitely long straight wire, carrying a current  $I$ , in a point at a distance ' $a$ ' normal to the wire is given by  $\frac{\mu_o \mu_r I}{2\pi a}$ . 5

4. (a) A sinusoidal current of 50Hz has maximum value of 120A.

(i) Write down the equation for instantaneous value.

(ii) Reckoning time from the instant the current is zero and becoming positive, find the instantaneous value after 1/360 second.

(iii) Time taken to reach 96A for the first time. 6

(b) Find the average value, r.m.s. value, form factor, and peak factor of half wave rectified alternating current. 8

(c) In a pure resistive circuit, the instantaneous voltage and current are given by

$$v = 250 \sin 314t$$

$$i = 10 \sin 314t$$

Determine the peak power and average power. 6

5. (a) Make a comparison of characteristics of MI and MC instruments. 6
- (b) A coil resistance  $100\Omega$  and inductance  $100$  micro-henry is connected in series with a  $100$  picofarad capacitor. The circuit is connected to a  $10V$  variable frequency supply.  
Calculate (i) Resonant frequency (ii) Current at resonance (iii)  $Q$ -factor of the circuit. 6
- (c) The meter element of a PMMC instrument has a resistance of  $5$  ohms and requires  $15mA$  for full scale deflection. Calculate the resistance to be connected
- (i) In parallel to enable the instrument to read upto  $1A$
- (ii) In series to read upto  $15V$ . 8
6. (a) Compare the merits and demerits of underground system versus overhead system. 5
- (b) Draw a neat sketch of the cross-section of  
(i) 3-core belted cable (ii) H-type cable. 6
- (c) Define and explain the following terms : 4  
(i) Fusing current (ii) Cutoff current.


(d) What do you mean by grounding or earthing? Explain it with an example. 5

7. (a) An emf given by  $326\sin 314t$  is applied to a certain circuit and current is  $2\sin(314t - 1.3736)$ .

Find (a) Frequency of voltage (b) Phase angle between current and voltage in degrees. (c) Resistance of the circuit. 6

(b) A bulb rated at  $110V, 60W$  is connected in series with another bulb rated  $110V, 100W$  across  $220V$  mains. Calculate the resistance that should be connected in parallel with the first bulb so that both the bulbs may take their rated power. 5

(c)

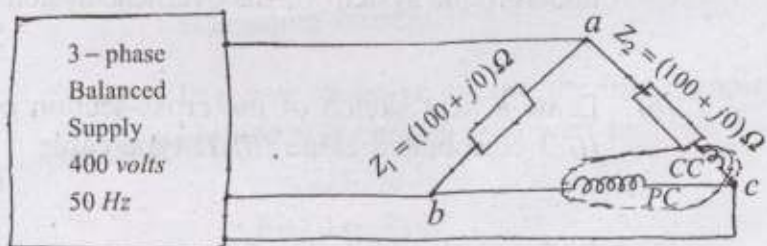

The pressure coil (*PC*) and current coil (*CC*) of a wattmeter are connected to the load as shown, with the coil polarities suitably selected to ensure a positive deflection. Calculate the wattmeter reading. 9

BASIC ELECTRICAL ENGINEERING

Nov. 11, 2011

Full Mark: 100

Time: 1 hour 15 min

Exam. No. 11/11/11

The cover of the student's answer full marks

\_\_\_\_\_