

2014

BASIC ELECTRICAL ENGINEERING

Paper : EE 201

Full Marks : 100


Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.


- (a) State the Maximum Power Transfer theorem in DC circuit. 4

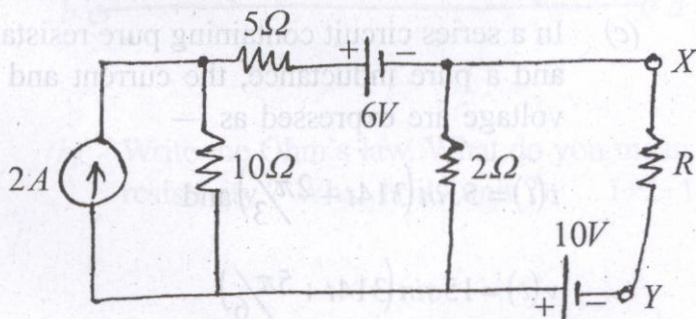(b) Find R to have maximum power transfer in the circuit shown below. Also obtain the amount of maximum power. 8



Contd.

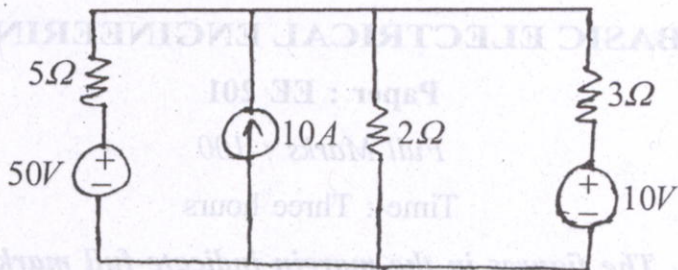- (c) Using mesh analysis, calculate the current through the 5Ω resistor in the given network. 8




2. (a) What do you mean by effective value of AC current? Why for a sinusoidal AC current wave average value is zero over a complete cycle? Establish a relation between RMS value and Maximum value. 2+2+3=7
- (b) Explain the significance of Power factor in AC circuits. 3
- (c) In a series circuit containing pure resistance and a pure inductance, the current and the voltage are expressed as — 10

$$i(t) = 5 \sin\left(314t + \frac{2\pi}{3}\right) \text{ and}$$

$$v(t) = 15 \sin\left(314t + \frac{5\pi}{6}\right)$$

- (i) What is the impedance of the circuit ?
- (ii) What is the value of the resistance ?
- (iii) What is the inductance in henry ?
- (iv) What is the average power drawn by the circuit ?
- (v) What is the Power factor ?


3. (a) Convert the following Δ to Y . 4

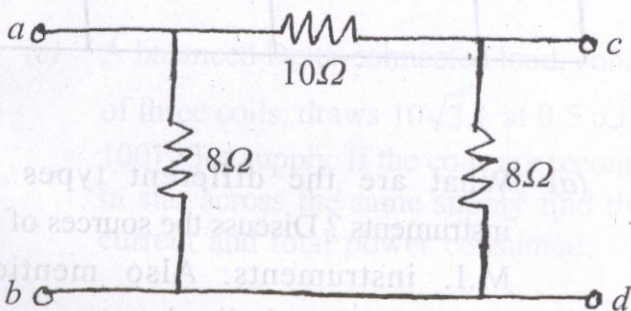

(b) Write the Ohm's law. What do you mean by resistivity ? What is its unit ? 1+2+1=4

- (c) Use nodal analysis method to find currents in the various resistors to the circuit shown—

12

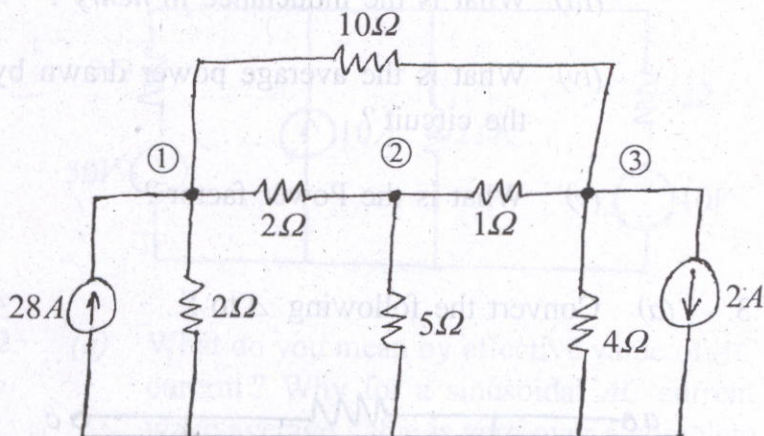

4. (a) What are the different types of MI instruments? Discuss the sources of error in M.I. instruments. Also mention the advantages and disadvantages of M.I. instruments. 8
- (b) What is the significance of shunt in Ammeters? Explain how the range of an ammeter can be extended? 6

10 (c) A $250V$ moving-iron voltmeter takes a current of $0.05A$ when connected to a $250V$ d.c. supply. The coil has an inductance of $1H$. Determine the reading on the meter when connected to a $250V, 100Hz$ ac supply.

6

5. (a) Derive a relation between line voltage and phase voltage in a balance star connected system.

5

(b) Mention any three advantages of 3- ϕ system over 1- ϕ system.

3

(c) A balanced Delta-connected load, consisting of three coils, draws $10\sqrt{3}A$ at 0.5 p.f. from $100V, 3-\phi$ supply. If the coils are reconnected in star across the same supply find the line current and total power consumed.

12

6. (a) Write about the following :

6


(i) Self-inductance

(ii) Electromagnet

(iii) Reluctance.

(b) State and explain Faraday's laws of electromagnetic induction. 4

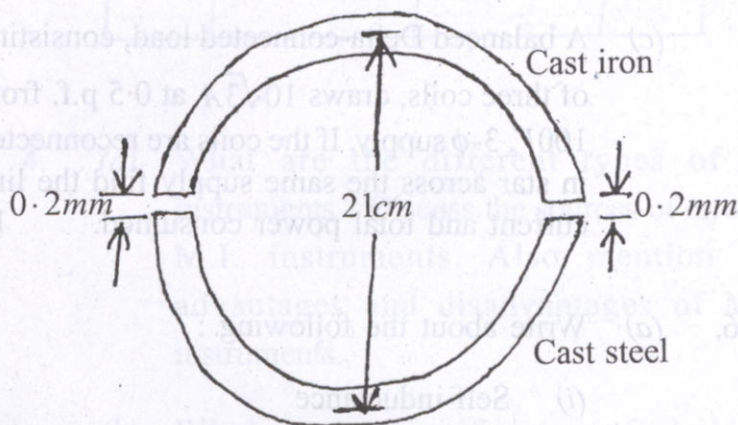(c) A ring has a diameter of 21cm and a cross-sectional area of 10cm^2 . The ring is made up of semicircular sections of cast iron and cast steel, with each joint having a reluctance equal to an air-gap of 0.2mm . Find the ampere-turns required to produce a flux of $8 \times 10^{-4}\text{wb}$. The relative permeabilities of cast steel and cast iron are 800 and 166 respectively. 10



7. (a) Explain how a fuse protects the appliances from damage when short-circuit occurs. 7

(b) Explain why earthing is very important for an electrical wiring system? Draw sketch if necessary. 7

(c) It is required to control two bulbs, one fan and a 3-pin socket outlet from 220V, 50Hz supply. Draw a neat diagram. 6

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions

Answer any five questions

(a) State the Maximum Power Transfer theorem for an AC circuit. 4

(b) Find R to have maximum power transfer in the circuit shown below. Also obtain the amount of maximum power. 8

