

Total number of printed pages-7

53 (EE 201) BEEN

2014

BASIC ELECTRICAL ENGINEERING

Paper : EE 201


Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.


Answer any five questions.

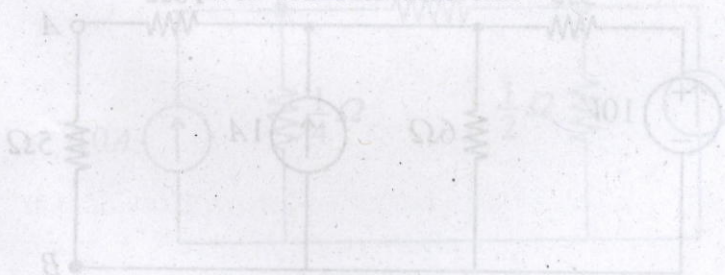1. (a) State Superposition theorem and Maximum Power Transfer theorem. 5




Contd.

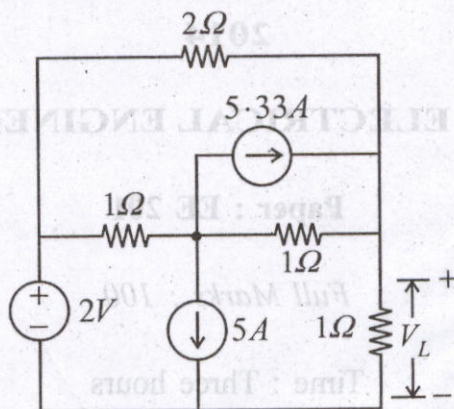- (b) Find V_L in the following circuit using superposition theorem 9




- (c) What do you mean by active and passive circuits and linear and non-linear elements? 6

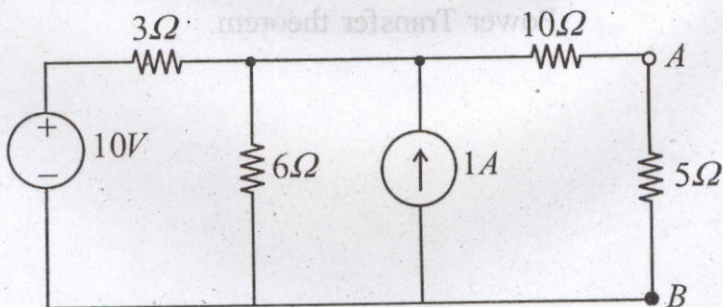2. (a) Find the current in 5Ω resistor using Norton's theorem 6




(b) Calculate Current I in the following circuit

8

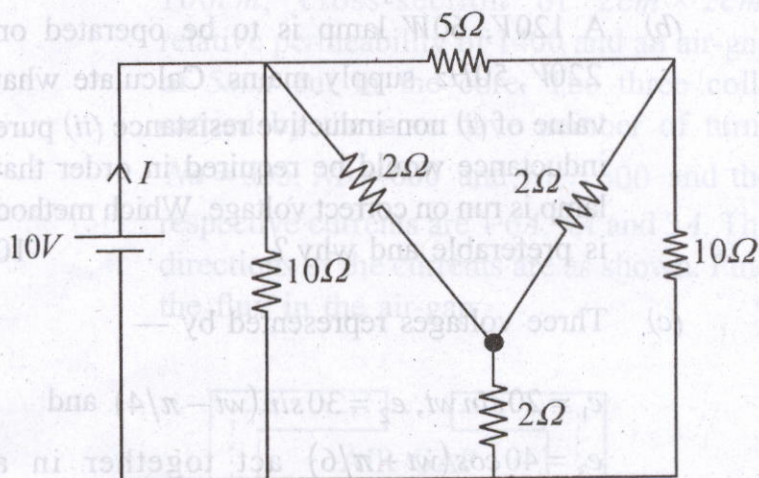

(c) Find V_1 and V_2 using nodal analysis.

6

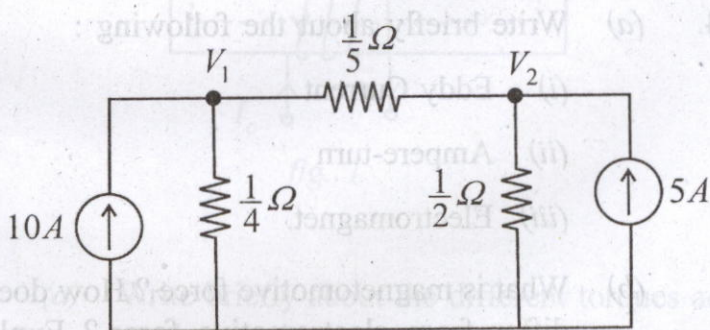

3. (a) Define Power factor. What do you mean by lagging and leading power factor? 1+2=3

(b) A 120V, 60W lamp is to be operated on 220V, 50Hz supply mains. Calculate what value of (i) non-inductive resistance (ii) pure inductance would be required in order that lamp is run on correct voltage. Which method is preferable and why? 10

(c) Three voltages represented by —

$e_1 = 20 \sin wt$, $e_2 = 30 \sin(wt - \pi/4)$ and $e_3 = 40 \cos(wt + \pi/6)$ act together in a circuit. Find an expression for the resultant voltage. Represent them by appropriate vectors. 7

4. (a) Write briefly about the following : 6

(i) Eddy Current

(ii) Ampere-turn

(iii) Electromagnet.

(b) What is magnetomotive force? How does it differ from electromotive force? Explain with examples, if necessary. 5

- (c) A rectangular iron core is shown in *fig. 1*. It has a mean length of magnetic path of 100cm , cross-section of $2\text{cm} \times 2\text{cm}$, relative permeability of 1400 and an air-gap of 5mm cut in the core. The three coils carried by the core have number of turns $N_a = 335$, $N_b = 600$ and $N_c = 600$ and the respective currents are 1.6A , 4A and 3A . The directions of the currents are as shown. Find the flux in the air-gap

9

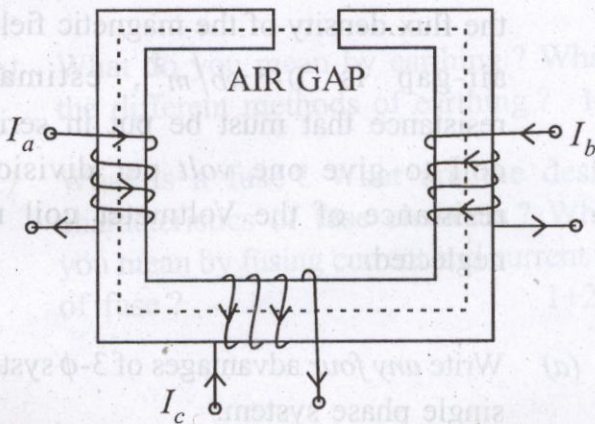


fig. 1

5. (a) Write briefly about the different torques act on the moving system of an instrument.

9

(b) A moving-coil instrument has a resistance of 10Ω and gives full-scale deflection when carrying a current of $50mA$. Show how it can be adopted to measure voltage upto $750V$ and currents upto $1000A$. 5

(c) The coil of a moving coil permanent magnet Voltmeter is $40mm$ long and $30mm$ wide and has 100 turns on it. The control spring exerts a torque of $120 \times 10^{-6} N-m$ when the deflection is 100 divisions on full-scale. If the flux density of the magnetic field in the air-gap is $0.5 wb/m^2$, estimate the resistance that must be put in series with coil to give one volt per division. The resistance of the Voltmeter coil may be neglected. 6

6. (a) Write any four advantages of 3- ϕ system over single phase system. 4

(b) Derive a relation between line current and phase current in a balance delta connected system. 6

(c) A balanced star-connected load of $(8 + j6)\Omega$ per phase is connected to a balanced 3- ϕ , 400V supply. Find the line current, power factor, power and total *volt-amperes*. 10

7. (a) What are the different types of internal wiring usually employed in industries and house? With the help of a neat diagram show, how a single phase energy meter, main switch and a distribution box (with 4 sub-circuits) are connected in a domestic wiring system.

4+7=11

(b) What do you mean by earthing? What are the different methods of earthing? 1+3=4

(c) What is a fuse? What are the desirable characteristics of fuse elements? What do you mean by fusing current and current rating of fuse? 1+2+2=5