

Total number of printed pages-9

53 (EE 201) BEEN

2019

BASIC ELECTRICAL ENGINEERING

Paper : EE 201

Full Marks : 100

Time : Three hours


The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

1. (a) Find the resistance between terminals A and B of the following figure when switch is — 5


(i) Open

(ii) Closed.

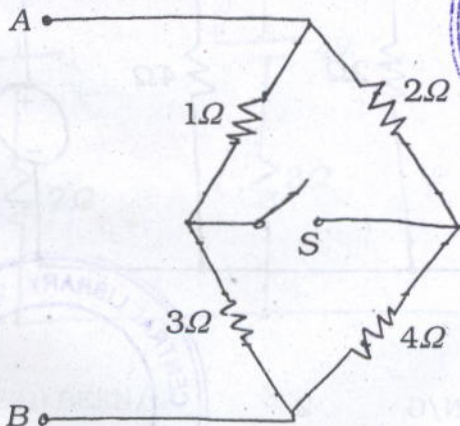


Contd.

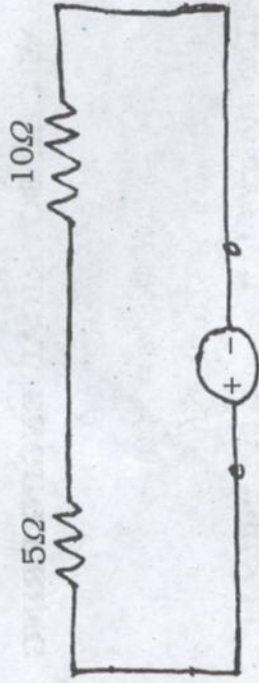
(b) In the following figure, the 10Ω resistor dissipates $360W$. What is the voltage drop across the 5Ω resistor? 5



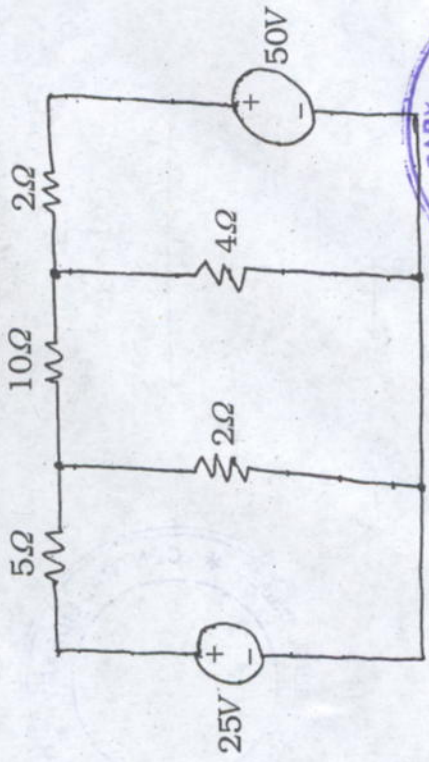
(c) Find the magnitude and direction of current flowing through 10Ω resistance of the given circuit — 10



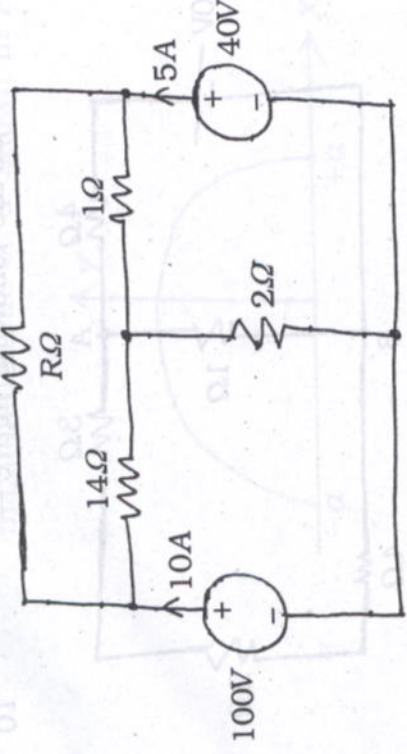
2. (a) In the following figure, calculate the value of R . 5



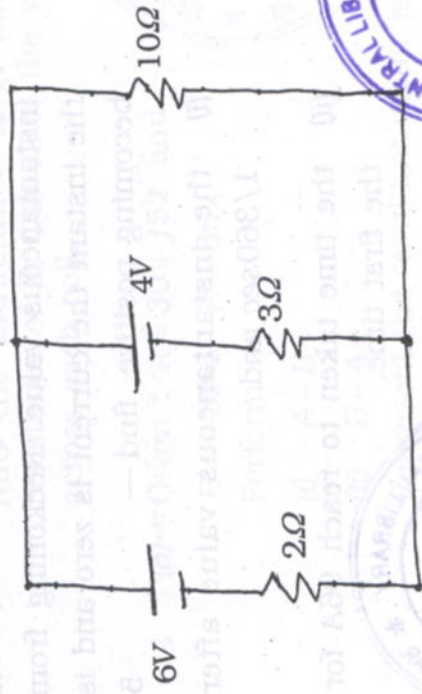(b) Using the Superposition theorem, calculate the current in the 10Ω resistance. 5



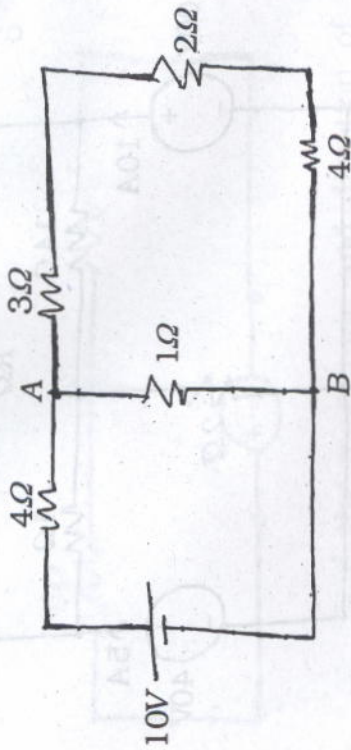
- (c) Use Thévenin's theorem to find current in the branch AB of the network shown in the following figure — 10



3. (a) An alternating current of frequency 60Hz has a maximum value of 120A. Write down the equation for its instantaneous value. Reckoning from the instant the current is zero and is becoming positive, find — 5

- (i) the instantaneous value after $1/360$ sec and
 (ii) the time taken to reach 96A for the first time.

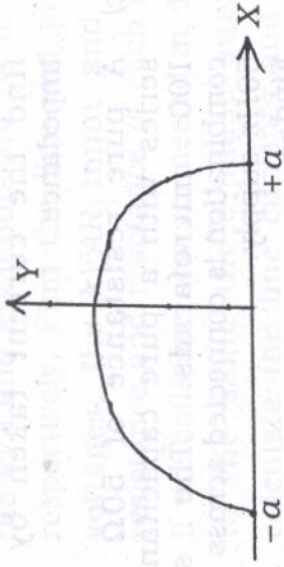- (b) Determine the r.m.s. value of semi-circular current wave which has a maximum value of 'a' shown in Fig. 5



- (c) Two coils A and B are connected in series across a 240V, 50Hz supply. The resistance of A is 50Ω and the inductance of B is $0.015H$. If the input from the supply is $3kW$ and $2kVAR$, find the inductance of A and the resistance of B . Calculate the voltage across each coil. 10

4. (a) Given : $A = 30 + j52$ and
 $B = -39.5 - j14.36$.

Perform —


- (i) $A - B$
 (ii) $B - A$

Represent the resultant vector in polar form. 5

(b) Two impedance $Z_1 = (8 + j.6)\Omega$ and $Z_2 = (3 - j.4)\Omega$ are in parallel. If the total current of the combination is 25A, find the current taken by each impedance. 5

(c) A pure resistance of 50Ω is in series with a pure capacitance of 100 microfarads. The series combination is connected across 100V, 50Hz supply. Find —

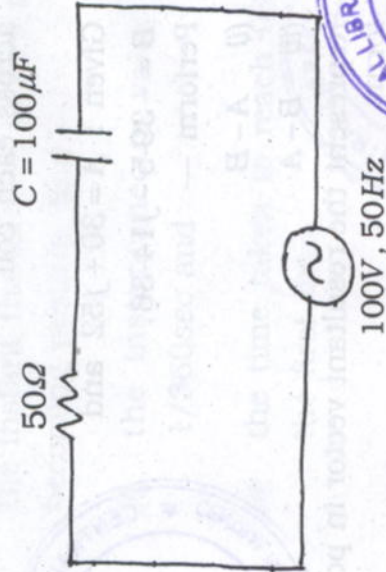- (a) the impedance
 - (b) current
 - (c) - voltage across resistor
 - (d) power factor
 - (e) phase angle
 - (f) voltage across capacitor.
- Draw the vector diagram. 10




5. (a) The load connected to a 3- ϕ supply comprises three similar coils connected in star. The line currents are 25A and the kVA and kW inputs are 20 and 11 respectively. Find the line and phase voltages, the kVAR input and the resistance and reactance of each coil. If the coils are now connected in delta to the same three-phase supply, calculate the line currents and the power taken. 10

(b) What is meant by phase sequence in the three-phase system? Write some advantages of three-phase system. 3+2=5

(c) Derive the relation between line voltage and phase voltage in a star-connection in the three-phase system. Draw the star-connection and its vector diagram. 5

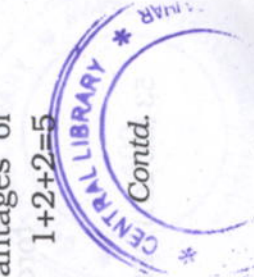6. (a) What is a fuse? Mention two advantages and two disadvantages of fuse. 1+2+2=5



(b) A moving coil ammeter has a fixed shunt of 0.02Ω with a coil circuit resistance of $R = 1k\Omega$ and need potential difference of $0.5V$ across it for full-scale deflection.

(i) Find the total current corresponding to the above data.

(ii) Calculate the value of shunt to give full-scale deflection when the total current is $10A$ and $75A$.

5

(c) A coil is wound uniformly with 300 turns over a steel ring of relative permeability 900 , having a mean circumference of $40mm$ and cross-sectional area of $50mm^2$. If a current of $25amp$ is passed through the coil, find —

(i) mmf

(ii) reluctance of the ring and

(iii) flux.

10

7. (a) Derive an expression for deflecting torque for PMMC instrument.

5

(b) Write the SI units of the following :
 $1 \times 5 = 5$

(i) Magnetic flux

(ii) Reluctance

(iii) Luminous intensity

(iv) Torque

(v) Angular momentum.

(c) A horseshoe magnet is formed out of a bar of wrought iron $45.7cm$ long, having a cross-sectional area of $6.45cm^2$. Exciting coils of 500 turns are placed on each limb and connected in series. Find the exciting current necessary for the magnet to lift a load of $68kg$ assuming that the load has negligible reluctance and makes close contact with the magnet. Relative permeability of iron = 700 .

5

(d) How will you use a PMMC instrument which gives full-scale deflection at $50mV$ p.d. and $10mA$ current as a voltmeter of $0-250V$ range?

5

