

Total number of printed pages-7

53 (EE 201) BEEN

2019

BASIC ELECTRICAL ENGINEERING

Paper : EE 201

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

1. (a) Find the unknown currents in the circuits shown in Fig. (i) 5

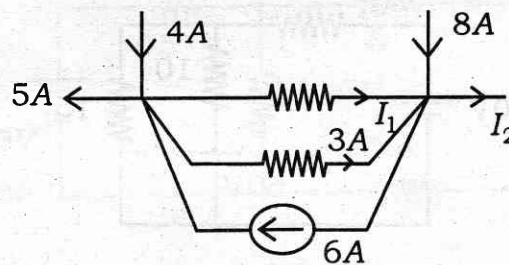


Fig. (i)

Contd.



(b) Find the equivalent Thevenin voltage across the open-circuited terminals A and B to the circuit shown in Fig. (ii). All resistances are in ohm. 5

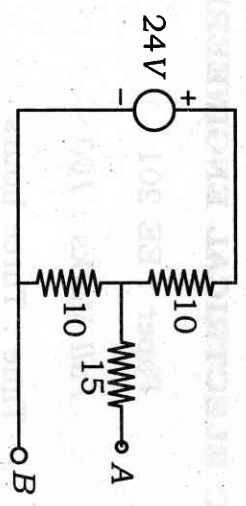


Fig. (ii)

(c) Find the current in every branch of the circuit shown in Fig. (iii). All resistances are in ohm. 5

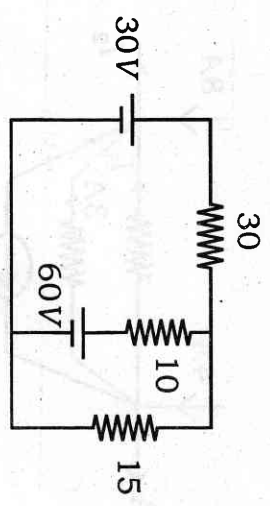


Fig. (iii)



2. (a) Find the equivalent resistances across the open-circuited terminals a and b of the Fig. (iv). All the resistances are in ohm. 5

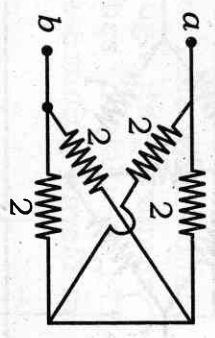


Fig. (iv)

(b) Find the Norton equivalent resistance for the active linear network shown in Fig. (v). All resistances are in ohm. 5

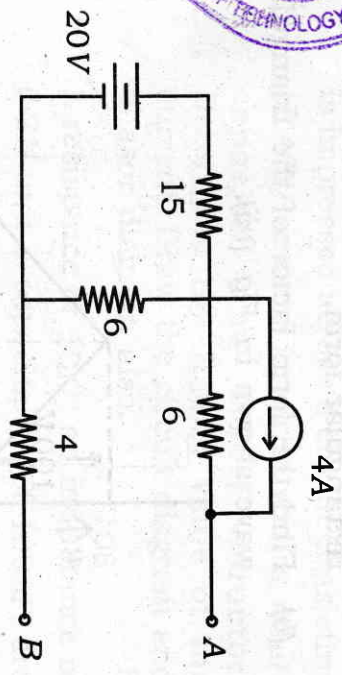


Fig. (v)



- (c) Using delta-star transformation, determine the current drawn from the source in the given circuit in Fig. (vi). All the resistances are in ohm. 10

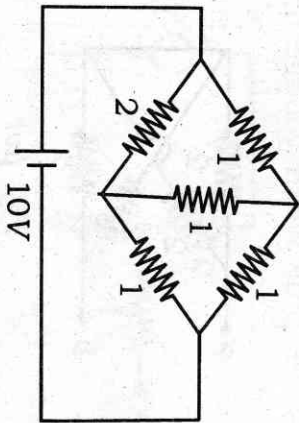


Fig. (vi)

3. (a) Perform the following operation.
 $(16 + 8j) \div (3 - 4j)$
 Write the answer in polar as well as rectangular form.
- (b) Find the form factor of the triangular wave shown in Fig. (vii).

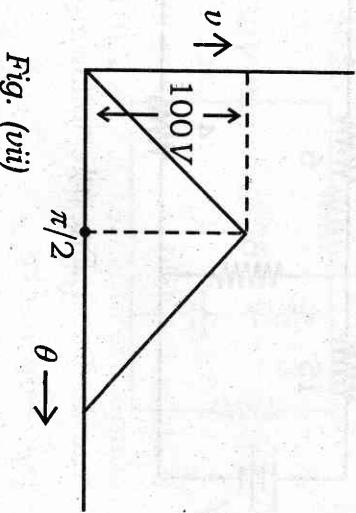


Fig. (vii)

- (e) A sinusoidal alternating voltage has an r.m.s. value of 200V and a frequency of 50Hz. It crosses the zero axis in a positive direction when $t=0$. Determine (i) the time when voltage first reaches the instantaneous value of 200V and (ii) the time when voltage after passing through its maximum positive value reaches the value of 141.4V. Draw the corresponding waveform. 10

4. (a) A circuit takes a current of 8A at 100V, the current lagging by 30° behind the applied voltage. Calculate the impedance in polar form as well as rectangular form. 5

- (b) An emf represented by $e = 100 \sin 100\pi t$ is impressed across a circuit consisting of 40Ω resistor in series with a $40\mu F$ capacitor and $0.25H$ inductor. Determine the R.M.S. value of the current. Draw the circuit diagram and phasor diagram also. 5

- (c) A resistance of 20Ω , an inductance of $0.2H$ and a capacitance of $100\mu F$ are connected in series across 220V, 50Hz mains. Determine the following:
 (a) impedance

- (b) current
- (c) voltage across R , L and C
- (d) power in $watt$ and VA
- (e) power factor and angle of lag/lead.
Draw the circuit diagram and phasor diagram also. 10
5. (a) Write the expressions of three-phase voltages of star-connected balanced voltage source. Also write the corresponding phasors. 5
- (b) Draw the phasor diagram of line voltages and phase voltages of star-connected balanced three phase voltage source. 5
- (c) Given a balanced 3-phase system with star-connected load for which line voltage is $230V$ and impedance of each phase is $(6+8j)\Omega$. Find the line currents and active power absorbed by each phase. Draw the circuit diagram also. 10
6. (a) A wire is bent into a plane to form a square of $30cm$ side and a current of $100A$ is passed through it. Calculate the magnetic field strength set up at the centre of the square. 5



- (b) Two infinite parallel conductors carry parallel currents of $10A$ each. Find the magnitude and direction of the force between the conductors per metre length if the distance between them is $20cm$. 5
- (c) An iron ring of mean length $50cm$ has an air gap of $1mm$ and a winding of 200 turns. If the permeability of iron is 300 when a current of $1A$ flows through the coil, find the flux density. 10
7. (a) With the help of neat diagram, show how a single phase energy meter, main switch and a distribution box (with 4 subcircuits) are connected in a domestic wiring system. 5
- Write the advantages of PMMC type instruments. 5
- How will you use a PMMC instrument which gives a full-scale deflection at $50mV$ potential difference and $10mA$ current as — 10
- (i) Ammeter $0-10A$ range
- (ii) Voltmeter $0-250V$ range ?
- Draw the circuit diagrams for each case and clearly show the necessary steps.