

Total No. of printed pages = 3

El-304/EEE/3rd Sem/2014/N

**ELEMENTS OF ELECTRICAL
ENGINEERING**

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer any *five* questions.

1. (a) Write at least three properties and uses of each of good conductor and good insulator. 4
- (b) Define with their units : work, power and energy. $3 \times 2 = 6$
- (c) Establish the relation between kWh and kcal. 4

2. (a) State and explain Kirchhoff's laws. 5
- (b) Name the active materials of lead acid battery. State the chemical reaction takes place during charging and discharging of a lead acid battery. $3 + 6 = 9$

[Turn over

3. (a) Draw the main parts of a d.c generator. 4
- (b) A 4 pole d.c shunt generator has 36 slots with 10 conductors in each slot. The flux is 0.03 Wb/pole and speed is 750 r.p.m. Calculate the emf generated for lap winding. 5
- (c) What is back emf ? Draw the symbolic diagram of d.c motors. $2+3=5$
4. (a) Define : Instantaneous value, cycle, RMS value, average value. $4 \times 2 = 8$
- (b) An emf is given by $170 \sin 377t$. Determine
- (i) its RMS value
 - (ii) frequency
 - (iii) value of the voltage after $t = 3 \text{ ms}$. $3 \times 2 = 6$
5. (a) Define : Inductance, capacitive reactance, impedance and power factor. $4 \times 2 = 8$
- (b) A coil having pure resistance of 75Ω and pure inductance of 318 mH connected in series with a 50 Hz supply source and the voltage across the 75Ω resistor is found to be 150 V . Calculate the supply voltage, phase angle and power factor of the circuit. $3 \times 2 = 6$

6. (a) Derive the EMF equation of transformer. 5
(b) Derive the relation between transformation ratio, turn ratio and current ratio. 5
(c) What do you mean by induction motor ? 4
7. Write short notes on : $3\frac{1}{2} \times 4 = 14$
(a) Current transformer
(b) Potential transformer
(c) Working of D.C motor
(d) R-L-C series circuit.