

Total No. of printed pages = 6

EI-401/ECN/4th Sem/2018/M

ELECTRICAL CIRCUIT AND NETWORK

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks
for the questions.

PART – A

Marks – 25

Time – One hour

Answer *all* the questions.

1. Fill in the blanks : 1×10=10
- (a) Norton's theorem can be applied only in _____ circuit.
- (b) A network having one or more than one source of e.m.f is known as _____ network.
- (c) In a parallel RLC circuit, with $X_L > X_C$ the circuit behaves as _____.

[Turn over

- (d) Admittance is equal to the reciprocals of _____.
- (e) Number of cycles per second is called _____.
- (f) The equation of true power is _____.
- (g) The ratio of true power by apparent power is called _____.
- (h) Negative phase angle means _____.
- (i) In delta connected three phase system, the line voltage = _____.
- (j) In the two parallel branches of a parallel circuit, more current will flow through that branch which has _____ impedance.

2. State true or false : $1 \times 10 = 10$

- (a) Kirchhoff's first law is based on the principle of law of conservation of charge.
- (b) The total resistance in a series circuit is always less than the least resistor.
- (c) The voltages across all components in a parallel circuit are equal.

- (d) Thevenin's resistance is found by removing voltage sources along with their internal resistance.
- (e) An ideal voltage source should have zero source resistance.
- (f) The superposition theorem requires as many circuits to be solved as there are sources.
- (g) The time period of a wave is same as frequency.
- (h) Form factor is the ratio of r.m.s value and average value.
- (i) At series resonance, applied voltage $V =$ voltage across R.
- (j) The power factor of pure capacitive circuit is 1.

3. Multiple choice questions : 1×5=5

- (a) In a star-connected system, the current flowing through the line is :
 - (i) Greater than the phase current
 - (ii) Equal to the phase current
 - (iii) Lesser than the phase current
 - (iv) None of these.

(b) Ohmic value of capacitive coil is called :

- (i) Impedance
- (ii) Resistance
- (iii) Capacitive reactance
- (iv) Inductive reactance

(c) In a three phase AC circuit, the sum of all three generated voltage is :

- (i) Infinite
- (ii) One
- (iii) Zero
- (iv) None of the above.

(d) In case of inductive circuit, frequency is _____ proportional to the inductive reactance.

- (i) directly
- (ii) inversely
- (iii) No effect

(e) Unit of admittance is :

- (i) Ohm
- (ii) Siemens
- (iii) Henry
- (iv) Farad.


PART - B

Marks - 45

Time - Two hours

Answer any *three* questions.

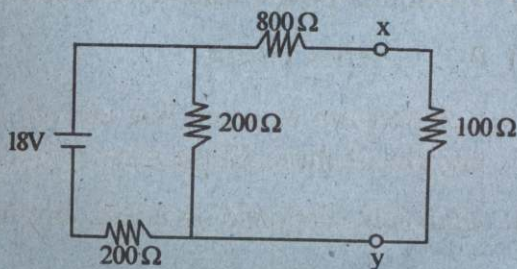4. (a) Define parameters, non-linear circuit, bilateral circuit and active network. 6
- (b) A circuit consisting of three resistances of 12Ω , 18Ω and 36Ω respectively joined in parallel is connected in series with a fourth resistance R . The whole circuit is supplied at $60V$ and it is found the power dissipated in 12Ω resistance is $36 W$. Determine the value of " R " and power absorbed in the parallel group. 9
5. (a) Prove the reciprocity theorem. 5
- (b) Find the voltage across 10 ohm resistor by constructing Norton's equivalent circuit in the figure to the left of terminals $x-y$. 10



6. (a) A coil of resistance 12Ω and inductive reactance of 25Ω is connected in series with a capacitive reactance of 15Ω . The combination is connected to a supply of 230V , 50 Hz . Find 9
- (i) Circuit impedance
 - (ii) Current
 - (iii) Power consumed.
- (b) Define RMS value, average value and form factor. 6
7. In a series parallel circuit the parallel branches A and B are in series with C. The impedances are $Z_A = 5 + j3$, $Z_B = 9 - j7$ and $Z_C = 6 + j5$. If the voltage applied to the circuit is 180V at 50 Hz . calculate : 15
- (a) Current I_A , I_B and I_C .
 - (b) The total power factor for the whole circuit.
8. Write short notes on any *three* : $5 \times 3 = 15$
- (a) Maximum power transfer theorem
 - (b) R-L-C series circuit
 - (c) Relationship between line current and phase current of three phase star-connect system.
 - (d) Transient response on a R-L circuit.