

Total No. of printed pages = 8



## END SEMESTER EXAMINATION – 2019

Semester : 4th (Old)

Subject Code : EI-401

### ELECTRICAL CIRCUITS AND NETWORKS

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks for the questions.

#### Instructions :

1. All questions of PART-A are compulsory.
2. Answer any *five* questions from PART-B.

PART – A

Marks – 25

1 Fill in the blanks : 1×10=10

(a) Ideal voltage source has \_\_\_\_\_ internal resistance.

(b) The most commonly used polyphase system is \_\_\_\_\_ system.

[Turn over

(c) In star connection, phase voltage is equal to \_\_\_\_\_.

(d) The frequency of AC supply in India is \_\_\_\_\_.

(e) The power equation of a R-L-C series circuit is \_\_\_\_\_.

(f) Admittance is equal to the reciprocal of \_\_\_\_\_.

(g) In purely capacitive circuit, the power absorbed is equal to \_\_\_\_\_.

(h) Under resonance condition, in R-L-C series circuit, inductive reactance is equal to \_\_\_\_\_.

(i) When voltage applied to a purely inductive circuit is  $v = V_m \sin \omega t$ , the current flowing through it is  $i =$  \_\_\_\_\_.

(j) Superposition theorem can be applied only in a circuit containing more than one \_\_\_\_\_.

2 Write true or false :  $1 \times 10 = 10$

(a) The reciprocal of resistivity of a material is called its conductivity.

(b) One ampere means the flow of one coulomb each second.

41/EI-401/EC&N (O) (2)

(c) The lower the resistivity, greater the resistance.

(d) Voltage applied across a circuit, acts as a force.

(e) Specific resistance is measured in  $\Omega/\text{m}^3$ .

(f) Bandwidth is defined as the range of frequency within which the power delivered to R is greater than half the power at resonance.

(g) Any practical voltage source can be converted in to a practical current source and vice-versa.

(h) The formula used to express true power in a balanced 3-ph circuit is  $3V_p I_p \cos \Phi$ .

(i) Constant voltage source is active and bilateral.

(j) An ideal current source has zero internal resistance.

3. Choose the correct answers :  $1 \times 5 = 5$

(a) The Q-factor of a circuit is defined as

(i)  $\frac{\text{Reactive power}}{\text{Resistive power}}$  (ii)  $\frac{1}{R} \sqrt{\frac{L}{C}}$

(iii)  $\frac{2\pi f L}{R}$

(iv) All of these

41/EI-401/EC&N (O) (3)

[Turn over

PART - B

Marks - 45

(b) Current flowing in a series circuit having four equal resistance is 1-ampere, what is the magnitude of the current if the four resistances are connected in parallel ?

(i) 0.25I (ii) I

(iii) 4I (iv) 8I

(c) In a network, if the number of nodes is  $n$  and the number of branches is  $b$ , the number of independent mesh equations required to solve the network is

(i)  $b - n + 1$  (ii)  $b + n + 1$

(iii)  $b + n - 1$  (iv)  $b - n - 1$

(d) Thevenin's theorem can be applied to network containing

(i) passive elements only

(ii) active elements

(iii) linear element only

(iv) All of the above

(e) When maximum power transfer takes place, the efficiency of power transfer of the circuit is

(i) 100% (ii) 75%

(iii) 50% (iv) 25%

4 (a) Express the polar form of voltage  $V = 50 \angle 36.87^\circ$  in trigonometrical and rectangular forms. 4

(b) An R-L-C circuit consists of resistance of  $1K\Omega$ , an inductance of  $0.1H$  and a capacitance of  $10\mu F$ . If a voltage of  $100V$  is applied across the combination, find

(i) the resonant frequency

(ii) Q-factor of the circuit. 5

5 (a) State Kirchoff's laws, Thevenin's theorem and Superposition theorem. 4

(b) Find the value of load resistance  $R_L$  in Fig. I for transfer of maximum power. Determine also the maximum power. 5

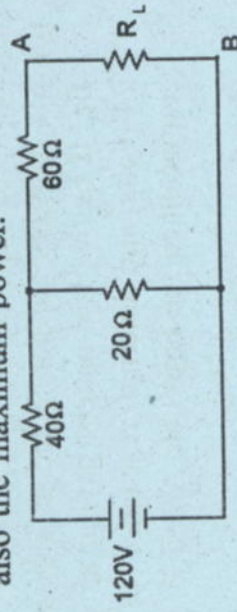


Fig. I

6. An impedance of  $(2 + j6) \Omega$  is connected in series with two impedances of  $(10 + j4) \Omega$  and  $(12 - j8) \Omega$  which are in parallel. Calculate the supply current and power factor if the circuit is connected to 200 volts. 9

7. (a) Write down the relationship between :

(i) the line voltage and phase voltage of a 3-phase balanced star and delta connected system.

(ii) the line current and phase current. 4

(b) Show that in both 3-phase star and 3-phase delta connected system 5

$$P = \sqrt{3} \cdot V_L \cdot I_L \cos \Phi$$

8. (a) Define R.M.S value, Form factor and Peak factor of an alternating quantity. 3

(b) Six resistors are connected as shown in the fig. II below. If a battery having an e.m.f of 24 volts and internal resistance of  $1 \Omega$  is connected to the terminals A and B, find :

(i) the current from the battery

(ii) p.d. across  $8 \Omega$  and  $4 \Omega$  resistors

41/EI-401/EC&N (O) (6)



(iii) the current taken from the battery if a conductor of negligible resistance is connected in parallel with  $8 \Omega$  resistor. 6

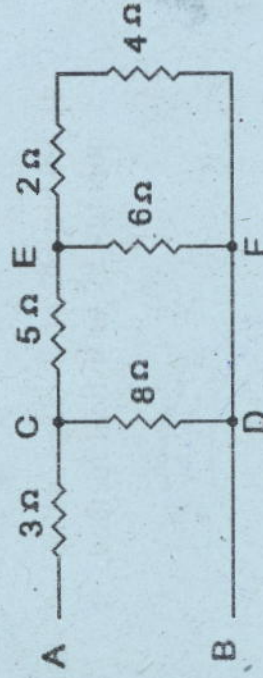


Fig.II

9. (a) What is the significance of the j-operator? 3

(b) A Wheatstone bridge ABCD is arranged as follows:  $AB = 1 \Omega$ ;  $BC = 2 \Omega$ ,  $CD = 3 \Omega$ ;  $DA = 4 \Omega$ . A resistance of  $5 \Omega$  is connected between B and D. A 4-volt battery of internal resistance  $1 \Omega$  is connected between A and C. Calculate

(i) the magnitude and direction of current in  $5 \Omega$  resistor and

(ii) the resistance between A and C. 6

41/EI-401/EC&N (O) (7)



10. Write short notes on any *three* : 3×3=9

- (a) Transient response on a R-L circuit
- (b) Norton's theorem
- (c) R-L-C series circuit
- (d) Deduction of average value of alternating quantity by analytical method.

