

Total No. of printed pages = 4

El-401/ECN/4th Sem/Elect/2017/M

ELECTRICAL CIRCUIT AND NETWORK

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer any *five* questions.

- (a) Define resistor and capacitor used in a circuit. 2

(b) A Wheatstone bridge circuit has $R_{AB} = 60\Omega$
 $= R_{CD}$; $R_{BC} = R_{AD} = 40\Omega$; $R_{BD} = 100\Omega$. Supply
is connected between A and C. If the current
drawn from the supply is 100 mA, find the
current through R_{CD} , R_{BC} and R_{BD} . 6

(c) Define parameters, linear circuits, bilateral
circuit and electric network. 6
- (a) State and explain Thevenin's theorem with
suitable diagrams. How does it differ from
Norton's theorem ? 5+2=7

[Turn over

- (b) The galvanometer in Fig.1 has a resistance of 5Ω . Find the current through the galvanometer using Thevenin's theorem. All resistances are in ohm. 7

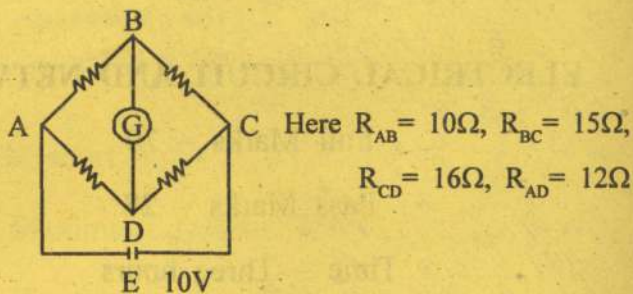


Fig. 1

3. (a) Deduce the expression of current, power angle, power and power curve when an A.C circuit containing resistance, pure inductance and capacitors only. 6
- (b) A chock coil having a resistance of 10Ω and inductance of 0.05H is connected in series with a capacitance of $100\ \mu\text{F}$. The whole circuit is connected to 200V , $50\ \text{Hz}$ supply. Calculate
- impedance
 - current
 - power factor
 - power input
 - apparent and reactive power. 8

4. (a) Describe any one method of solving parallel A.C circuits. 4
- (b) In a series-parallel circuit shown in Fig. 2, calculate
- Z_{AC}
 - I and branch current I_1 and I_2
 - power taken by each impedance and the total power
 - overall power factor of the circuit
 - V_{AB} and V_{BC} . 10

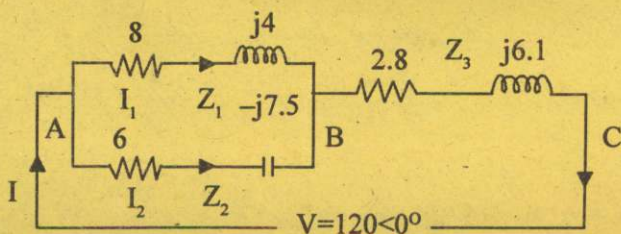


Fig. 2

5. (a) What do you mean by real, apparent and reactive power ? 6
- (b) What are the differences between series and parallel resonance ? 3
- (c) What are the different types of transients occur in a power system ? 5

6. (a) How delta can be converted into star connection ? 5

(b) What are the relationship of line and phase parameters in case of 3-phase balanced star and delta connected system ? 9

7. Write short notes on : $2 \times 7 = 14$

(a) Maximum power transfer theorem

(b) Resonance in parallel circuits.