

Retest Examination – 2020
Element of Electronic Engineering

Full Marks: 70

Time: Three hours

Subject code: Et - 304 (Old)

The figures in the margin indicate full marks for the questions.

PART - A
Marks - 25

All questions of PART - A are compulsory

1x10=10

1. Fill in the blanks

- i) Silver is a _____.
- ii) The base of a transistor is _____ doped.
- iii) A transistor has _____ junction.
- iv) The element that has the biggest size in a transistor is _____.
- v) Reverse bias is a condition that essentially _____.
- vi) The most commonly used semiconductor element is _____.
- vii) An amplifier is stable if the absolute magnitude of _____.
- viii) The unit of electrical conductance is _____.
- ix) A transistor is a _____ operated device.
- x) A (n) _____ is the simplest of semi-conductor devices.

1x10=10


2. Write true or false :

- i) Vacuum tube will only conduct if its anode is kept at a positive terminal with respect to cathode.
- ii) Example of an active device in electric bulb.
- iii) Integrated circuits are passive components.
- iv) The control element in a basic short voltage regulator is a Zener diode.
- v) The feedback component in an op-amp integrator is a capacitor.
- vi) A zero level detector is a type of comparator circuit.
- vii) Transformer coupling is used for voltage amplification.
- viii) A radio receiver has more than one stage of amplification.
- ix) Transformer coupling provides the maximum voltage gain.
- x) R.C. coupling is used for voltage amplification.

1x5=5

3. Choose the correct answer :

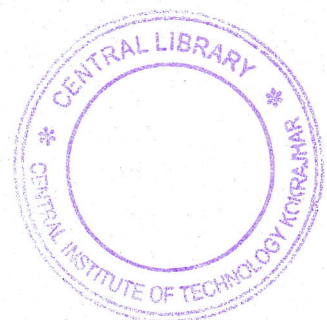- i) The number of depletion layers in a transistor is
a) four b) three c) one
- ii) In a PNP transistor, the current carries are
a) acceptor ions b) donor ions c) holes
- iii) A crystal diode has
a) one Pn junction b) two Pn junction c) three Pn junction
- iv) The forward current in a diode is of the order of
a) KA b) mA c) uA
- v) A vacuum diode can be used as
a) rectifier b) amplifier c) oscillator



PART - B
Marks – 45

(Any five from part-B)

- | | | |
|-----|--|-------|
| 4. | (a) What is electron emission ? What are the different types of electronic emission? | 6 |
| | (b) What are the active and passive components in electronic circuits? | 3 |
| 5. | (a) What is a vacuum diode ? | 3 |
| | (b) Describe the construction and working principle of a Zener diode. | 6 |
| 6. | (a) Explain the input and output characteristics of a transistor in CE configuration. | 6 |
| | (b) Define α and β for a transistor. | 3 |
| 7. | (a) Describe with circuit diagram, the operating principle of a full wave Center tapped rectifier. | 6 |
| | (b) Why filter circuits are used at the rectifier output ? | 3 |
| 8. | (a) Draw the input and output characteristics of a transistor in CC configuration and mark the cutoff saturation and active regions. | 6 |
| | (b) State the advantage of optocouples. | 3 |
| 9. | What is an amplifier? Based on the transistor configuration how amplifiers are classified. | 3+6=9 |
| 10. | Write short notes on any three of the following : | 3x3=9 |
| | a) Photo diode | |
| | b) Multistage amplifier | |
| | c) Bipolar Junction Transistor | |
| | d) Formation of P-N junction | |

