

	i) Increases iii) Remains same	ii) Decreases iv) None of the above	
c	The relation between α and β in BJT is i) $\alpha=1+\beta$ iii) $\beta=1+\alpha$	ii) Both (i) & (iii) are correct iv) None of the above.	
d	A BJT acts as an amplifier when it operates in i) Saturation region iii) Active region	ii) Cutoff region iv) None of the above	
e	A push-pull amplifier contains i) One transistor iii) Three transistors	ii) Two transistors iv) Four transistors	

PART - B

Question no.	Questions	marks
Question 4	Answer all the questions	2x5=10
a	Define intrinsic and extrinsic semiconductors.	
b	Draw the symbols of varactor and schottky diodes.	
c	Define Q-point in a transistor.	
d	What is pinch off voltage?	
e	What is crossover distortion?	
Question 5	Answer any five questions	3x5=15
a	Write the differences between zener breakdown and avalanche breakdown.	
b	Derive an expression to find the maximum rectifier efficiency of half wave rectifier.	
c	If $\beta=49$ and $I_E=1.5$ mA in a transistor, the find the values of α , I_B and I_C .	
d	Explain briefly the working of a CB transistor amplifier.	
e	Draw the basic structure of a UJT. Write one application of it.	
f	Discuss the frequency response of RC coupled transistor amplifier.	
g	Compare voltage amplifier with power amplifier.	
Question 6	Answer any four questions	5x4=20
a	Explain the operation of clamper circuits with appropriate diagrams.	
b	Draw a neat circuit diagram of centre tap full wave rectifier. Also explain its operation.	
c	Explain the formation of NPN transistor.	
d	Draw the circuit diagrams for n-channel and p-channel JFETs. Write the working principle of an n-channel JFET.	
e	With a neat circuit diagram, explain the working a transformer coupled transistor amplifier.	
f	Write short notes on- (i) Solar Cell, (ii) Complementary-symmetry amplifier.	

