

Total No. of printed pages = 6

RETEST EXAMINATION – 2019

Semester : 3rd (Old)

Subject Code : Et-304

**ELEMENTS OF ELECTRONICS
ENGINEERING**

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Instructions :

1. *All* questions of PART–A are compulsory.
2. Answer any *five* questions from PART–B.

PART – A

Marks – 25

1. Fill in the blanks : 1×10=10
 - (a) A pure semiconductor is known as _____.
 - (b) A semiconductor has _____ temperature coefficient of resistance.
 - (c) A semiconductor has generally _____ valence electrons.

[Turn over

- (d) An oscillator employs _____ feedback.
 - (e) ICs are generally made of _____.
 - (f) The SiO_2 layer in an IC acts as _____.
 - (g) The value of negative feedback fraction is always _____.
 - (h) Amplifiers use _____ feedback.
 - (i) A transistor has a β_{DC} of 250 and a base current, I_B , of $20 \mu\text{A}$. The collector current I_C equals _____.
 - (j) To operate properly, a transistor's base-emitter junction must be forward biased with reverse bias applied to _____ junction.
- 2 Write true or false : 1×10=10
- (a) A reverse biased diode will act as an open switch.
 - (b) P-terminal of P-N junction diode is known as cathode.
 - (c) Electrons in p-type material of a semiconductor are called as majority carriers.
 - (d) A donor to a semiconductor material is pentavalent.



- (e) The current gain of a PNP transistor is near zero.
 - (f) The emission of electrons from a heated source is thermionic emission.
 - (g) Ratio of small change in plate current to small change in plate voltage with constant plate voltage is known as transconductance.
 - (h) Function of focussing anode is to increase the brightness.
 - (i) Oscillator function is to convert DC to AC.
 - (j) Full form of CRO is Cathode Ray Oscillator.
3. Choose the correct answer : 1×5=5
- (a) When a pure semiconductor is heated, its resistance
 - (i) Goes up
 - (ii) Goes down
 - (iii) Remains the same
 - (iv) Initially goes up and then goes down

(b) In the depletion region of a P-N junction, there is a shortage of

- (i) Acceptor ions
 - (ii) Holes and Electrons
 - (iii) Donor ions
 - (iv) Electrons only
- (c) A zener diode is used as

- (i) an amplifier
 - (ii) a rectifier
 - (iii) a voltage regulator
 - (iv) a multivibrator
- (d) The ripple factor of a half-wave rectifier is

- (i) 1.21
 - (ii) 1.12
 - (iii) 0.48
 - (iv) 0.84
- (e) The maximum efficiency of a half-wave rectifier is
- (i) 81.2 %
 - (ii) 82.1 %
 - (iii) 40.3 %
 - (iv) 40.6 %

358/Et-304/EEE(O) (4) 300(W)

PART - B
Marks - 45

4. (a) Define semiconductor with examples. 1

(b) Explain P-type semiconductor with crystal diagram. 2

(c) Draw the block diagram of DC power supply. Describe the operation of each component. 6

5. (a) Define doping. 1

(b) Draw the V-I characteristics of P-N junction diode indicating knee voltage, reverse breakdown voltage. 2

(c) Explain the operation of bridge rectifier using circuit diagram and waveforms. 6

6. (a) Draw the symbol for PNP transistor. 1

(b) Explain the operation of NPN transistor. 4

(c) Draw the input and output characteristics of common base (CB) transistor. Explain it. 4

7. (a) What is the function of rectifier? 1

(b) What are the essential conditions of maintaining oscillations? 2

358/Et-304/EEE(O) (5) [Turn over

- (c) Explain the operation of vacuum triode ? 6
8. (a) What is multimeter ? Draw the circuits for the following : 1+4=5
- (i) Multimeter as voltmeter
 - (ii) Multimeter as ohmmeter.
- (b) Compare negative feedback with positive feedback. 4
9. (a) Discuss about working of Hartley oscillator with suitable diagram. 5
- (b) Explain about different types of biasing circuit of transistor. 4
10. Draw the block diagram of multistage amplifier. What are the variety types of coupling devices available in multistage amplifier and name them. With a diagram explain class B push pull amplifier. 2+2+5=9
11. Establish a relationship between α , β and γ . Write some applications of transistor amplifier ? 5+4=9
12. Write short notes on the following topics : 4½×2=9
- (i) Electronic Emission
 - (ii) RC coupled amplifier.