

Total No. of printed pages = 3

Et-304/EOEtE/3rd Sem/2013/N

**ELEMENTS OF ELECTRONICS
ENGINEERING**

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer any *five* questions.

- 1 (a) What are the active and passive components in electronic circuits ? 4
- (b) What is electron emission ? What are the different types of electron emission ? 5
- (c) Find the value of resistor whose band of sequence is as given below :
Brown / Black / Grey / Gold 5
2. (a) Give the procedure for determining the plate characteristics of a vacuum diode. 6
- (b) What are the limitations of vacuum triode and what are its applications ? 8

[Turn over

3. (a) Discuss the conduction properties of semiconductors and explain the process of electron-hole pair generation and recombination. 3
- (b) Discuss the behaviour of a p-n junction under forward and reverse biasing. 5
- (c) Define : 6
- (i) Intrinsic and extrinsic semiconductor
- (ii) Majority and minority carriers
- (iii) P-type and N-type semiconductor.
4. (a) Describe with a circuit diagram, the operation of a full-wave bridge rectifier. 7
- (b) What is a zener diode? How the zener diode is used as a voltage regulator ? 7
5. (a) What is transistor? Explain the operation of transistor as an amplifier. 6
- (b) With a neat circuit diagram, explain the working of RC coupled amplifier. 8

6. (a) What do you understand by Class A, Class B, Class C and Class AB amplifiers ? 8
- (b) What are the advantages of negative feedback ? 6
- 7 (a) Explain the construction and working of a cathode ray tube. 10
- (b) Draw the front panel view of a CRO and explain the function of each control switch. 4