

Total No. of printed pages = 6

RETEST EXAMINATION - 2019

Semester : 3rd (Old)

Subject Code : Et-305

ANALOG ELECTRONIC - I

Full Marks - 70

Time - Three hours

The figures in the margin indicate full marks
for the questions.

Instruction :

1. All questions of PART-A are compulsory.

PART - A

Marks - 25

1. (a) Fill in the blanks with appropriate words :
1×10=10

(i) When a trivalent impurity is added to a pure semiconductor, it becomes _____.

(ii) A semi-conductor is formed by _____ bonds.

[Turn over

- (iii) The reverse current in a diode is of the order of _____.
 - (iv) The efficiency of half wave rectifier is _____.
 - (v) _____ number of diodes are used in a full wave bridge rectifier.
 - (vi) In a transistor, the lead marked with the arrow is _____.
 - (vii) In a NPN-transistor, the current carriers are _____.
 - (viii) A multistage amplifier consists of _____ than one transistor.
 - (ix) LED stands for _____.
 - (x) Most widely used transistor configuration is _____.
- (b) Write true or false : 1×5=5
- (i) To remove the AC components in a rectifier circuit, a *filter circuit* is used.
 - (ii) The most commonly used semi-conductor is Germanium.
 - (iii) Best biasing method for transistor biasing is voltage divider method.
 - (iv) Most commonly used transistor configuration is CC configuration.



- (v) α value of a transistor is always greater than 1.
- (c) Choose the correct answer from the choices given below : 1×5=5
- (i) When a pentavalent impurity is added to a pure semi-conductor, it becomes _____.
 - (a) An insulator
 - (b) An intrinsic semi-conductor
 - (c) p-type semi-conductor
 - (d) n-type semi-conductor
- (ii) An ideal diode appears as an _____ when reversed biased.
 - (a) infinite resistance (b) zero resistance
 - (c) conductor (d) capacitor
- (iii) Which of the following correctly determines the relation between α and β ?
 - (a) $\beta = \alpha/(1-\alpha)$
 - (b) $\alpha = \beta/(1-\alpha)$
 - (c) $\beta = \alpha/(1-\beta)$
 - (d) None of the mentioned

(iv) For common emitter configuration, which of the following is the correct relation ?

- (a) $I_c < I_E$
- (b) $I_c = \beta I_B$
- (c) $I_c = \alpha I_E$
- (d) All of the mentioned

(v) The phase difference between the output and input voltages of a CE amplifier is _____.

- (a) 0°
- (b) 90°
- (c) 180°
- (d) 270°

(d) Match each of the item from LIST - A with each item in LIST - B : $1 \times 5 = 5$

LIST - A	LIST - B
(a) Semiconductor	(i) trivalent
(b) Boron	(ii) zener diode
(c) BJT	(iii) silicon
(d) Hartley	(iv) oscillator
(e) Special Purpose Diodes	(v) bipolar



PART-B

Marks - 45

2. Answer any five questions : $5 \times 5 = 25$

- (a) Discuss formation of N-type semi-conductor.
- (b) Explain and draw V-I characteristics of diode.
- (c) Explain a full wave rectifier with circuit diagram.
- (d) Classify the different types of transistor amplifier.
- (e) What is biasing ? Name the different types of biasing circuits of transistor. Draw any one of it.

- (f) A cascaded voltage amplifier having Gains $A_{v1}=10$, $A_{v2}=15$, $A_{v3}=20$. Determine overall voltage gain and Gain in Decibels.
- (g) Explain Voltage divider bias with a neat Circuit diagram.
- (h) Draw an oscillator tank circuit and explain.

3. Answer any two questions : $10 \times 2 = 20$

- (a) Explain with diagram the input and output characteristics of a transistor in CE configuration.

- (b) What is coupling? Explain any one of coupling amplifiers? Explain any one.
- (c) Explain the working of push pull power amplifier with a neat circuit.
- (d) What is positive feedback amplifier? Find its gain.



388/Et-305/AE-I(O)

(6)

500(W)