

Total No. of printed pages = 6

Et-305/AE-I/3rd Sem/ETC/2017/M

## ANALOG ELECTRONICS - I

Full Marks - 70

Pass Marks - 28

Time - Three hours

The figures in the margin indicate full marks for the questions.

Answer question Nos.1 and 2 and any *five* from the rest.

1. Fill in the gaps :

10

- (a) The electron in the outermost orbit of an atom are called ..... electron.
- (b) A pure semiconductor is also called ..... semiconductor.
- (c) The barrier potential for a silicon P-N junction is ..... volt.
- (d) Zener diodes are widely used as ..... regulators.
- (e) The maximum voltage that can be applied to a diode without destroying it is called .....

[Turn over

- (f) The turn on voltage of Ge function diode is nearly ..... volt.
- (g) Zener diode is operated in ..... region.
- (h) Ripple factor of a bridge rectifier is .....
- (i) In NPN transistor the emitter-to-collector carrier is the .....
- (j) The ratio of  $I_C$  and  $I_E$  gives the ..... of a transistor.

2. (A) Identify whether the following statements are true (T) or false (F): 6

- (i) Silicon has atomic number 14 and is half filled.
- (ii) A good biasing circuit should stabilize the  $I_C$  against variations in temperature.
- (iii) Class A operation gives more efficiency than class B operations.
- (iv) The decibel is a measure of voltage level.
- (v) Amplifiers are coupled to increase gain.
- (vi) For increasing the stability of an amplifier, positive feedback is employed.

(B) Choose the correct answer from the following :

4

(i) Which of the following will serve as a donor impurity in silicon ?

(a) Boron

(b) Indium

(c) Germanium

(d) Antimony

(ii) In a symbol of transistor, the sign of arrow shows :

(a) emitter

(b) base

(c) collector

(d) emitter and base both

(iii) The alpha ( $\alpha$ ) of a transistor is

(a) 1

(b) 0.99

(c) 20

(d) 0.1

- (iv) Oscillators use following feedback :
- (a) negative
  - (b) positive
  - (c) both
3. (a) What are N-type and p-type semiconductors ?  
Distinguish between Zener breakdown and avalanche breakdown. 3
- (b) Draw the V-I characteristic curve of Zener diode. 2
- (c) Draw the circuit diagram of a half-wave rectifier and explain its working giving input and output waveforms. What is its efficiency ? 5
4. (a) Draw a NPN and PNP transistor and label all the currents. Define  $\alpha$  and  $\beta$  of a transistor and derive the relationship between them. 2+3=5
- (b) Draw common emitter (CE) configuration of NPN transistor and draw its input and output characteristic curve. 2+3=5

5. (a) Draw the DC load line of a CE circuit. What is quiescent point ? 3
- (b) What are the essential conditions needed for biasing a transistor ? 2
- (c) Define stability factor. Draw and label a base bias with collector feedback circuit. 5
6. (a) Classify transistor based on its biasing conditions and distinguish among them. 5
- (b) In a two-stage cascaded amplifier, the first stage has a voltage gain of 2000 and second stage has voltage gain of 1000. Find the overall voltage gain in dB. Neglect the loading effect of first stage by the second stage. 5
7. (a) What are the various coupling schemes used in cascaded amplifier ? Draw the circuit diagram of each. 5
- (b) Draw the frequency response curve of an RC coupled amplifier and label it. 3
- (c) When a direct-coupled amplifier is used ? 2

8. (a) What is a feedback amplifier ? Derive an expression for the gain of an amplifier using negative feedback. 5
- (b) What is an oscillator ? How does it differ from an amplifier ? Draw the circuit diagram of a Hartley oscillator. 5
9. Write short notes on any *two* :  $2 \times 5 = 10$
- (a) How transistors amplifies the input signal ?
- (b) Vacuum tube
- (c) Push-pull amplifier
- (d) Special semiconductor diode.