

Total No. of printed pages = 5

Et-305/AE-I/3rd Sem/2017/N

ANALOG ELECTRONICS - I

Full Marks - 70

Time - Three hours

The figures in the margin indicate full marks for the questions.

PART - A

Marks - 25

All questions are compulsory.

1. Fill in the blanks : 1×10=10
- (a) A vacuum diode can be used as a _____.
 - (b) When an electron jumps from a higher orbit to a lower orbit, it _____ energy.
 - (c) In a type semiconductor _____ are the minority carriers.
 - (d) If pn junction is forward biased its resistance is _____.
 - (e) A full wave rectifier is _____ efficient than a half wave rectifier.

[Turn over

- (f) The output of a rectifier contains _____ and _____.
- (g) A transistor has _____ pn junctions.
- (h) The base of a transistor is _____ doped.
- (i) The intersection of the DC load line with the given base current curve is the _____.
- (j) RC coupling is used for _____ amplification.

2. Select the correct answer : $1 \times 10 = 10$

- (a) The screen grid potential is somewhat (lower/higher) than plate potential.
- (b) The addition of pentavalent impurity to a semiconductor creates (holes/electrons).
- (c) The frequency response of transformer coupling is (poor/good/excellent).
- (d) An oscillator produces (damped/undamped) oscillations.
- (e) An oscillator is a (rotating/non-rotating) device.
- (f) Negative feedback reduces (distortion/stability) in amplifiers.

- (g) The best frequency response is of (RC/ Direct/ Transformer) coupling amplifiers.
- (h) A Zener diode is operated in the (Breakdown/ Forward biased characteristics) region.
- (i) The maximum efficiency of a full wave rectifier is (40/81.2/90.1) per cent.
- (j) The function of a transistor is to (amplify/ rectify).

3. Answer true or false : 1×5=5

- (a) Forward resistance of a diode is quite large as compared to reverse resistance.
- (b) The current amplification factor in a CE configuration is given by α .
- (c) The RC coupled amplifier provides excellent audio fidelity over a wide range of frequency.
- (d) Semiconductor devices are sensitive to temperature variations.
- (e) When the feedback energy is out of phase with the input signal, it is called positive feedback.

PART - B

Marks - 45

Answer any five questions.

4. (a) Classify vacuum tubes and explain the working principle of any one among them.
- (b) Prove that $\mu = r_p \times g_m$. 2+4+3=9
5. (a) Explain the process of formation of an extrinsic semiconductor with arsenic being the impurity to be added.
- (b) Also explain the formation of the potential barrier. 5+4=9
6. (a) What are rectifiers ? Discuss the working principle of a half wave rectifier .
- (b) Also derive an expression for the efficiency of such a rectifier. 1+4+4=9
7. (a) Draw the input and output characteristic curve for a CE configuration.
- (b) Also derive a relationship between α , β , and γ . 5+4=9

8. (a) Explain the process of amplification of a signal by a single stage transistor amplifier.

(b) Define and explain the terms : Gain, Frequency response, and bandwidth in a multistage amplifier. $3+6=9$

9. (a) Define positive and negative feedback.

(b) Derive an expression for the gain of an amplifier with feedback.

(c) Discuss in brief the process of generation of oscillations in a tank circuit. $2+4+3=9$

10. Write short notes on any two : $4\frac{1}{2}\times 2=9$

(i) Zener diode.

(ii) Filters.

(iii) Hartley Oscillator.