

Total No. of printed pages = 6

RETEST EXAMINATION - 2019

Semester : 4th (Old)

Subject Code : Et-403

DIGITAL ELECTRONICS

Full Marks - 70

Time - Three hours

The figures in the margin indicate full marks for the questions.

Instruction :

1. All questions of PART - A are compulsory.

PART - A

Marks - 25

1. Multiple choice questions : 1×5=5
 - (a) The number of cells of a four variable K-map is
 - (i) 4
 - (ii) 8
 - (iii) 16
 - (iv) 20

[Turn over

(b) In Excess-3 code the decimal equivalent of 46 is

- (i) 1000 0110 (ii) 0110 1001
(iii) 0100 0110 (iv) 1001 1000

(c) How many bits are required to store one BCD digit

- (i) 1 (ii) 2
(iii) 4 (iv) 8

(d) In SR flip-flop which condition is not allowed?

- (i) $S=R=0$ (ii) $S=0, R=1$
(iii) $S=1, R=0$ (iv) $S=R=1$

(e) Which one of the following is the De-Morgan's theorem

- (i) $\overline{AB} = AB$
(ii) $\overline{A+B} = \overline{AB}$
(iii) $AB = \overline{A+B}$
(iv) $\overline{A+B} = A+B$

292/Et-403/DE(O) (2)

2. Write true or false:

$1 \times 10 = 10$

- (a) 2's complement of $(1000)_2$ is $(1000)_2$.
(b) Gray code of decimal digit 6 is 0011.
(c) In signed binary numbers, MSB is the sign bit.

(d) A seven segment display consist of seven LED.

(e) IC 74138 is a multiplexer IC.

(f) A decoder as demultiplexer.

(g) Memory is an example of combinational logic.

(h) Clear signal is same as reset signal.

(i) In a synchronous counter all the flip-flops are clocked together.

(j) Logic gat can be used as electronics switched.

3. Fill in the blanks :

$1 \times 10 = 10$

(a) ROM is a _____ memory.

(b) The octal equivalent of binary number (1001010) is _____.

292/Et-403/DE(O) (3)

Turn over

- (c) ASCII stands for _____.
- (d) Each term in SOP form is called _____.
- (e) Race around condition is occurred in _____ flip-flop.
- (f) A Giga byte equals _____ bytes.
- (g) A full Adder consists of _____ gates.
- (h) Flip-flop can be used as _____.
- (i) Nand and NOR gate is called _____.
- (j) $10010.11_2 + 1000.01_2 =$ _____.

PART - B
Marks - 45

4. Convert the following : 2×5=10

- (a) 10111011_2 into gray code
- (b) 255_{10} into hexadecimal code
- (c) 352_8 into decimal
- (d) 10111011_2 into 2's complement from
- (e) 625.25_{10} into binary.

292/Et-403/DE(O) (4) 300(W)



5. Answer any *three* questions : 3×5=15

- (a) Give the difference between static and dynamic RAM.
- (b) With symbol and truth table, define OR, NOR and EX OR gate.
- (c) Prove using Boolean algebra $A + \bar{A}B = A + B$.
- (d) Distinguish between synchronous and asynchronous counter.

Answer any *four* questions : 4×5=20

- (a) What is flip-flop ? Describe JK flip-flop with circuit diagram and truth table.
- (b) Minimise the following logic function using K-Map method.
 $f(A,B,C,D) = (0,1,2,4,5,7,8) + d(10,11,14)$
- (c) What is shift register ? Explain any one type of shift register with neat diagram.
- (d) What is a counter ? Explain the principle of a 4-bit counter.

292/Et-403/DE(O) (5) [Turn over

- (e) What is multiplexer? Draw and explain the logic circuit of a 4:1 multiplexer.
- (f) Write short note on any *one* of the following :
- (i) LED and LCD
 - (ii) TTL circuit
 - (iii) A/D converter.

