

Total No. of printed pages = 6

Et-403/DE/4th Sem/2018/M

DIGITAL ELECTRONICS

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks for the questions.

PART – A

Marks – 25

Answer *all* questions.

1. Multiple choice questions : 1×5=5

(a) How many entries will be in the truth table of a 3 input NAND gate ?

(i) 3

(ii) 6

(iii) 8

(iv) 9

(b) How many bits are required to store one BCD digit ?

(i) 1

(ii) 2

(iii) 3

(iv) 4

[Turn over

- (c) In binary number system the first digit (bit) from right to left is called as
- (i) LSB (Least significant bit)
 - (ii) MSB (Most significant bit)
 - (iii) First bit
 - (iv) Last bit
- (d) In an SR latch built from NOR gates, which condition is not allowed ?
- (i) $S=0, R=0$
 - (ii) $S=0, R=1$
 - (iii) $S=1, R=0$
 - (iv) $S=1, R=1$
- (e) Which of these sets of logic gates are designated as universal gates ?
- (i) NOR, NAND.
 - (ii) XOR, NOR, NAND.
 - (iii) OR, NOT, AND.
 - (iv) NOR, NAND, XNOR.

2. Fill in the blanks :

1×5=5

- (a) The digit that changes most often when counting, is called the _____.
- (b) Memory devices that use electronic latching circuits are called _____.
- (c) If a HIGH logic level is assigned a binary zero (0), and a low level is assigned a binary one (1), the logic is called _____.
- (d) A binary number can be converted to be viewed on a 7-segment display by a (n) _____.
- (e) _____ is the highest-value seven-bit binary number.

3. State true or false :

1×5=5

- (a) The voltage levels used to represent binary values (0 and 1) in a digital system are nearly equal in value.
- (b) Temperature variation is normally an analog quantity.
- (c) Transistor-transistor logic (TTL) uses the bipolar transistor as its main circuit element.

- (d) With an OR gate, the output is HIGH only when both inputs are HIGH.
- (e) Digital circuits cannot perform logic comparisons since the circuit can have only one of two values at any instant.

4. Answer the following questions : $1 \times 10 = 10$

- (a) What is the base in binary number system ?
- (b) What are the advantages of gray code over binary ?
- (c) What is the maximum number that can be counted using 10 bits ?
- (d) Give another name for digital circuit.
- (e) Which gates can be combined to give a NAND gate ?
- (f) What is the full form of ECL ?
- (g) How many gates does a full adder have ?
- (h) What is tristate logic ?
- (i) What is a LCD ?
- (j) Draw symbol of a Clock D latch.

PART – B

Marks – 45

Instruction : The answers should be comprehensive and criteria for valuation are the contents but not the length of the answer.

5. Answer any *five* questions of the following :

$3 \times 5 = 15$

- (a) Convert the decimal numbers 268, 39 into hexadecimal.
- (b) What is meant by 1's complements and 2's complements ? Explain.
- (c) What is an exclusive NOR gate ? How it can be realized ? Show truth table of 2 inputs X-NOR gate.
- (d) Name some important specification of digital IC.
- (e) Explain the working of CMOS NAND gate.
- (f) Draw the circuit of a full adder and explain its working.

6. Answer any *three* questions of the following :

$5 \times 3 = 15$

- (a) What are Demorgan's Theorems ? Write them in equation form. Prepare their truth table to prove their correctness.

- (b) Plot on Karnaugh Map $Y(A, B, C, D) = \sum m(0, 2, 3, 6, 8, 9, 14, 15)$.
- (c) What is an encoder ? Draw the logic circuit of decimal to BCD encoder and explain its working.
- (d) Draw common anode circuit of LED seven segment display.
- (e) What is JK master slave flip-flop ? Draw its logic circuit and explain its working.
7. Answer any *two* of the following : $7.5 \times 2 = 15$
- (a) Draw and explain the logic circuit of a 4:1 multiplexer.
- (b) Draw the circuit of a 4-bit ripple counter. Explain its working. Draw its timing diagram.
- (d) Explain the various parameters of flip-flops.
- (e) What is a register ? What are the various types of registers ? Explain the working of any one of them.
- (f) How is computer memory classified ? Explain them.