

Total No. of printed pages = 6

Et-405/AE-II/4th Sem/2017/N

ANALOG ELECTRONICS – II

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks
for the questions.

PART – A

1. State true or false : 1×7=7
- (i) FETs are bipolar device.
 - (ii) A differential amplifier is basically a direct-coupled amplifier.
 - (iii) In an ideal Op-Amp the output should be zero when both the inputs are grounded.
 - (iv) The output of an unregulated DC power supply is pulsating DC.
 - (v) A differentiator circuit is also a high-pass filter.

[Turn over

- (vi) Bi-stable multivibrators are also called free-running multivibrators.
- (vii) Schmitt trigger circuit can be used for converting sine-wave to a square-wave.

2. Fill up the gaps : 1×8=8

- (i) In a UJT, the semiconductor bar is _____ doped.
- (ii) In a JFET, the drain current is _____ when gate-to-source voltage is zero.
- (iii) The ability of a differential amplifier to reject _____ signal is expressed by a ratio called CMRR.
- (iv) _____ has been considered as mostly used industry standard Op-Amp IC.
- (v) An IC-7912 is used to obtain _____ volt DC regulated output.
- (vi) A _____ circuit removes the portion of a given waveform.
- (vii) In multivibrators the trigger signal is applied to the _____ of one of the transistors.
- (viii) A _____ deflection system uses a sweep signal as the horizontal sweep signal.

3. Choose the correct answer : $1 \times 10 = 10$

(i) When a UJT is turned on, the resistance between the emitter and lower base terminal

- (a) increases
- (b) decreases
- (c) becomes infinite
- (d) remains the same

(ii) In enhancement n-channel MOSFET, an induced channel is created if

- (a) $V_{GS} = 0$
- (b) V_{GS} is negative
- (c) V_{GS} is positive
- (d) None of these

(iii) The output of a differential amplifier is proportional to the

- (a) differentiation of input signal
- (b) multiplication of the two input signals
- (c) difference of the two input signals
- (d) sum of the two input signals

- (vii) A clamping circuit is used to
- (a) remove a portion of a waveform,
 - (b) shifts the average level of a signal
 - (c) amplifies a signal,
 - (d) changes the shape of a waveform
- (viii) Multivibrators belongs to the category of
- (a) Sinusoidal oscillators
 - (b) Triangular wave oscillators
 - (c) Ramp oscillators
 - (d) Square wave oscillators
- (ix) One of the followings can be used to generate a pulse whenever triggered
- (a) Mono-stable multivibrator
 - (b) Bi-stable multivibrator
 - (c) Astable multivibrator
 - (d) Schmitt Trigger
- (x) A sweep signal generator produces
- (a) DC signal
 - (b) Square waves
 - (c) Sinusoidal waves
 - (d) Triangular waves

PART – B

Answer any *three* questions.

1. Classify Field Effect Transistor (FET) and explain the working of a MOSFET. 15

2. Mention the characteristics of an ideal Operational Amplifier. Also, explain how an Op-Amp can be used as an Adder and as a Differentiator. 5+10=15

3. What are Clipping and Clamping circuits ? Explain. Also explain the working of a combinational biased clipper. 6+9=15

4. Differentiate between the three types of multi-vibrators and using neat circuit and waveforms explain the working of any one of them. 3+12=15

5. Write short notes on any *two* from the followings : 2×7½=15
 - (a) BJT V/s FET
 - (b) Differential amplifier
 - (c) DC Voltage Regulators
 - (d) RC High-Pass and Low-Pass Filter
 - (e) Schmitt Trigger.