

Total No. of printed pages = 2

ET-405/AE-II/4th Sem/2013/N

## ANALOG ELECTRONICS – II

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

1. What is a field effect transistor ? How does it differ from a BJT ? Explain the construction and working of JFET. 2+2+5+5=14
2. Mention the characteristics of an ideal operational amplifier. Draw the circuit diagram of a differentiator and an integrator using OP-AMP and deduce the expression for the output voltage of each circuit. 4+10=14
3. What are the different types of filter circuits ? Explain with proper characteristic curves. Also explain the working of RC low pass filter. 4+4+6=14

[Turn over

4. What is Schmitt trigger ? What are its applications ? Explain the operation of a transistorized Schmitt trigger circuit.

$$3+3+8=14$$

5. What is a Multivibrator ? What are its types ? Explain the operation of any one of them.

$$3+3+8=14$$

6. What is a voltage regulator ? Why do we need this in a circuit ? Explain the working of a transistorized DC voltage regulator circuit.

$$2+2+10=14$$

7. Write short notes on any *two* :  $7 \times 2 = 14$

- (a) UJT
- (b) Diode clamper circuit
- (c) Sweep signal generation
- (d) Differential amplifier
- (e) Depletion type MOSFET.