

Total No. of printed pages = 3

ET-403/DE/4th Sem/2013/N

DIGITAL ELECTRONICS

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

1. (a) Convert the following : 2×5=10
 - (i) $(257)_8$ to decimal
 - (ii) $(2AB.IF)_{16}$ to binary
 - (iii) 10101011_2 to Gray code
 - (iv) $(57)_{10}$ to Ex-3 code
 - (v) 1011011.10_2 to octal
- (b) (i) Subtract 5 from 9 using 2's complement method. 2
- (ii) Subtract 5 from 9 using 1's complement method. 2
2. (a) Define De Morgan's theorem and prove it with logic circuit and truth table. 4

[Turn over

- (b) Realize the equation
 $Y = A\bar{B} + B\bar{C} + C\bar{A}$ using only NAND and NOR gates. 4
- (c) Convert the equation
 $Y = ABC + A\bar{B}D + BC + AD$ into standard SOP form. 4
- (d) What is K-map? 2
3. (a) Minimize the logic function
 $F(A, B, C, D) = \sum m(0, 1, 4, 5, 7, 8) + d(10, 11, 14)$ by using K-map. 7
- (b) What is full adder? Explain it with proper circuit and truth table. 5
- (c) What is duality theorem? 2
4. (a) Classify various types of memory and explain the magnetic memory in details. What is cache memory? 5+2=7
- (b) What is counter? Describe any one type of synchronous counter in details. 5
- (c) What is a Ring counter? 2

5. (a) Why flip-flop is called 1-bit of memory cell? Describe the operation of a clocked S-R flip-flop. $2+4=6$
- (b) What is race around condition in J-K flip-flop ? How can it be overcome ? Explain. $3+5=8$
6. (a) Explain the operation of a 4-bit serial in serial out shift register. 6
- (b) Explain the operation of an analog to digital converter using neat diagram. 6
- (c) Differentiate sequential logic circuit and combinational logic circuit with examples. 2
7. Write short notes on any *four* : $3\frac{1}{2}\times 4=14$
- (a) Seven segment display
- (b) TTL IC and CMOS IC
- (c) D/A converter
- (d) PROM
- (e) Multiplexer.