

Total No. of printed pages = 2

Et-503/PE/5th Sem/ETC/2017/M

POWER ELECTRONICS

Full Marks - 70

Pass Marks - 28

Time - Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

- (a) What is a SCR ? Explain the construction and working of SCR with a neat circuit diagram. 2+5=7

(b) Explain the two transistor analogy of a thyristor with a proper diagram. Also derive the equation for anode current. 4+3=7
2. What is controlled in a controlled rectifier ? Explain the working of a 1ϕ half-wave controlled rectifier with a purely resistive load. Also draw the waveform of input voltage, firing pulses, output voltage and load current. 2+8+4=14

Turn over

3. What is an inverter ? Discuss the working of voltage driven and current driven inverter with a neat circuit diagram. Also state its applications.
 $2+10+2=14$
4. What is an UPS ? How are they classified ? State some of its uses. Explain the working of online and offline UPS with a proper diagram.
 $1+2+2+9=14$
5. What is an SMPS ? What are the configurations of SMPS ? Explain any two of them.
 $2+2+5+5=14$
6. State and explain the different methods of speed control of a D.C motor. 14
7. (a) Write the comparison of linear and switching power supply. 4
- (b) Explain buck and boost regulator with a proper circuit diagram. 10
8. Write short notes on any *two* : $2 \times 7 = 14$
- (a) GTO
- (b) IGBT
- (c) Power MOSFET
- (d) Snubber circuit.