

Total No. of printed pages = 5

Et-503/PE/5th Sem/2018/M

## POWER ELECTRONICS

Full Marks - 70

Time - Three hours

The figures in the margin indicate full marks for the questions.

PART - A

Marks - 25

1. Multiple choice questions : 1×5=5
- (i) TRIAC can not be turned on
- (a) By applying a positive signal at the gate
  - (b) By applying a negative signal at the gate
  - (c) By applying either positive gate or negative signal at the gate
  - (d) None of the above
- (ii) Power MOSFETs find application in
- (a) High power high frequency applications
  - (b) Low power high frequency applications

[Turn over

- (c) High power low frequency applications
  - (d) Low power low frequency applications
- (iii) In a 3-phase full wave rectifier
- (a) Each diode conducts for  $120^\circ$
  - (b) Each diode conducts for  $60^\circ$
  - (c) Each thyristor conducts for  $120^\circ$
  - (d) None of the above is correct
- (iv) UPS is never used in
- (a) Street lighting
  - (b) Computers
  - (c) Communication link
  - (d) Instrumentation
- (v) Free wheeling diode is useful when the load is
- (a) Inductive
  - (b) Capacitive
  - (c) Resistive
  - (d) None of the above

2. State whether the following statements are true or false : 1×10=10

- (a) To turn off SCR it is necessary to reduce holding current.
- (b) A GTO can be turned off by a positive gate pulse.
- (c) A TRIAC has two terminals.
- (d) A single phase half bridge inverter uses two thyristors.
- (e) In a controlled rectifier allows variations of output voltage by variation of firing angle of thyristors.
- (f) The use of free wheeling diodes improves the wave shape of the load current.
- (g) An UPS is invariably needed for critical loads.
- (h) A switching regulator is a dc-dc converter.
- (i) The speed of a DC motor can be controlled by varying either the armature voltage or the field current.
- (j) A SMPS is a multistage power supply.

3. Fill in the blanks :

1×10=10

- (a) An IGBT is a ..... controlled device.
- (b) CMOS stands for .....
- (c) A SCR is two ..... analogy.
- (d) A TRIAC is a ..... thyristor.
- (e) An AC regulator is an ..... converter.
- (f) A 3-phase inverter can operate in ..... mode or ..... mode.
- (g) A snubber circuit is a ..... circuit.
- (h) The conversion of ac to dc is known as .....
- (i) An inverter is a ..... to ..... conversion.
- (j) A switching regulator converts an ..... dc voltage to ..... dc voltage.

PART – B

Marks – 45

- 1. Explain the construction and principle of operation of a thyristor with a proper diagram. 4
- 2. Discuss the operation of a TRIAC. 4

3. Explain the working of a 1 phase full wave controlled rectifier with proper circuit diagram. 4
4. What is an inverter ? Classify inverter. 4
5. Explain the working of a voltage source inverter with proper circuit diagram. 5
6. Explain buck and boost regulator in brief.  $2+2=4$
7. What is an UPS ? Classify UPS. Explain the working of online UPS.  $2+2+2=6$
8. What is SMPS ? What is its utility ? 4
9. What is an AC regulator ? Give some of its applications.  $2+3=5$
10. State the various methods of speed control of DC motors. 5