

Total No. of printed pages =



END SEMESTER EXAMINATION - 2019

Semester : 5th

Subject Code : Et-503

POWER ELECTRONICS

Full Marks - 70

Time - Three hours

The figures in the margin indicate full marks for the questions.

Instructions :

1. *All* questions of PART - A are compulsory.
2. Answer any *five* questions from PART - B

PART - A

Marks - 25

1. Fill in the blanks : 1×10=10

(a) The operation of SCR can be explained by _____ .

(b) A DIAC is used to trigger _____ .

[Turn over

- (c) A thyristor can be turned on by _____ gate signal.
- (d) The _____ diode is connected across the load.
- (e) An IGBT has _____ losses as well as low switching time.
- (f) Rectifier circuits using thyristors are known as _____ rectifiers.
- (g) An inverter is a _____ converter.
- (h) A SMPS is a multistage _____ power supply.
- (i) A _____ regulator gives an output voltage which is less than input voltage.
- (j) UPS stands for _____.

2. Write true or false : $1 \times 10 = 10$

- (a) SCR is a unidirectional device.
- (b) A TRIAC has two terminals.
- (c) A parallel inverter uses a transformer.
- (d) A Single phase half-bridge inverter uses two thyristors

294/Et-503/PE

(2)



- (e) A switching regulator uses PWM.
- (f) An UPS is invariably needed for critical loads.
- (g) A switching regulator can be buck, boost and buck-boost.
- (h) In a series inverter the circuit is under damped.
- (i) A SMPS is a multistage power supply.
- (j) SMPS stands for Single Mode Power Supply.

3. Choose the correct answer : $1 \times 5 = 5$

- (a) IGBT is a
- (i) voltage controlled device
- (ii) current controlled device
- (iii) power controlled device
- (iv) All of the above
- (b) The number of thyristors in a single phase fully controlled bridge rectifier is
- (i) 16
- (ii) 8
- (iii) 4
- (iv) 2

294/Et-503/PE

(3)

[Turn over

(c) An RC snubber circuit is used to protect a thyristor against

- (i) false triggering
 - (ii) failure to turn on
 - (iii) switching transients
 - (iv) failure to commutate
- (d) UPS is never used in

- (i) street lighting
- (ii) computers
- (iii) Communication link
- (iv) instrumentation

(e) Triac is a

- (i) Bi-directional switch
- (ii) Uni-directional switch
- (iii) Mechanical switch
- (iv) None of the above

294/Et-503/PE

(4)

500(W)

PART – B
Marks – 45

4. (a) What is a power diode ? 2

(b) How is power diode classified ? Give the main features of each type. 5

(c) Name some applications of power diode. 2

5. (a) Name any four members of a thyristor family. 4

(b) Draw the symbols of SCR, Diac, Triac and IGBT. 2

(c) Explain the two transistor analogy of a thyristor. 3

6. (a) What is a controlled rectifier. 2


(b) Explain the working of a single phase full wave controlled rectifier feeding purely resistive load. 5

(c) Draw the waveform diagram of input voltage, output voltage, output current and gate current. 2

294/Et-503/PE

(5)

[Turn over

- 
7. (a) What is an inverter? 4
(b) Give a brief classification of inverter.
(c) Explain three phase bridge inverter with a proper circuit diagram. 4
8. (a) Explain the working of a shunt regulator with a proper circuit diagram. 5
(b) What is SMPS? Name some commonly used configurations of SMPS. 4
9. (a) What is UPS? How is it classified? 5
(b) Explain the working of OFF-LINE UPS with a proper diagram. 4
10. What is an AC regulator. Give some of its applications. 9
11. What is a stepper motor? Explain the principle of operation of a stepper motor. 9
12. Write a note on switching regulator and servo regulators. 9