

Total No. of printed pages = 5

EI-304/EEE/3rd Sem/2016/N

ELEMENTS OF ELECTRICAL ENGINEERING

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer question No.1 and any *five*
from the rest.

1. Fill in the blanks : 1×10=10

- (i) Current flows from _____ to _____ .
- (ii) The power consumed by a purely inductive circuit is _____ .
- (iii) In a purely resistive circuit, the angle between current vector and voltage vector is _____ .
- (iv) The voltage of a cell when fully charged is _____ .
- (v) Kirchoff's voltage law can be applied in _____ circuit only.

[Turn over

- (vi) An ideal transformer is one which has _____.
- (vii) At series resonance, circuit current is _____.
- (viii) One kilowatt-hour of electrical energy is _____ Joule.
- (ix) The value of crest factor is _____.
- (x) The conductor has _____ temperature coefficient of resistance.

2. (a) Define conductor and insulator. 4
- (b) Write down the industrial use of conductor and insulator. 4
- (c) The following are details of load on a circuit connected through a supply meter :
- (i) 8 lamps of 60 watt each working for 8 hours per day.
- (ii) 5 fluorescent tubes of 40 watt each working for 5 hours per day.

If each unit of energy cost is Rs. 6.00, what will be the monthly electricity bill ? 4

3. (a) Define Kirchhoff's current law. 2
- (b) Determine the algebraic sign of voltage drop in applying Kirchhoff's voltage law. 2
- (c) A Wheatstone bridge ABCD is arranged as follows :
- $AB = 15\Omega$, $BC = 20\Omega$, $CD = 10\Omega$, and $DA = 15\Omega$.
- A galvanometer of resistance 5Ω is connected between B and D. A 100 volt supply of negligible internal resistance is connected between A and C with A positive. Applying Kirchhoff's laws find the magnitude and direction of galvanometer current. 8
4. (a) Deduce the equation of alternating voltage. 4
- (b) Define r.m.s value and form factor. 2
- (c) An alternating current is given by $i = 20 \sin 314t$. Determine the maximum value, r.m.s value, frequency and time period. 6

5. (a) A coil having a resistance of 7Ω and an inductance of 31.8 mH is connected to 230V , 50 Hz supply. Calculate inductive reactance, impedance, circuit current, power factor and power consumed. 7
- (b) Define series resonance. 2
- (c) An R-L-C series circuit consists of a resistance of 1000Ω , an inductance of 100 mH and a capacitance of 10 microfarad . If a voltage of 200V is applied across the combination, find the resonance frequency. 3
6. (a) Deduce the e.m.f equation of transformer. 5
- (b) Describe the short circuit test of a transformer. 4
- (c) A single phase $2200 / 250\text{V}$, 50 Hz transformer has a net core area of 36 cm^2 and a maximum flux density of 6 wb/m^2 . Calculate the number of turns of primary and secondary winding. 3

7. (a) Deduce the e.m.f equation of a DC generator. 4
- (b) What are the types of DC motor and draw the circuit diagram of these. 4
- (c) Write down the working principle of DC motor. 4