

Total No. of printed pages = 5

EI-401/ECN/4th Sem/2016/N

ELECTRICAL CIRCUIT AND NETWORK

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer question No.1 and any *four* from the rest.

1. Fill in the blanks : $1 \times 10 = 10$
- (i) The power equation of R-L-C series circuit is $P = \underline{\hspace{2cm}}$.
 - (ii) Admittance is equal to the reciprocal of $\underline{\hspace{2cm}}$.
 - (iii) Super position theorem can be applied only in $\underline{\hspace{2cm}}$ circuit.
 - (iv) In delta connected three-phase system, the line voltage = $\underline{\hspace{2cm}}$.
 - (v) $VI \sin \phi$ is called $\underline{\hspace{2cm}}$ power.
 - (vi) A linear circuit is one whose parameters are constant, they do not change with $\underline{\hspace{2cm}}$ or $\underline{\hspace{2cm}}$.

[Turn over

(vii) Number of cycles per second is called _____.


(viii) An ideal voltage source has _____ internal resistance.

(ix) A network having one or more than one source of e.m.f is known as _____ network.


(x) Equivalent dynamic impedance of parallel circuit at resonance is given by _____.

2. (a) State and explain the Thevenin's theorem. 7

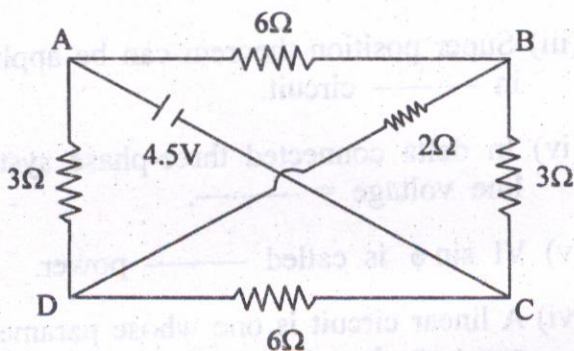(b) ABCD is a rectangle whose opposite sides AB, DC represent resistance of 6Ω each, while AD and BC represent 3Ω each. A battery of e.m.f 4.5V and negligible resistance is connected between diagonal points A and C and 2Ω resistance between B and D. Find the magnitude and direction of current in the 2Ω resistor by using Thevenin's theorem. 8



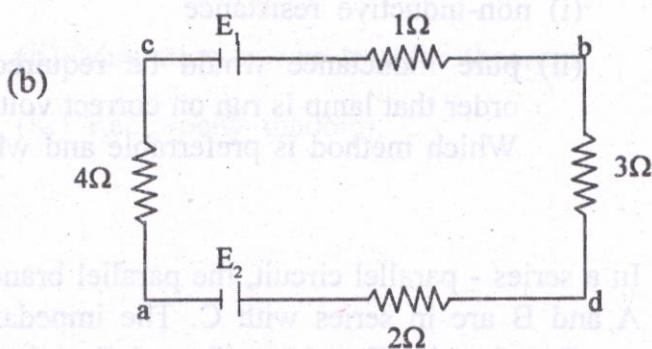3. (a) State and explain Kirchoff's laws. 7



In the above figure, the voltage rise from a to b is 16.0 volt and that from c to d is 17.4 volt. Determine

- the magnitude of each e.m.f E_1 and E_2 .
 - the daily energy output in watt-hour of the part cb .
- 8

4. (a) Define the following terms : $2 \times 3 = 6$

- Phase difference
- Form factor
- J-operator.

(b) A 120V, 60W lamp is to be operated on 220V, 50 Hz supply mains. Calculate what value of

(i) non-inductive resistance

(ii) pure inductance would be required in order that lamp is run on correct voltage.

Which method is preferable and why ?

9

5. In a series - parallel circuit, the parallel branches A and B are in series with C. The impedances are $Z_A = 4 + j3$, $Z_B = 10 - j7$, and $Z_C = 6 + j5$.

If the voltage applied to the circuit is 200V at 50 Hz, calculate

(a) Current I_A , I_B and I_C

(b) The total p.f for the whole circuit. 15

6. (a) Establish the relationship between 8

(i) Line current and phase current

(ii) Line voltage and phase voltage of three phase star and delta connected system.

(b) Prove that the resonance frequency of a parallel circuit is given by 7

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

7. Write short notes on any *two* : $7\frac{1}{2} \times 2 = 15$

- (i) Transient response in R-L circuit
- (ii) Maximum power transfer theorem
- (iii) Reciprocity theorem.