

Total No. of printed pages = 3

Et-304/E.Et.E/3rd Sem/2015/M

**ELEMENTS OF ELECTRONICS
ENGINEERING**

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer any *five* questions.

1. (a) What are the active and passive components of electronic circuits ? 4
- (b) What is electron emission ? What are the different types of electron emission ? 4
- (c) A resistor has a colour band sequence : brown, green, grey and gold. Find the range in which its value must lie depending upon the manufacturer's tolerance to suit a circuit. 6

[Turn over

2. (a) Describe the construction of a vacuum diode with suitable diagram. 6
- (b) Describe how control grid controls the operation of a vacuum triode. 6
- (c) What is the function of screen grid in a vacuum tetrode ? 2
3. (a) What do you mean by conductor, insulator and semiconductor ? 3
- (b) What is a p-n junction and how it is formed ? Describe with a neat diagram. 1+5=6
- (c) Define P-type and N-type semiconductors with suitable diagram. 5
4. (a) Draw the circuit diagram and explain the construction and operation of a bridge type full wave rectifier. 7
- (b) What is a Zener diode and what are the characteristics of it ? How a Zener diode can be used for wave shaping ? 7
5. (a) Draw common emitter (CE) configuration of transistor. 2

- (b) Define class A, class B and class C amplifier. 6
- (c) With a neat circuit diagram, explain the working of RC coupled amplifier. 6
6. (a) Describe the construction and operation of a Colpitt's oscillator. 8
- (b) What are the advantages of negative feedback? 6
7. Write short notes on any two : $7 \times 2 = 14$
- (i) Cathode ray tube
- (ii) Push-pull amplifier
- (iii) Colour coding of resistor
- (iv) Behaviour of p-n junction under biasing.