

Total No. of printed pages = 3

Et-304/EEtE/3rd Sem/2014/N

**ELEMENTS OF ELECTRONICS
ENGINEERING**

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer any *five* questions.

1. (a) How resistances are colour coded ? Write the colour coding table of resistances. 3+5=8
- (b) A resistor has a colour band sequence of yellow, brown, blue and silver. Find the range of the resistance of the resistor. 6
2. (a) Describe with diagram the plate characteristic of vacuum diode. 7
- (b) Describe the construction of vacuum triode. 5
- (c) Find the relationship between μ , r_p and gm of vacuum tube constants. 2

[Turn over

3. (a) What do you mean by semiconductor and what are the properties of semiconductors ?
2+3=5
- (b) Describe the volt-ampere characteristics of pn junction. 5
- (c) What is the difference between p-type and n-type semiconductor ? 4
4. (a) What is a crystal diode ? How polarities of crystal diode are identified ? 2+3=5
- (b) Describe a half-wave rectifier using crystal diode. 5
- (c) What are filter circuits and how they are classified ? 4
5. (a) What is transistor ? Describe the working of a n-p-n and p-n-p transistor. 2+8=10
- (b) On what basis the amplifiers are classified ? 4
6. (a) What is oscillator ? Discuss the advantages of oscillators. 1+5=6
- (b) Describe the construction and operation of a C.R.T. 8

7. Write short notes on any *two* : $7 \times 2 = 14$

- (i) Push pull amplifier
- (ii) Wein bridge oscillator
- (iii) Class A, Class B, Class C and Class AB power amplifier
- (iv) Characteristics of common emitter connection.