

Total No. of printed pages = 4

Et-304/EEtE/3rd Sem/2016/N

## ELEMENTS OF ELECTRONICS ENGINEERING

Full Marks –70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks  
for the questions.

Answer question No. 1 and any *four* from the rest.

1. Fill in the blanks by inserting appropriate words / figures. 1×10=10
- (i) The most commonly used type of emission in electronic valve is ..... emission.
  - (ii) In the colour coding bands of resistor the value of tolerance in case of no colour is .....
  - (iii) In the colour coding bands of resistor the third band is known as .....
  - (iv) A vacuum diode can be used as a .....

[Turn over

- (v) The control grid is near to ..... than .....
- (vi) A full-wave rectifier is ..... efficient than a half-wave rectifier.
- (vii) R - C coupling is used for ..... amplification.
- (viii) A semiconductor has..... temperature co-efficient of resistance.
- (ix)  $\beta = \infty / \dots\dots\dots$
- (x) Negative feedback reduces ..... in amplifiers.
2. (a) What is Electron emission? What are the different types of Electron emission?  
1+4=5
- (b) How resistors are colour coded? Explain with a neat diagram. 5
- (c) A resistor has a colour code band sequence : green, blue, orange and gold. Find the range in which its value must lie depending upon the manufacturer's tolerance to suit a circuit. 5
3. (a) Give the procedure for determining the plate characteristics of a vacuum diode. What important points we can draw from these characteristics? 6

- (b) Describe the construction of a vacuum triode with a neat diagram. 5
- (c) Establish a relationship between plate resistance, transconductance and amplification factor of a triode. 4
4. (a) Discuss the properties of conductor, insulator and semiconductor. 6
- (b) What is a pn junction ? Explain the formation of potential barrier in a pn junction. 1+4=5
- (c) What do you understand by Intrinsic and Extrinsic Semiconductors ? 2+2=4
5. (a) Draw the graphical symbol of crystal diode and explain its significance. How the polarities of crystal diode are identified ? 5
- (b) Describe a half-wave rectifier using a crystal diode. 6
- (c) What are the characteristics of a zener diode ? 4
6. (a) Draw the input and output characteristics of CB configuration. What do you understand from these characteristics ? 4
- (b) Explain with a neat circuit diagram the working of a Transformer coupled transistor amplifier. 7

- (c) What do you understand by Class A, Class B amplifier. 2
- (d) Write two advantages of negative feedback. 2
7. (a) Describe the construction and working of a Hartley Oscillator. 7
- (b) What are the various controls of a CRO ? Explain it with a neat diagram. 8