

Total No. of printed pages = 3

Et-305/AE-I/3rd Sem/M/2013

ANALOG ELECTRONICS - I

Full Marks - 70

Pass Marks - 28

Time - Three hours

The figures in the margin indicate full marks for the questions.

Answer question No.1 and any *five* from the rest.

1. (a) On the basis of conductivity, classify the solids. Explain their behaviour on the basis of energy band phenomenon. 5
- (b) Explain with suitable diagram, how a p-type semiconductor is formed. 5
2. (a) Draw the V-I characteristic curve of a P-N junction diode. What is avalanche breakdown? 2+2=4
- (b) Draw the circuit diagram of half wave rectifier. Explain its working principle. Derive an expression for its efficiency. 2+3+3=8

[Turn over

3. (a) Draw the symbol for an npn transistor. Draw the CE transistor amplifier configuration using npn transistor and explain how voltage amplification is achieved. $1+5=6$
- (b) Draw the output characteristics of a transistor in CE configuration and label all the parameters. 6
4. (a) Define α and β for a transistor and establish a relation between them. 5
- (b) Write a note on DC load line. 3
- (c) Give a comparison table for CB, CE and CC transistor amplifier. 4
5. (a) What do you mean by faithful amplification? Write the basic conditions for faithful amplification in transistor. $2+3=5$
- (b) What are the various methods of biasing a transistor? Draw and explain the circuit diagram of base resistor biasing circuit. $2+5=7$
6. (a) Define gain, frequency response and band width. Name various methods of cascading multi-stage amplifier. $3+2=5$

- (b) Draw the circuit diagram of a multi-stage RC coupled amplifier. Draw its gain v/s frequency characteristic and indicate cut-off frequency and band width. $3+4=7$
7. (a) Classify amplifier on the basis of its biasing condition and explain each in short. 5
- (b) Draw a circuit diagram of push-pull amplifier. What is cross-over distortion ? Explain with diagram. $3+4=7$
8. (a) Derive a formula for negative feedback amplifier gain. 4
- (b) Classify transistor oscillator circuit. Explain Hartely oscillator with neat diagram. $2+6=8$
9. Write short notes on any *two* : $6 \times 2 = 12$
- (a) Zener diode
- (b) Vacuum tube
- (c) Regulated power supply
- (d) Filter circuit.