

Total No. of printed pages = 3

Et-305/AE-I/3rd Sem/2014/N

ANALOG ELECTRONICS – I

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

1. (a) Distinguish between conductor, insulator and semiconductor with the help of energy band diagram.
- (b) Differentiate between intrinsic and extrinsic semiconductor.
- (c) Explain how a n-type semiconductor is formed. 6+2+6=14
2. (a) Draw the V-I characteristic curve for PN junction diode. What is PIV ?
- (b) Write 3 essential conditions that must be satisfied for proper working of Zener diode.

[Turn over

- (c) Write two applications of Zener diode.
- (d) Draw a circuit diagram of voltage regulator using Zener diode. $3+3+2+6=14$
3. (a) Draw the output characteristic (V-I) of an npn transistor in CB mode for different emitter currents.
- (b) Define α and β and deduce a relationship between them.
- (c) Write down the difference between CE and CC modes in terms of input impedance, output impedance, current gain and voltage gain. $4+6+4=14$
4. (a) What is faithful amplification ?
- (b) Draw voltage divider biasing circuit for an npn transistor.
- (c) Mention two reasons for shifting operating point in DC load line.
- (d) Draw a practical single-stage CE amplifier circuit showing all components. $2+3+2+7=14$

5. (a) Draw a R-C coupled 2-stage amplifier. What are its advantage. Draw its frequency versus gain curve.

(b) Derive an expression for gain of an amplifier using negative feedback. $8+6=14$

6. What is an oscillator ? How does it differ from an amplifier ? Explain with a neat diagram the working principle of Hartley oscillator.

$2+2+10=14$

7. Write short notes on any *two* : $2 \times 7 = 14$

(a) Bridge rectifier

(b) Push pull amplifier

(c) Filters

(d) LED

(e) Triode.