

Total number of printed pages—11

53 (IE 301) NWTH

2014

NETWORK THEORY

Paper : IE 301

Full Marks : 100


Pass Marks : 30

Time : Three hours

The figures in the margin indicate full marks for the questions.


Answer any five questions.

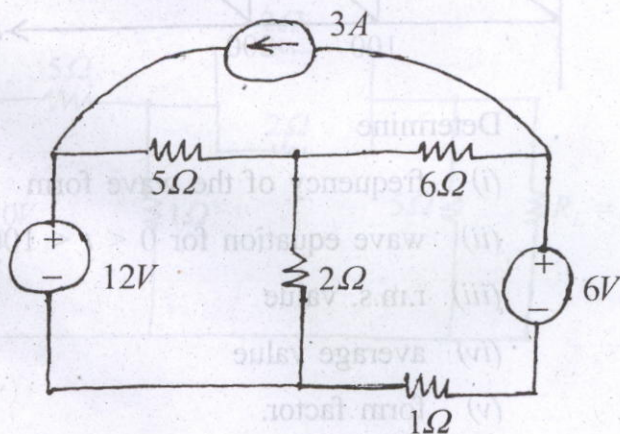1. (a) Determine the currents through the resistors using mesh method for the network shown below — 10




Contd.

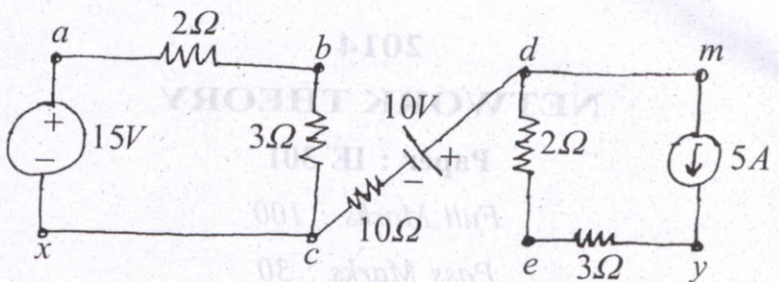- (b) Find voltage drop between terminals a and e for the following network. 5



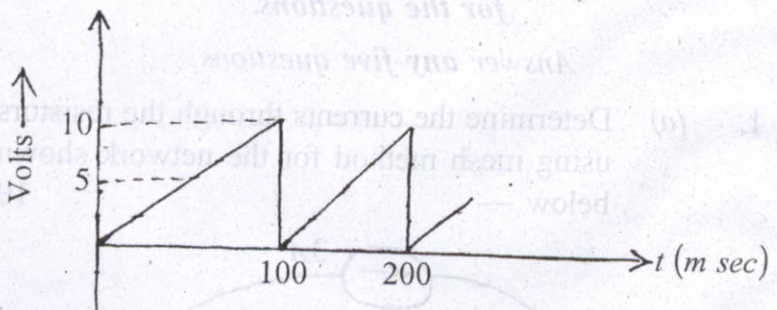- (c) A periodic voltage waveform has been shown below — 5




Determine

- (i) frequency of the wave form
- (ii) wave equation for $0 < t < 100m \text{ sec}$
- (iii) r.m.s. value
- (iv) average value
- (v) form factor.


2. (a) Find the resistance at the $A-B$ terminals in the electric circuit using delta-star transformation. All resistances are in ohm .

6

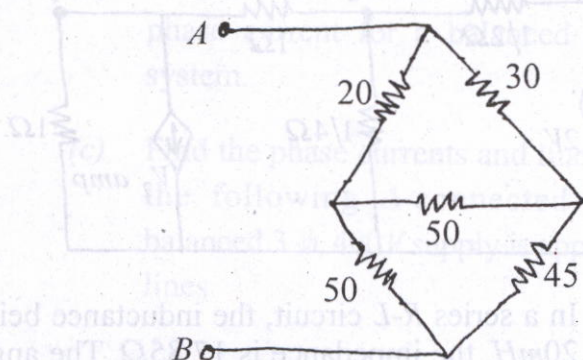


- (b) In the circuit shown below, find I and voltage drop across R_L .

7

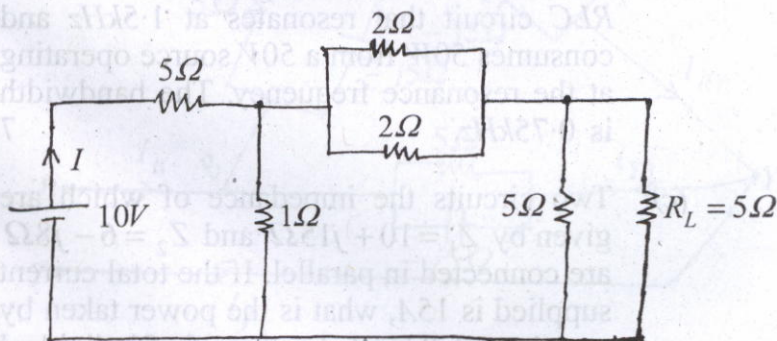


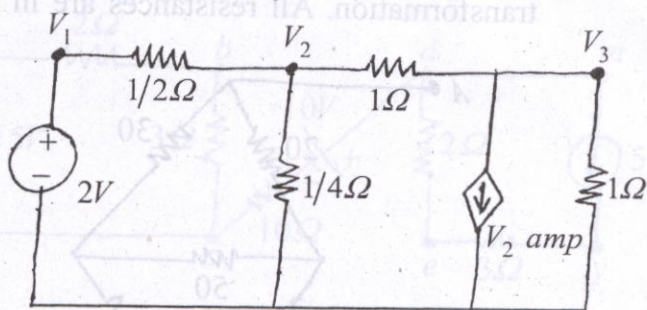- (c) In the network given below, find V_1 , V_2 and V_3 by nodal analysis. 7.



3. (a) In a series R - L circuit, the inductance being 20mH , the impedance is 17.85Ω . The angle of lag of the input current from the applied voltage being 63.5° , find the values of angular frequency and the resistance of the circuit. 6
- (b) Obtain the values of R , L and C in a series RLC circuit that resonates at 1.5kHz and consumes 50W from a 50V source operating at the resonance frequency. The bandwidth is 0.75kHz . 7
- (c) Two circuits the impedance of which are given by $Z_1 = 10 + j15\Omega$ and $Z_2 = 6 - j8\Omega$ are connected in parallel. If the total current supplied is 15A , what is the power taken by each branch? Find also the $p.f.$ of individual circuits and of the combination. Also draw the vector diagram. 7

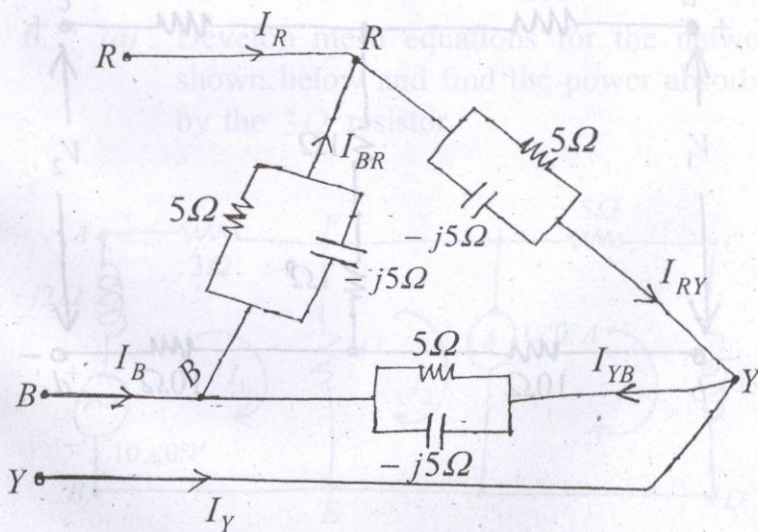4. (a) Write *three* advantages of 3- ϕ system over 1- ϕ system. 3
- (b) Derive a relation between line current and phase current for a balanced Δ -connected system. 5
- (c) Find the phase currents and line currents for the following Δ -connected loads, if a balanced 3- ϕ , 400V supply is applied between lines 12




5. (a) Define the following :

(i) Unilateral and bilateral circuits


(ii) Linear and non-linear elements.

2+2=4

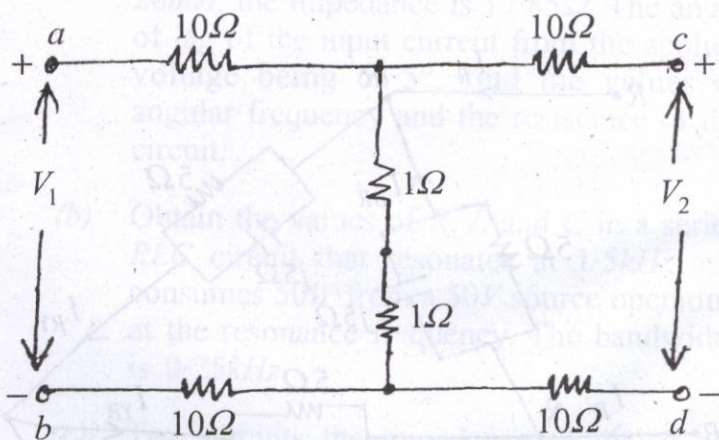
(b) Determine the Z-Parameters for the following network — 9



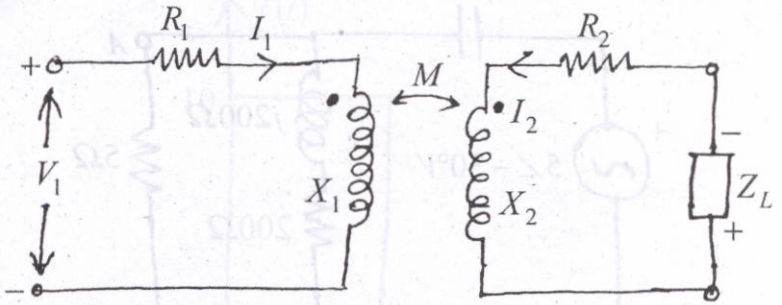- (c) For an ideal transformer, shown below, find the input impedance. Assume load impedance to be Z_L 7




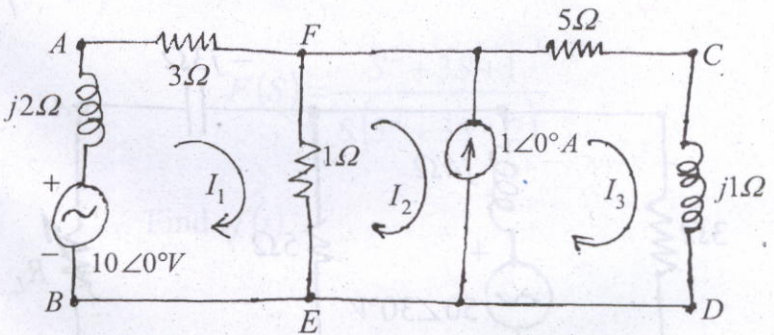6. (a) Develop mesh equations for the network shown below and find the power absorbed by the 3Ω resistor 7




- (b) In the network given below, calculate current in the 5Ω resistor using Thevenin's theorem

6

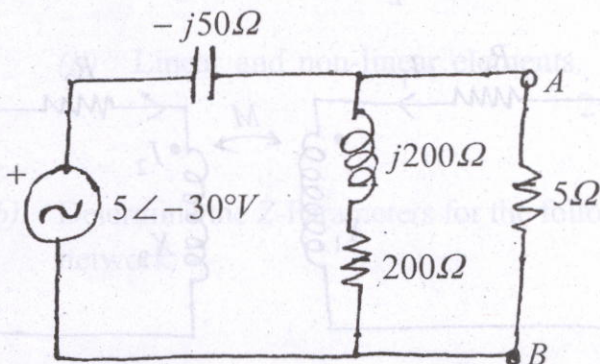


- (c) What should be the value of R_L so that maximum power can be transferred from the source to load in the circuit given below?

7

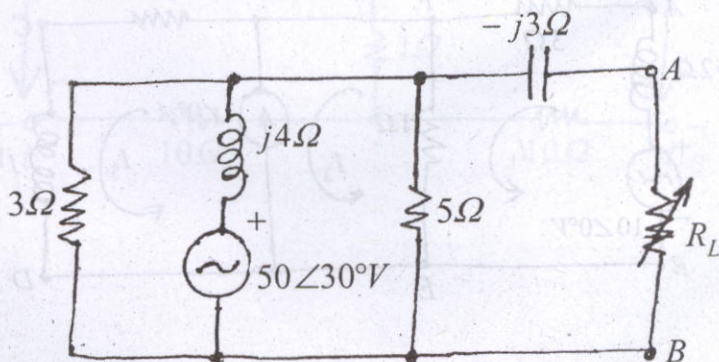

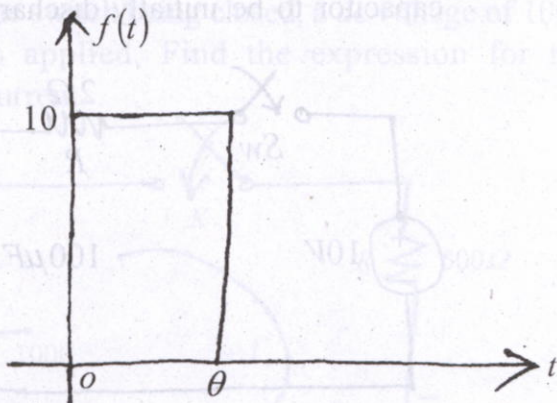7. (a) A pulse waveform is shown below. Obtain its Laplace transform 5




- (b) Function in S -domain is given by — 5


$$F(S) = \frac{S^2 + 3S + 1}{S(S^2 + 3S + 2)}$$

Find $f(t)$.

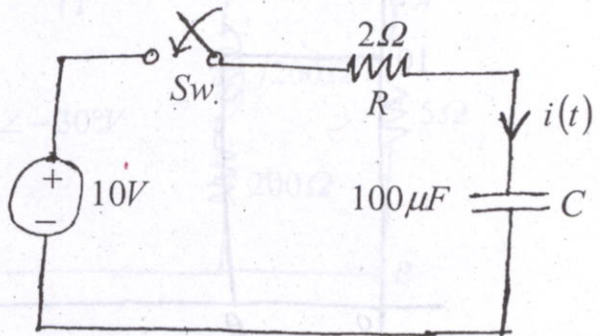
- (c) For the circuit shown below, obtain the current through the capacitor C at $t=0+$ following switching at $t=0$. Assume the capacitor to be initially discharged 10



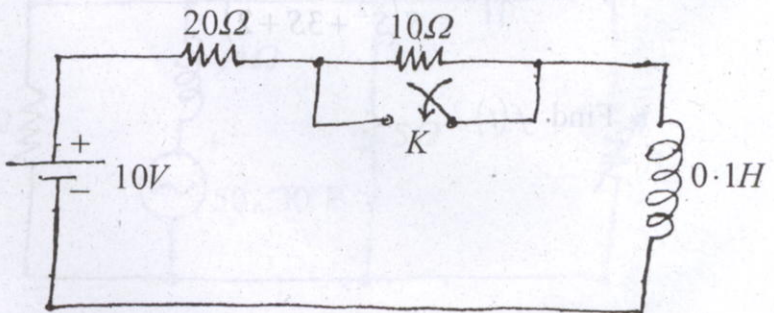8. (a) A dc voltage of $100V$ is applied in the following circuit and the switch K is open. The switch K is closed at $t=0$. Find the complete expression for the current 8



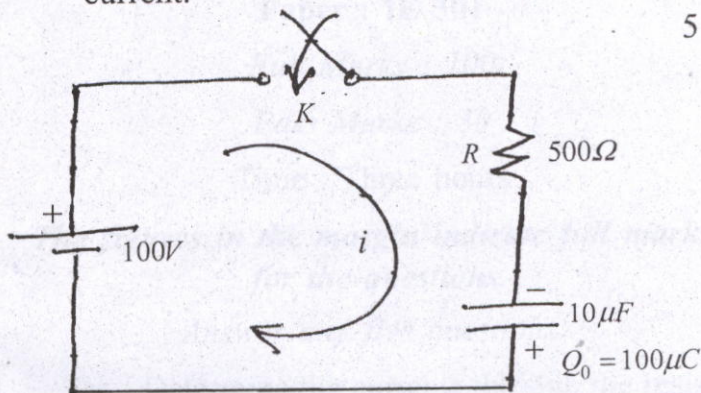- (b) The $10\mu F$ capacitor in RC circuit shown below has initial charge of $100\mu C$ with polarities as shown in the fig. below At $t = 0$, the switch being closed, a dc voltage of $100V$ is applied. Find the expression for the current.



- (c) What do you mean by lagging and leading power factor? Draw a phasor diagram of RLC series circuit with sinusoidal excitation. If this circuit is in resonance, what will be the impedance and power factor of the circuit?
- 1+1+3+2=7