

Total number of printed pages-9

53 (IE 301) NWTH

2017

NETWORK THEORY

Paper : IE 301


Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.


Answer **any five** questions.

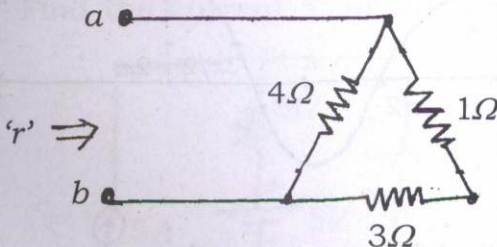1. (a) Find the resistance 'r' across a-b in the following figure: 2




Contd.

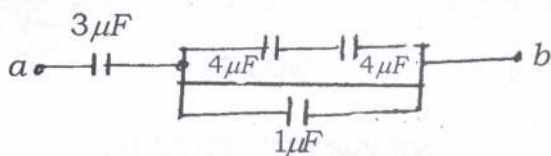
- (b) Find the equivalent capacitance of the combination below across $a-b$: 2



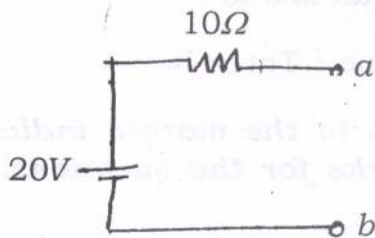- (c) Convert the following into current source: 4



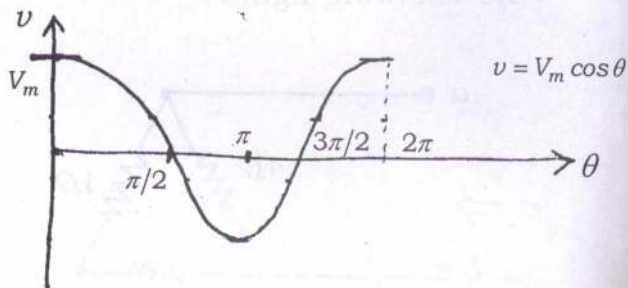- (d) A voltage waveform is shown below: 4




Find its average value.


(e) In an a.c. circuit containing pure inductance, the voltage applied is 220V, 50Hz ; while the current is 10A. Find the value of inductive reactance (X_L) and inductance (L). 5

(f) The voltage and current through an a.c. circuit are given by $v = v_m \sin \omega t$ and $i = I_m \cos \omega t$. What is the phase difference between these two variables? 3

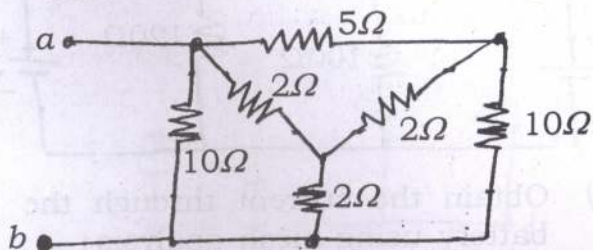
2. (a) Find the equivalent resistance between terminals $a-b$ in the following: 7



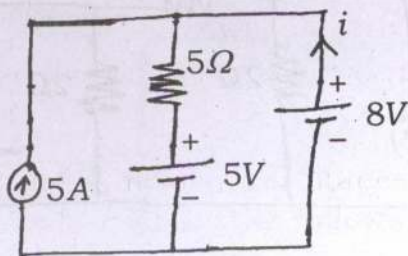
(b) Find the current 'i' in the figure: 6



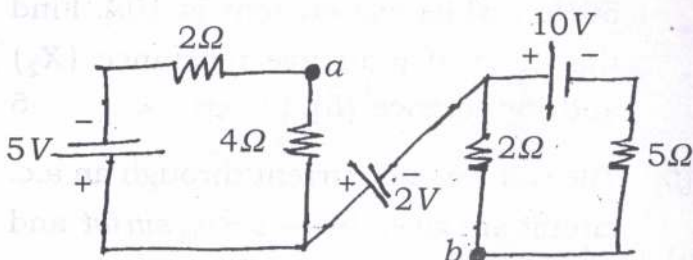
- (c) Find the voltage drop across the terminals $a-b$: 7



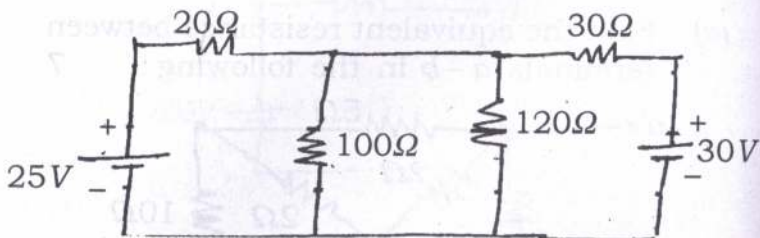
3. (a) Using Nodal analysis find the current through 100Ω resistance: 7



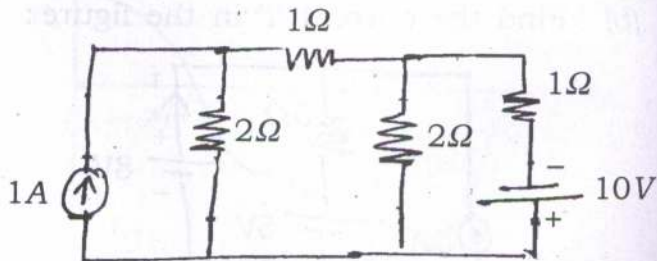
- (b) Obtain the current through the $10V$ battery using mesh analysis: 7



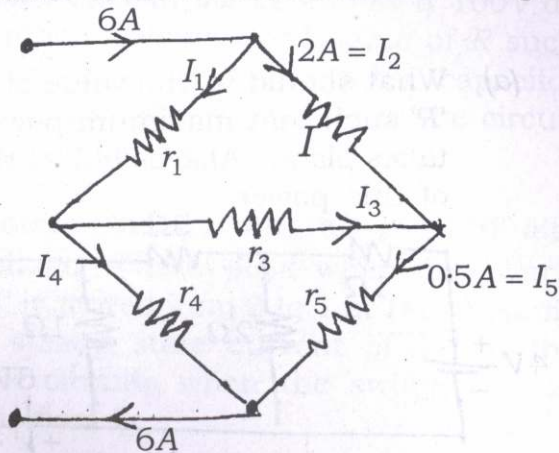
- (c) Using KCL, obtain the values of unknown currents in the following: 6



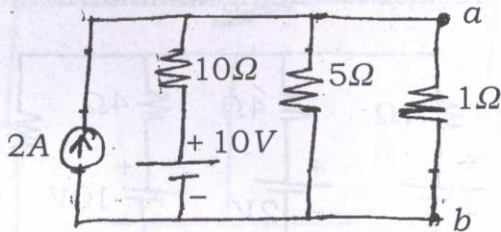4. (a) Find the power loss in the 1Ω resistance by Thevenin's theorem: 7




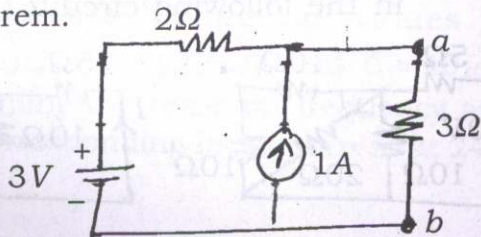- (b) Prove that the current flowing through 3Ω resistance is $1A$; using Norton's theorem. 7




(c) State and prove the Superposition Theorem as applicable to d.c. circuits. 6


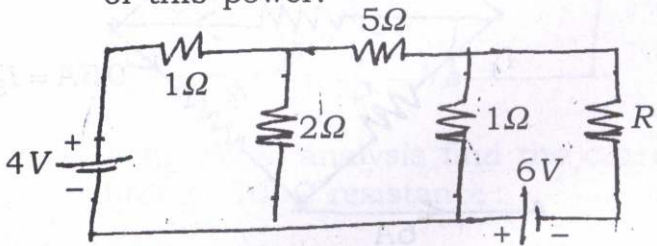
5. (a) What should be the value of resistance 'R' such that maximum power transfer takes place? Also calculate the amount of this power. 8



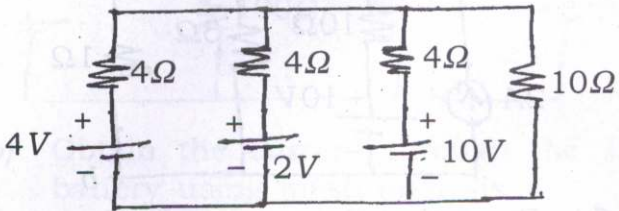(b) Find the current through 10Ω resistance using Millman's theorem. 6




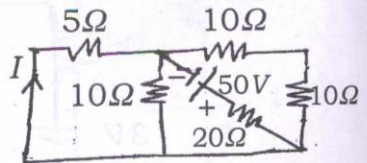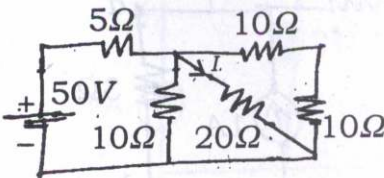(c) Show the validity of Reciprocity theorem in the following circuits: 6



6. (a) A resistance ' R ' and $5\mu F$ capacitor are connected in series across a $100V$ dc supply. Calculate the value of R such that the voltage across the capacitor becomes $50V$ in 5 sec after the circuit is switched on. 7

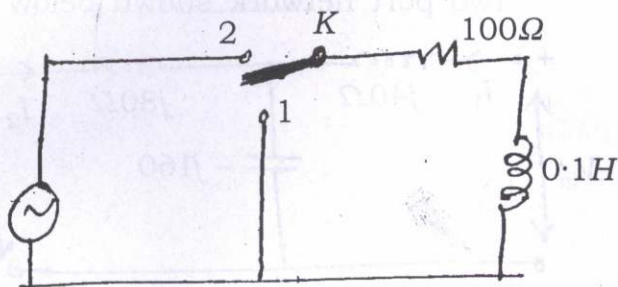(b) Obtain the current at $t > 0$; if a.c. voltage ' v ' is applied when the switch ' K ' is moved from 2 to 1 at $t=0$. Assume a steady state current of $1A$ in the L-R circuits when the switch was at position 1. 8



(c) A R - L - C tank circuit is composed of components having the values as $R = 0.3\Omega$; $L = 120mH$ and $C = 40\mu F$. Determine the resonant frequency and the corresponding input current at $24V$. 5


7. (a) Find the current in a series R - L circuit having $R=2\Omega$ and $L=10H$, while a dc voltage of $100V$ is applied. What is the value of this current after 5sec of switching on? 5

(b) A function in s -domain is given by — 5


$$F(s) = \frac{50}{s^2 + 2s + 2}$$

Find the inverse Laplace transform.

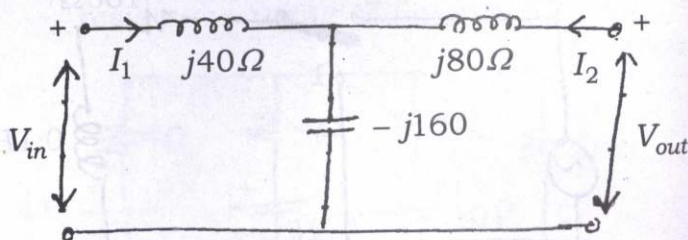(c) Find the open circuit parameter of the two port network shown below: 5



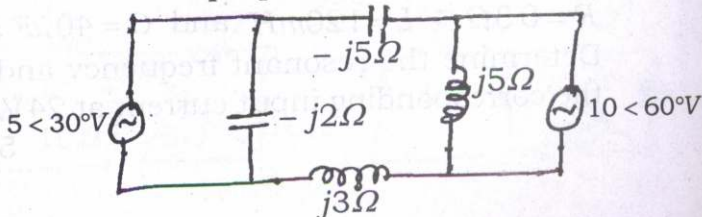(d) Obtain the current through $j3\Omega$ inductive reactance using the principle of superposition. 5



8. Write short notes on : **(any four)** $5 \times 4 = 20$

- (i) Initial and final value theorem
 - (ii) Q-factor
 - (iii) Reciprocity theorem
 - (iv) Poles and zeroes in network function
 - (v) Y-parameters.
-