

Total number of printed pages-7

53 (IE 301) NWTB

2018

NETWORK THEORY

Paper : IE 301

Full Marks : 100

Time : Three hours


The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

1. (a) What are the active elements and passive elements? A 4.0Ω resistor has a current $i = 2.5 \sin \omega t$. Find the voltage, power and energy over one cycle. $\omega = 500 \text{ rad/s}$. 2+6=8

Contd.


(b)

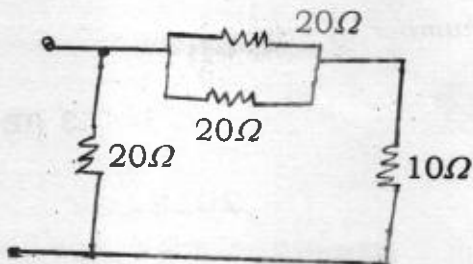

Find the equivalent resistance of the circuit. 5

(c) How a voltage source can be converted into current source and current source can be converted into voltage source? 7

2. (a)

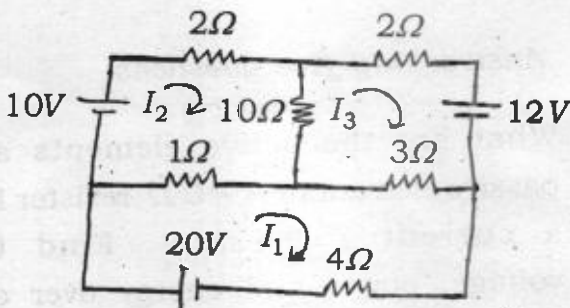

Find the current through 1Ω resistor. 10

(b) Obtain the response of an RL circuit to the following inputs.


(i) Unit impulse

(ii) Unit step

(iii) Unit ramp

3+3+4=10

3. (a)

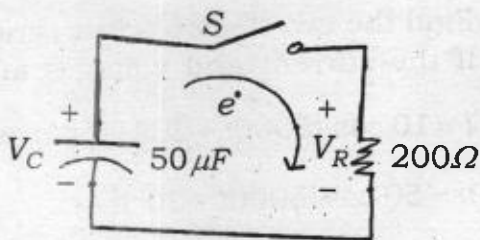

At $t = 0_-$, just before the switch S is turned on, $V_C = 50V$. Obtain the current and charge transients. 5

(b) A series RLC circuit with $R = 100\Omega$, $L = 0.1H$, $C = 10\mu F$, has an initial charge on the capacitor of $Q_0 = 2.67 \times 10^{-3}C$. A switch is closed at $t = 0$, allowing the capacitor to discharge. Obtain the current transient.

10

(c) Define the terms — driving point impedance and transfer impedance.

5

4. (a) If $V_1 = 25.0 \angle 143.13^\circ$ and $V_2 = 11.2 \angle 26.57^\circ$, find the ratio V_1/V_2 and the sum $V_1 + V_2$.

5

(b) Find the two elements in a series circuit if the current and voltages are

$$i = 10 \cos(5000t - 23.13^\circ) \text{ (A) and}$$

$$v = 50 \cos(5000t + 30^\circ) \text{ (A)}$$

5


(c) Find P delivered from a sinusoidal voltage source with $v_{eff} = 110 \text{ V}$ to an impedance of $z = 10 + j8$. Find the power factor.

5

(d) A certain passive network has equivalent impedance $z = 3 + j4R$ and $v = 42 \cos(2000t + 20^\circ)$. Find P and Q.

5


5. (a)

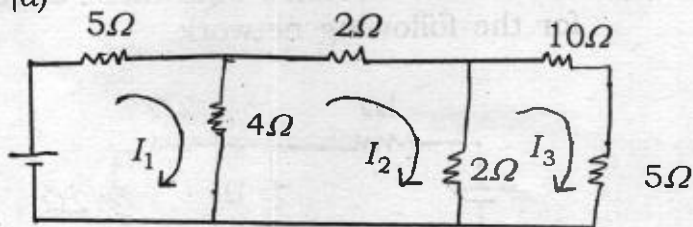

Obtain the current I_1 , I_2 , I_3 using mesh analysis.

7


(b)

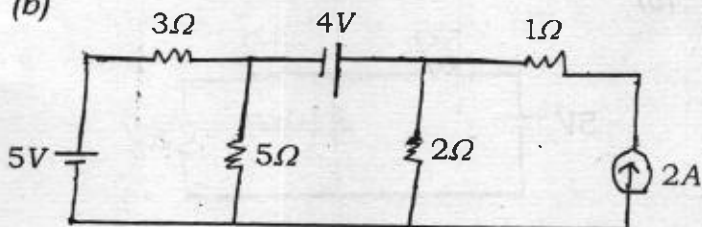

Find the current through the 1Ω resistor using superposition theorem.

7


(c)

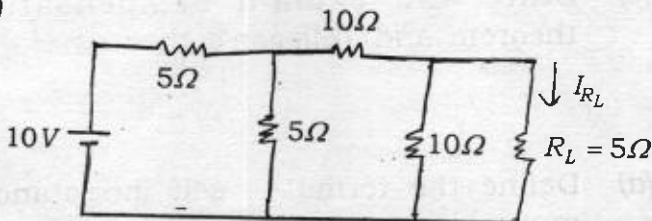


Using Thévenin's theorem obtain the current I_{RL} .

6

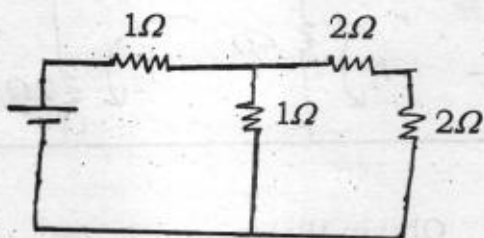6. (a) Obtain the Norton's equivalent circuit for the following network. 5



(b)

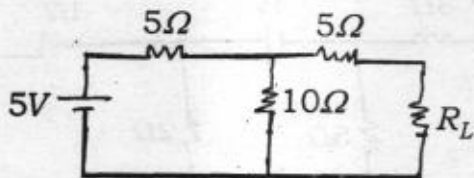

Obtain value of R_L for maximum power transfer. 5

- (c) State and explain compensation theorem and Tellegen's theorem. 10

7. (a) Define the terms — self inductance, mutual inductance, coupling coefficient. 6

- (b) When one coil of a magnetically coupled pair has a current 5.0 A , the resulting fluxes ϕ_{11} and ϕ_{12} are 0.2 mWb and 0.4 mWb respectively. If the turns are $N_1 = 500$ and $N_2 = 1500$, find L_1 , L_2 , M and the coefficient of coupling. 8
- (c) What are the advantages of three phase system over single phase system. 6
-

(a) When the coil is magnetically coupled
the bar has a current of 5.0 A, the resulting
fluxes of the two coils are 3.2 mWb and
0.4 mWb respectively. If the turns are
100 and 200 respectively, find the
self and mutual inductance of the coils.

(b) What are the advantages of three phase
system over single phase system.