

Total number of printed pages-5

53 (IE 301) NWTH

2019

NETWORK THEORY

Paper : IE 301

Full Marks : 100

Time : Three hours



The figures in the margin indicate full marks for the questions.

1. (a) How a voltage source can be converted into current source and vice versa? Explain. 6
- (b) What are active elements and passive elements? 4
- (c)

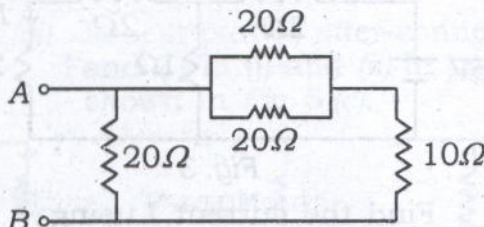


Fig. 1

Find the equivalent resistance of the circuit. 6

Contd.

(d) State Kirchoff's current and voltage law. 4

2. Obtain the response of an RL and an RC circuit to the following inputs: 20

- (i) Unit impulse
- (ii) Unit step
- (iii) Unit ramp.

3. (a) State and prove final value theorem and initial value theorem. 6

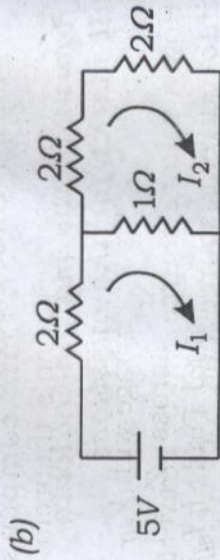


Fig. 2

Find the currents I_1 and I_2 . 4

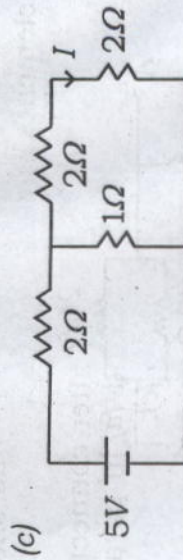


Fig. 3

Find the current I using — 5+5=10

- (i) Thevenin's theorem
- (ii) Norton's theorem.

4. (a) Determine the condition under which the input impedance of the network shown in Fig. 4 will be equal to R . 5

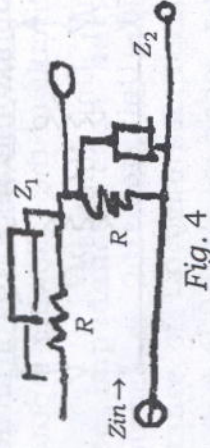


Fig. 4

(b) State Reciprocity and Millman's theorem. 10

(c) State and explain compensation theorem and Telegen's theorem. 10

5. (a) (i) A sinusoidal voltage with $V_{eff} = 10V$ is connected across $Z_1 = 1 + j$ as shown in Fig. 5 (a). Find: i , I_{eff} , $P(t)$, P_1 , Q_1 , power factor pf and S .

(ii) Repeat part (i) replacing the load Z_1 in (i) by $Z_2 = 1 - j$ as shown in Fig. 5 (b).

(iii) Repeat part (i) after connecting Z_1 and Z_2 in (i) and (ii) in parallel as shown in Fig. 5 (c). 10

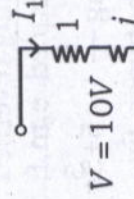


Fig. 5 (a)

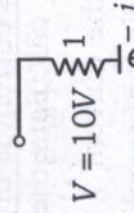


Fig. 5 (b)



Fig. 5 (c)

(b) Find the Z parameters of the network shown in Fig. 6. 5

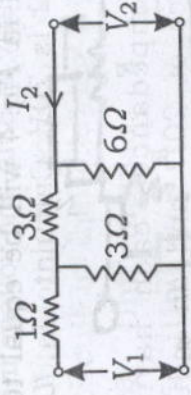


Fig. 6

(c) Using Maximum power transfer theorem find the maximum power transferred to the load in the following network — 5

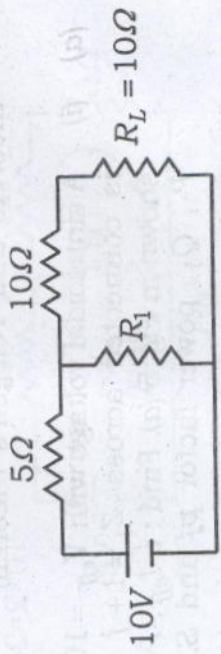


Fig. 7

6. (a) If a coil of 150 turns is linked with a flux of 0.01 Wb when carrying current of 10A, calculate the inductance of the coil. If this current is uniformly reversed in 0.01 s, calculate the induced e.m.f. 5

(b) The coefficient of coupling between two coils is 0.75. There are 250 turns in coil 1. The total flux linking coil 1 is

0.4 mWb, when the current in this coil is 3A. When i_1 is changed from 3A to zero linearly in 3ms, the voltage induced in coil 2 is 70V. Calculate L_1 , L_2 , M , N_2 . 7

(c) Three impedances each having a resistance of 20Ω and an inductive reactance of 15Ω are star connected across a 400V, three phase supply. Calculate (i) line current, (ii) power factor, (iii) total power in kW. 8

7. Write short notes on : $10 \times 2 = 20$

- (a) Inductive coupling in series
- (b) Three phase system.

