

Total number of printed pages-7

53 (IE 301) NWTB

2021

**NETWORK THEORY**

Paper : IE 301

Full Marks : 100

Time : Three hours

**The figures in the margin indicate full marks for the questions.**


Answer any five questions.

1. (a) Define the following terms : 5
- (i) Mesh
  - (ii) Node
  - (iii) Ideal voltage source
  - (iv) Passive Network
  - (v) Lumped Network.
- (b) Differentiate between : 2+2=4
- (i) Time invariant and time variant sources


Contd.

- (ii) Unilateral and bilateral networks.
- (c) Explain with a suitable example how to obtain — 4+4=8
- (i) an equivalent current source from a given voltage source
- (ii) loop analysis of analysing a given network.

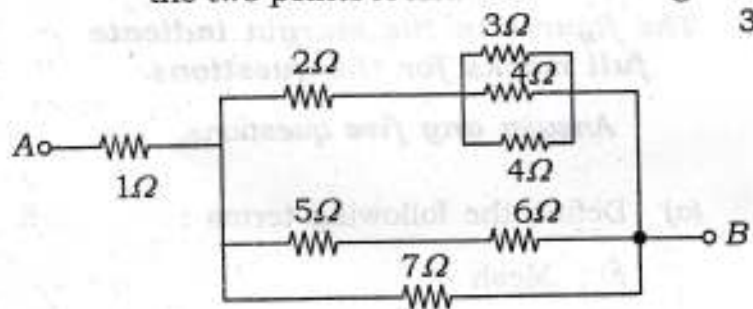
(d) Find the equivalent resistance between the two points A and B shown in figure :



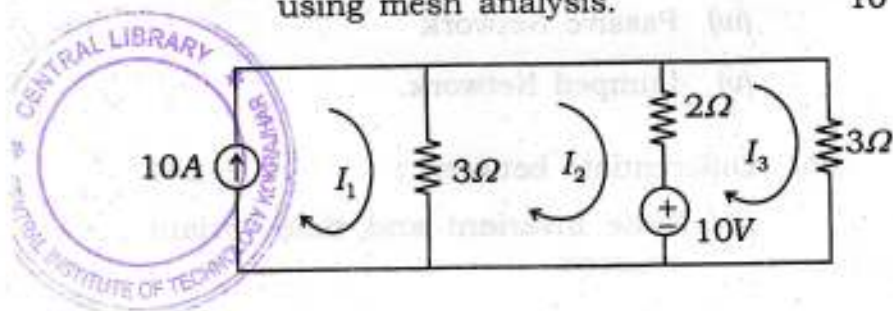
2. (a) Write the mesh equation for the circuit shown and determine mesh currents using mesh analysis. 10



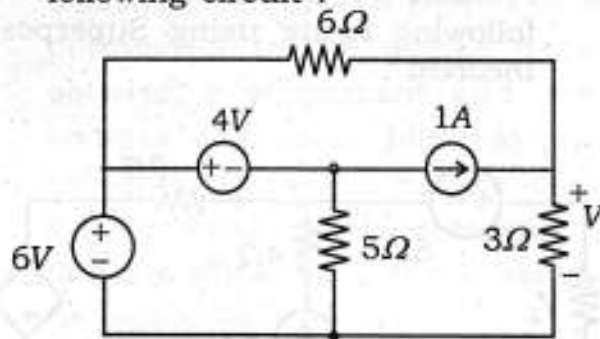- (b) Find the value of voltage  $V$  in the following circuit : 6



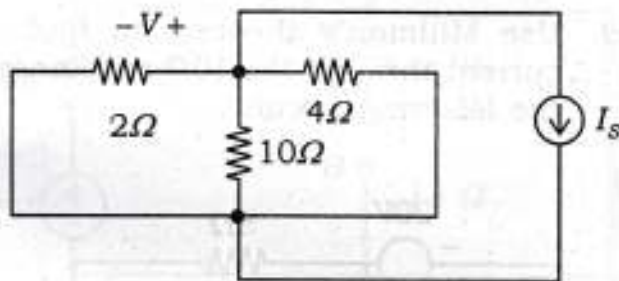- (c) In the following circuit if  $V = 10V$ , then find value of  $I_s$  4




3. (a) State and explain the following theorem : 5+5=10


- (i) Superposition theorem  
(ii) Millman's theorem.



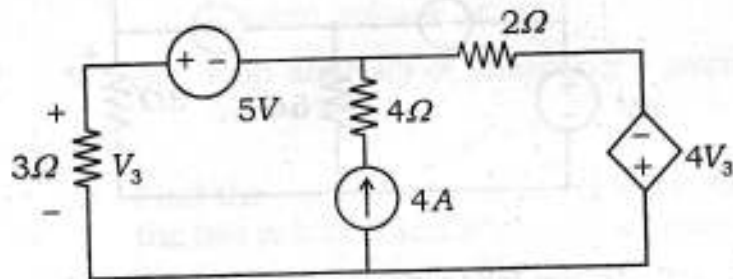- (b) Determine the current through  $2\Omega$  resistor of the network shown in following figure using Superposition theorem : 7



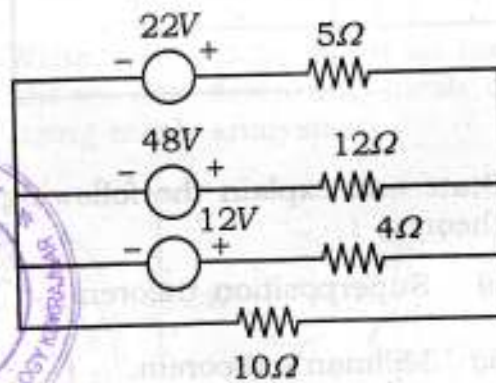- (c) Use Millman's theorem to find the current through the  $10\Omega$  resistance in the following circuit : 3




4. (a) State and prove the maximum power transfer theorem for a passive network connected to an active network consisting of current and voltage sources and linear bilateral passive elements, when the passive network load consists a variable resistance. Also find the efficiency of transmission.

10

- (b) Replace the network at terminals AB with Norton's and Thevenin's equivalent circuit.

10

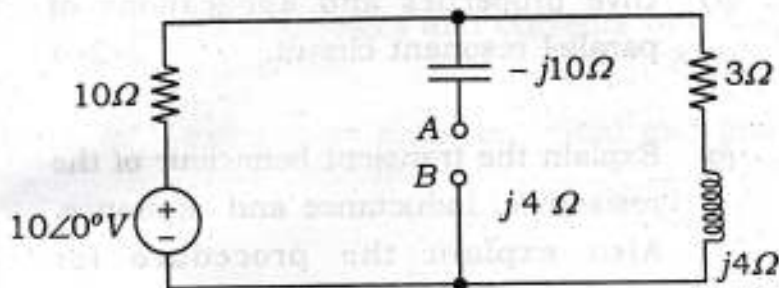

5. (a) Define quality factor and bandwidth. Also establish the relationship between them in a series resonance circuit.

10



(b) A series RLC circuit consists of a resistance  $1k\Omega$  and an inductance of  $120mH$  is series with capacitance of  $12pF$ . If  $120V$  is applied as input across the combination, determine : 6

(i) The resonant frequency

(ii) Maximum current in the circuit


(iii)  $Q$ -factor

(iv) Half frequencies.


(c) Give properties and applications of parallel resonant circuit. 2+2=4

6. (a) Explain the transient behaviour of the resistance, inductance and capacitance. Also explain the procedure for evaluating transient behaviour. 10

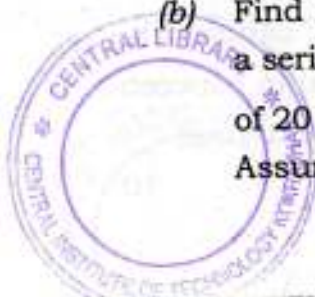(b) Find the expression for the current in a series RLC circuit fed by a d.c. voltage of  $20V$  with  $R=4\Omega$ ,  $L=1H$  and  $C=\frac{1}{4}F$ . Assume initial conditions to be zero. 10



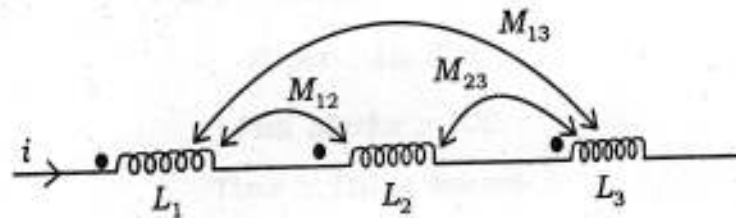7. (a) Find the total inductance of the three series connected coupled coils in the given figure if  $L_1 = 1H$ ,  $L_2 = 2H$ ,  $L_3 = 5H$ ;  $M_{12} = 0.5H$ ,  $M_{23} = 1H$  and  $M_{13} = 1H$ . 6



- (b) Give advantages of three phase system. Derive relationship between line and phase voltages and currents in a star connection. 3+7=10
- (c) Write short notes on initial and final value theorem. 4

