

Total number of printed pages-5

53 (IE 402) ELMI

2014

ELECTRICAL MEASUREMENT & INSTRUMENTS

Paper : IE 402

Full Marks : 100

Time : Three hours

*The figures in the margin indicate full marks
for the questions.*

Answer any five questions out of seven.

1. (a) Describe the constructional details and principle of operation of d'Arsonval galvanometer. 5

(b) Compare merits and demerits of moving coil and moving iron instruments. 5

Contd.

- (c) A moving coil milli-voltmeter has a resistance of 200Ω and full-scale deflection is reached when a potential difference of $100mV$ is applied across its terminals. The moving coil has effective dimensions of $30 \times 25mm^2$ and is wound with 100 turns. The flux density in the gap is $0.2 wb/m^2$. Determine the control constant of the spring if the final deflection is 100° and suitable diameter of copper wire for the coil winding of 20% of total instrument resistance is due to coil winding. Resistivity of copper is $1.7 \times 10^{-8} \Omega\text{-m}$.

10

2. (a) A basic d'Arsonval movement galvanometer with a full scale reading of $5\mu A$, and internal resistance of 1800Ω is available. It is to be converted into a $0-1V$, $0-5V$, $0-25V$, $0-125V$, multi-range voltmeter using individual multipliers for each range. Calculate the value of the individual multiplier. 5
- (b) Give the basic principle of working of an electrostatic voltmeter. Explain how the voltage range of the voltmeter can be increased. 5+5

- (c) The inductance of a moving iron ammeter is given by $L = (0.01 + C\theta)^2 \text{ mH}$ where θ is the deflection from the zero position in degree. The angular deflection of the instrument corresponding to $1.5A$ and $2A$ are respectively 90° and 120° . Find the value of C . 5
3. (a) Explain the procedure of measuring a low resistance with the help of Kelvin's double bridge. Derive the relation for unknown resistance. 10
- (b) What is the principle of using loss of charge technique for measurement of high resistance? Derive necessary relation.
- A length of cable was tested for insulation resistance using this method. A capacitance formed by sheath of cable of $300 \mu\text{F}$ is found to have drop in voltage from $300V$ to $100V$ in 120 seconds . Calculate the insulation resistance of the cable. 6+4
4. (a) Which bridge is used for measurement of frequency? Explain the bridge with circuit diagram. 1+4

(b) An *a.c.* schering bridge has the following constants —

Arm *ab* → Unknown capacitor C_x and R_x in series

Arm *bc* → Resistance of $2k\Omega$

Arm *cd* → capacitor of $0.5\mu F$ in parallel with $1k\Omega$ resistor.

Arm *da* → Capacitor of $0.5\mu F$

Frequency → $1kHz$.

Determine the unknown capacitance and dissipation factor. 5

(c) Describe and explain with the help of neat sketches the construction and working of megger. 10

5. (a) Describe the constructional details and working of a single phase electrodynamicmeter type of wattmeter. Derive the expression for deflection for *a.c.* operation if the instrument is spring controlled. 10

(b) If the reactance coil circuit of a wattmeter is 1 per cent of its resistance, calculate the error due to this cause at power factors 0.8 and 0.1 respectively. 6

- (c) What are the errors in energy meter and how they are compensated ? 4
6. (a) Describe the basic principle of operation of a *d.c.* potentiometer. Explain why a potentiometer does not load the voltage source whose voltage is being measured. 4+2
- (b) Draw the equivalent circuit and phasor diagram of a current transformer. Also derive the transformation ratio and phase angle. 10
- (c) Differentiate between CT and PT. 4
7. Write short notes on the following : (*any four*) 4×5
- (a) Vibration Galvanometer
- (b) Earth resistance measurement
- (c) Shunt type ohmmeter
- (d) Rectifier type instrument
- (e) Ammeter-voltmeter method
- (f) Maxwell inductance bridge.
-