

Total number of printed pages-6

53 (IE-402) ELMI

2017

**ELECTRICAL MEASUREMENTS  
AND INSTRUMENTS**

Paper : IE-402

Full Marks : 100

Time : Three hours

**The figures in the margin indicate  
full marks for the questions.**

Answer **any five** questions.

1. (a) Describe the construction and working of a ballistic galvanometer.

Explain in brief the basic principle of operation of a d'Arsonval galvanometer.

8

- (b) Describe the construction of attraction and repulsion type moving Iron instruments.

6

Contd.

- (c) Explain the principle of working of thermocouple instruments with a suitable diagram. 6
2. (a) Show that in a Electro-dynamometer type instrument, the deflection  $\theta$  under a.c. operation is given by the relation :

$$\theta = \frac{I_1 I_2}{K} \cos \phi \frac{dM}{d\theta} \quad 8$$

- (b) Describe the working of a Quadrant Electrometer or Quadrant type Electrostatic instruments. Discuss the conditions of its operation. 6
- (c) Describe the constructional features of potential Transformer and draw the equivalent circuit diagram and the phasor diagram. 6
3. (a) Describe the theory of Electro-dynamometer Wattmeter with mathematical expressions. 7
- (b) Derive that the total deflecting torque  $T_d$  in an Induction type meter is given by the relation : 7

$$T_d = K \phi_1 \phi_2 \frac{f}{Z} \sin \beta \cos \alpha$$

- (c) Explain the constructional features of Single Phase Induction type Energy Meters. Also draw the phasor diagram.

6

4. (a) Sketch the circuit diagram of a basic D.C. Potentiometer. Discuss the calibration procedures for the Potentiometers and explain how it may be used for precise measurement of D.C. voltages.

6

- (b) Explain the Direct Deflection Method for the measurement of insulation resistance of cables.

6

- (c) Derive the expression for bridge sensitivity for a Wheatstone bridge with equal arms.

8

In a Wheatstone bridge, the values of resistances of various arms are

$$P = 500\Omega, Q = 200\Omega, R = 720\Omega \text{ and}$$

$$S = 330\Omega. \text{ The battery has an } emf \text{ of}$$

5V. The galvanometer has a current sensitivity of  $5\text{mm}/\mu\text{A}$  and an internal resistance  $10\Omega$ . Calculate the deflection of galvanometer.

5. (a) Explain how a D.C. Potentiometer can be used for following applications ?

8




- (i) Calibration of ammeter
- (ii) Measurement of resistance
- (iii) Calibration of wattmeter.

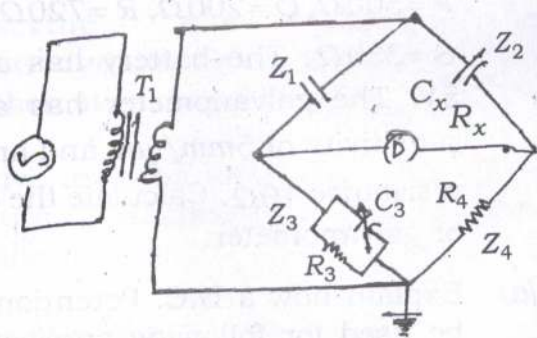(b) A high-voltage capacitor is investigated using a Schering bridge as shown in the figure below. The bridge components at balance are following :

$$C_1 = 0.3 \mu F, C_3 = 1000 pF, R_3 = 2k\Omega \text{ and } R_y = 5k\Omega.$$

The supply is 1000V with a 300 Hz frequency. Calculate the measured capacitance ( $C_x$ ) and its dissipation factor, and determine the approximate magnitudes of the voltage drop across  $z_2$  and  $z_4$ .



(c) Describe in brief the construction and working of Earth Tester. 6

6. (a) Draw the circuit diagram of a Maxwell bridge. Explain the bridge operation, and derive the equations for the inductor under investigation.

A Maxwell bridge uses a standard Capacitor of  $C_3 = 0.3 \mu F$  and operates at a supply frequency of  $200 Hz$ . Balance is achieved when  $R_1 = 1.5 k\Omega$ ,  $R_3 = 550 \Omega$  and  $R_y = 300 \Omega$ . Calculate the inductance and resistance of measured inductor, and determine its  $Q$  factor. 8

(b) Discuss a method for the measurement of Mutual inductance. 7

(c) A Wien bridge circuit has the following components  $C_1 = 0.2 \mu F$ ,  $C_2 = 0.4 \mu F$ ,  $R_1 = R_2 = 820 \Omega$ ,  $R_3 = 1.5 k\Omega$ . Calculate the bridge balance frequency, and the required resistance for  $R_4$  to achieve balance. 5

7. (a) Write short notes on : **(any three)**

6×3=18

- (i) Gall Tinsley (Coordinate) type Potentiometer.
- (ii) Kelvin Double Bridge
- (iii) Localization of cable faults
- (iv) Anderson Bridge.

(b) List the following for PMMC, M-I and Electro-dynamometer type instruments

2

- (i) Type of operation
- (ii) Operating range