

Total number of printed pages-5

53 (IE 402) EMIN

2018

ELECTRICAL MEASUREMENTS AND INSTRUMENTS

Paper : IE 402

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. (a) Derive the torque equation of a moving iron instrument. 7
- (b) Describe the constructional features and working of attraction and repulsion type moving iron instrument. 8
- (c) Show that in an electrostatic instrument, the deflection θ is given by the relation 5

$$\theta = \frac{1}{2} \frac{V^2}{K} \frac{dL}{d\theta}$$

Contd.

2. (a) Why is damping required for an electromechanical measuring instrument ? Describe Eddy current damping with a suitable diagram. 6

(b) Explain the different effects used in producing deflecting torque in an analog instrument. 8

(c) The following data refers to a moving coil galvanometer whose resistance is 320Ω and a resistance of 1250Ω is connected in series with it.

Number of turns = 200,

flux density = 0.1 Wb/m^2 ,

control constant = $0.15 \times 10^{-6} \text{ Nm/rad}$,

dimension of the coil = $40 \times 50 \text{ mm}$,

moment of inertia of coil = $0.3 \times 10^{-6} \text{ kgm}^2$.

Calculate :

(a) The resistance to be connected to galvanometer for critical damping

(b) Relative Damping.

6

3. (a) Write the advantages and disadvantages of PMMC instrument. 5

(b) Describe the construction and working of hot wire instruments. 5

- (c) Derive the relation for Inductance and Quality factor for Maxwell Bridge.

Given that

ARM AB = R_1 and series inductor L_1

BC = R_2 ,

CD = R_4 parallel to capacitor C_4 ,

DA = R_3

Detector is connected between BD and supply is connected to AC at balance condition. 5

- (d) Write down the errors in A.C. bridge methods and their compensation techniques. 5

4. (a) Describe the construction of Electrodynamic Wattmeter. Show that the deflection θ in Electrodynamic Wattmeter is given by the relation : 10

$$\theta = \left(K_1 \frac{dM}{d\theta} \right) P$$

- (b) Derive the equation for deflecting torque in an Induction Type Energymeter. 7

- (c) Discuss in brief the errors in Energymeter. 3

5. (a) Differentiate between C.T. and P.T. Draw the equivalent circuit diagram and phasor diagram for C.T. 6
- (b) Explain the term "standardization" of a Potentiometer. Describe the procedure of standardization of a D.C. Potentiometer. Also, discuss some of the applications of D.C. Potentiometer. 10
- (c) A Maxwell Inductance Bridge uses a standard capacitor of $C_3 = 0.1 \mu F$ and operates at a supply frequency of $100 H_2$. Balance is achieved when $R_1 = 1.26 K\Omega$, $R_3 = 470 \Omega$ and $R_4 = 500 \Omega$. Calculate the
- (i) Inductance
- (ii) Resistance of the measured inductor
- (iii) θ factor 4
6. (a) Derive the relation for frequency in a Wien Bridge where arm AB consists of resistance R_1 and a series capacitor C_1 , arm BC consists of resistance R_2 , arm CD consists of resistance R_4 , and arm DA consists of parallel combination of resistance R_3 and capacitor C_3 . 5

(b) Draw a neat diagram of vibration galvanometer and explain its working.

5

(c) Derive the expression for Q of coil for series RL, series RC, parallel RL and parallel RC combination.

10

7. (a) Write short notes on : **(any two)**

$7 \times 2 = 14$

(i) Megger

(ii) Kelvin Double Bridge

(iii) A.C. Potentiometer.

(b) Describe a method for the measurement of insulation resistance.

6

