

2013

(May)

ELECTRONIC INSTRUMENTATION

Paper : IE 504

Full Marks : 100

Pass Marks : 30

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. (a) What is the need of electronic instrumentation in advances of technology ? 4
- (b) State the components of a oscilloscope subsystem. Discuss in detail *any two* of them. 10
- (c) What are the ideal characteristics of an OP-AMP ? How we can get unity gain using IC 741 ? Define CMRR in case of OP-AMP. 6

Contd.

2. (a) Discuss the operation of a Colpitt's oscillator. 8
- (b) Discuss IEEE 488 Bus structure. 7
- (c) A moving coil instrument has a resistance of 10Ω and gives full scale deflection, when carrying a current of $50mA$.
Show how it can be adopted to measure
- (i) Currents upto $100A$
- (ii) Voltage upto $750V$ 5
3. (a) What is PLL? How PLL is used as a frequency synthesizer? 10
- (b) How operating ranges of DC ammeter and voltmeter can be increased? 4
- (c) Convert a basic D'Arsonval movement with an — internal resistance of 50Ω and a full scale deflection current of $2mA$ into a multirange d.c. voltmeter with voltage ranges of, $(0-10V)$, $(0-50V)$, $(0-100V)$. 6
4. (a) Discuss the construction and application of electro-dynamometer movement based instrument. Derive the expression for deflection and deflecting torque in case of this type of instruments. 8

- (b) Discuss the principle of working, construction, and related torque equation for PMMC meters. 8
- (c) Explain power measurement in 3- ϕ load. 4
5. (a) Define ground loop. How ground loop interference occurs and how it is reduced? 8
- (b) Explain how audio frequency can be generated? 8
- (c) Describe the operation of magnetic tape recorder. 4
6. (a) What is Q -meter? State the principle of working of a Q -meter based upon $R-L-C$ circuit. 8
- (b) Sketch a practical circuit diagram of a Q -meter. How we can measure inductance and effective resistance using Q -meter circuit? 7

- (c) A circuit consisting of a coil, a resistance and a variable capacitor connected in series is to be tuned to resonance using a Q meter. If the frequency is 500KHz , the resistance 0.5Ω and the variable capacitor set to 350pF calculate the effective inductance and resistance of the coil, if Q meter indicates 90.

5

7. Write short notes on *any two* of the following :
 $10 \times 2 = 20$

- (i) True RMS Responding voltmeter
- (ii) Function Generator
- (iii) Potentiometric Strip Chart Recorder
- (iv) Input guarding to reduce ground loop interference.
- (v) Hartley Oscillator.