

Total number of printed pages—4

53 (IE 504) ELIN

2014

ELECTRONIC INSTRUMENTATION

Paper : IE 504

Full Marks : 100

Pass Marks : 30

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. (a) Explain the principle of working of a Q meter.
Derive the relationship between input and output voltage in a RLC circuit in terms of Q factor. 3+5=8
- (b) A coil of 10Ω resistor is connected in a Q meter circuit. Resonance occurs at a frequency of 1MHz with a tuning capacitor set at 65pF . Calculate the percentage error introduced in the calculated value of Q if resistor 0.2Ω is used across the oscillator circuit. 5

Contd.

(c) Describe the working of PMMC type meter.

7

2. (a) Explain the working of a parallelly connected crystal oscillator.

6

(b) Determine the frequency of oscillation and the minimum value of R_f to sustain oscillation in a Hartley oscillator Fig. 1 (a)

6

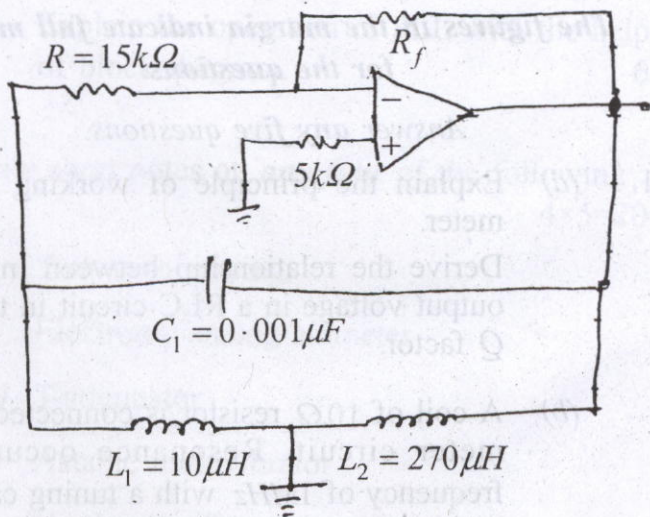


Fig. 1 (a)

(c) What is 'resonant frequency'? Draw and explain the circuit of Colpitt's oscillator.

1+7=8

3. (a) What do you mean by inverting and non-inverting OPAMP? 2

(b) Determine the CMRR in dB of an OPAMP having difference gain of 200 and common mode gain is 15. 3

(c) With the help of block diagram, explain the working of sweep frequency generator. 10

(d) Draw and explain the circuit to generate square wave using OPAMP. 5

4. (a) What is attenuator? Explain the operation of a basic attenuator circuit. 1+5=6

(b) Design a 20dB, 50Ω T attenuator. 6

(c) Describe the electronic analog DC voltmeter with necessary block diagram. 8

5. (a) Explain how analog ohmmeter works? 6

(b) What do you mean by common mode interface? What are the causes of current flow in ground loops? 2+2=4

(c) With the help of circuit diagram, describe how audio frequency can be generated. 8

(d) What is the function of IEEE 486 bus? 2

6. (a) Describe how a digital voltmeter works? 5

(b) How much of voltage is required at the CRT to deflect the deflection plate?
Discuss in details about the horizontal deflection sub system. 1+8=9

(c) Explain the operation of PLL with the help of block diagram. 6

7. Write short notes on **any four** of the following :
4×5=20

(i) Two wire sensing

(ii) Electronic analog ammeter

(iii) T-attenuator

(iv) Astable multivibrator

(v) Hartley oscillator.