

Total number of printed pages-4

53 (IE 602) PWEL

2021

POWER ELECTRONICS

Paper : IE 602

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

1. (a) What are the different types of power diodes ? How is the reverse recovery time significant in classification of power diodes ? 2+3=5
- (b) Draw the forward-biased safe operating area and reverse-biased safe operating area of a power BJT. 4

Contd.

- (c) Give a comparison of power MOSFET and power BJT. 5
- (d) Explain the working of an IGBT. 6
2. (a) Draw the I-V characteristics of an SCR and define the terms—holding current, latching current and forward breakover voltage. 5
- (b) Using two-transistor analogy, explain the Turn Off process of a GTO. 10
- (c) What is MCT ? How can an MCT be Turned On and Off ? 5
3. (a) What is a phase controlled rectifier ? Explain the working of a single-phase half-wave controlled rectifier with RL-load. 10
- (b) A single-phase 230V, 1kW heater is connected across 1-phase, 230V, 50Hz power supply through an SCR. For firing angle delays of 45° and 90° , calculate the power absorbed in the heater element. 4



- (c) A dc battery is charged through a resistor R as shown in *fig. 1*. Derive an expression for the average value of charging current in terms of V_m , E , R etc. on the assumption that the SCR is fired continuously. For an ac source voltage of $230V$, $50Hz$ find the value of average charging current for $R = 8\Omega$ and $E = 150V$, $V_s = V_m \sin \omega t$. 4+2=6


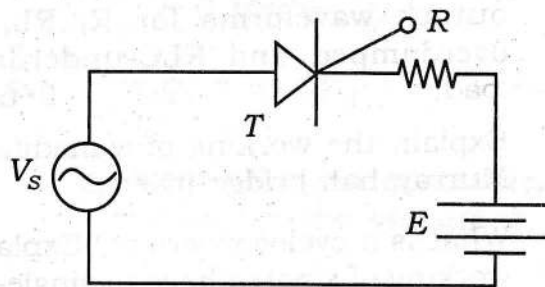


Fig.1

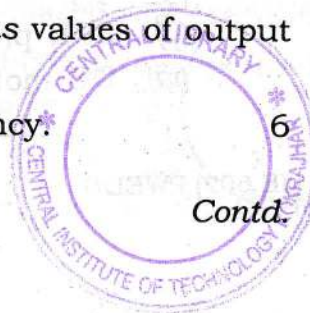4. (a) What is a chopper ? Explain the control strategies of a chopper. 8
- (b) For a type A chopper dc source voltage is $230V$, load resistance is 10Ω . Voltage drop across the chopper is $2V$ when it is ON. For a duty cycle of 0.4 , calculate –
- average and *rms* values of output voltage
 - chopper efficiency. 6



- (c) A step-up choper has input voltage of 220V and output voltage of 660V. If the non-conducting time of thyristor-chopper is $100 \mu\text{s}$, compute the pulse width of the output voltage. In case pulse width is halved for constant frequency operation, find the new output voltage. 6
5. (a) What is an inverter ? Give the steady-state analysis of a voltage source single-phase bridge inverter and draw its output waveforms for R, RL, RLC-overdamped and RLC-underdamped load. 2+6+4=12
- (b) Explain the working of a modified MC Murray half-bridge inverter. 8
6. (a) What is a cycloconverter ? Explain the working of single-phase to single-phase step up cycloconverter. 10
- (b) What is SMPS ? Explain *any one* configuration of SMPS. 10
7. (a) What is UPS ? Explain various types of UPS. 10
- (b) Write short notes on : **(any two)** 5×2=10

- (i) SIT
(ii) SCR protection circuits
(iii) DC motor control.

