

B.Tech 6th Semester examination (compartmental), 2022

Course Title – Power Electronics

Course Code – IE602

Full marks -100

Pass Marks -30

Time- 3 hours

1. (a) What are the different types of power diodes? How the reverse recovery time is significant in classification of power diodes? 2+3=5
- (b) Draw the forward biased safe operating area and reverse biased safe operating area of a power BJT. 4
- (c) Give a comparison of power BJT and power MOSFET. 5
- (d) Explain the working of an IGBT. 6
2. (a) Draw the I-V characteristics of an SCR and define the terms- holding current, latching current and forward break over voltage. 5
- (b) Using two transistor analogy explain the turn off process of a GTO. 10
- (c) What is MCT? How an MCT can be turned on and off? 5
- 3 (a) What is a phase controlled rectifier? Explain the working of a half wave phase controlled rectifier with RL-load. 10
- (b) A single phase 230V, 1KW heater is connected across 1-phase, 230V, 50Hz power supply through an SCR. For firing angle delays of 45° and 90°, calculate the power absorbed in the heating element. 4
- (c) A dc battery is charged through a resistor R as shown in fig.1. Derive an expression for the average value of charging current in terms of V_m , E, R etc. on the assumption that the SCR is fired continuously. For an AC source voltage of 230V, 50Hz find the value of average charging current for $R=8\Omega$ and $E=150V$. 2+4=6

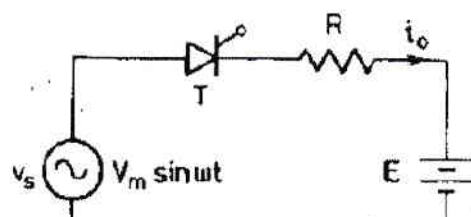


Fig. 1

4. (a) What is a chopper? Explain the control strategies of a chopper. 8
- (b) For a type A chopper dc source voltage is 230V, load resistance is 10Ω . Voltage drop across the chopper is 2V when it is on. For a duty cycle of 0.4 calculate -
- (i) average and rms values of output voltage
 - (ii) chopper efficiency 6
- (c) A step up chopper has input voltage of 220V and output voltage of 660V. If the non-conducting time of thyristor chopper is $100\mu\text{s}$, compute the pulse width of the output voltage. In case pulse width is halved for constant frequency operation, find the new output voltage. 6
5. (a) What is an inverter? Give the steady state analysis of a voltage source single phase bridge inverter and draw its output waveforms for R, RL, RLC – over damped and RLC- Under damped load. 2+6+4=12
- (b) Explain the working of a modified McMurray half bridge inverter. 8
6. (a) What is a cycloconverter? Explain the working of single phase to single phase step up cycloconverter. 10
- (b) What is SMPS? Explain any one configuration of SMPS. 10
7. (a) What is UPS? Explain various types of UPS. 10
- (b) Write short notes on (any two) - 5x2=10
- (i) SIT
 - (ii) SCR protection circuits
 - (iii) DC motor control

