

Total number of printed pages-10

53 (IE 602) PWEL

2014

## POWER ELECTRONICS

Paper : IE 602

Full Marks : 100

Time : Three hours

*The figures in the margin indicate full marks for the questions.*

*Answer any 5 (Five) questions.*

1. (a) Derive an expression for the anode current in the two-transistor model of a thyristor. Discuss the turn-on mechanism of the thyristor with the application of gate signal. 7
  
- (b) A thyristor, having maximum *rms* on-state current of 45A, is used in a resistive circuit. Compute its average on-state current rating for half-sine wave for conduction angle of  $\pi/3$ . 4

Contd.

(c) Draw a firing circuit for thyristor and mention the equation for gate voltage. 3


(d) A relaxation oscillator using an UJT as shown in figure below, is to be designed for triggering an SCR. The UJT has the following data :

$$\eta = 0.72, I_P = 0.6 \text{ mA}, V_P = 18.0 \text{ V},$$

$$V_v = 1.0 \text{ V}, I_v = 2.5 \text{ mA}, R_{BB} = 5 \text{ k}\Omega,$$

Normal leakage current with emitter open =  $4.2 \text{ mA}$ . 4

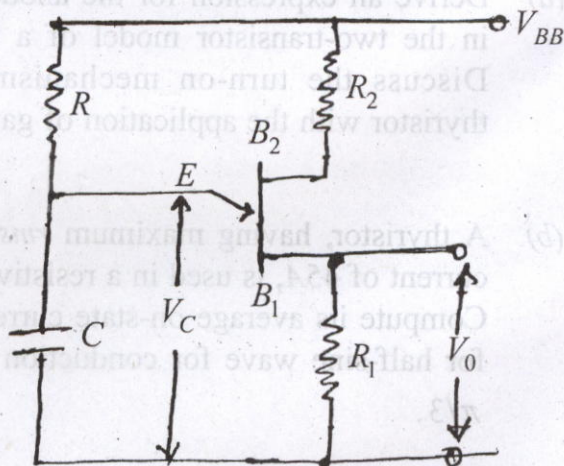The firing frequency is  $2 \text{ KHz}$ . For  $C = 0.04 \mu\text{F}$ , compute the values of  $R$ ,  $R_1$  and  $R_2$




(e) What do you mean by latching current and holding current in a thyristor? 2

2. (a) What do you mean by Snubber Circuits? Why they are used?

In the following figure, a thyristor is used to control power in a load resistance  $R_L$ . The supply voltage is  $220V\ dc$  and the specified limits for  $di/dt$  and  $dv/dt$  for the SCR are  $40A/\mu sec$  and  $300V/\mu sec$  respectively.

Determine the values of  $L$ ,  $R_S$  and  $C_S$ .

7

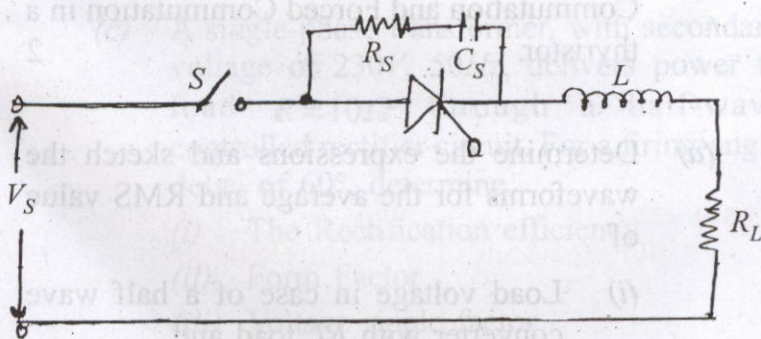




- (b) A thyristor string is made up of a number of SCRs connected in series and parallel. The string has voltage and current ratings of  $11kV$  and  $4kA$  respectively. The voltage and current ratings of available SCRs are  $1800V$  and  $1000A$  respectively. For a string efficiency of  $90\%$ , calculate the number of series and parallel connected SCRs.  
For these SCRs, maximum off-state blocking current is  $12mA$ . Determine the value of static equalizing resistance for the string. 5
- (c) Explain the different modes of operation of a Triac. 6
- (d) Draw the circuit diagram for Load Commutation and Forced Commutation in a thyristor. 2
3. (a) Determine the expressions and sketch the waveforms for the average and RMS value of
- (i) Load voltage in case of a half wave converter with  $RL$  load and
- (ii) Load voltage in case of a full wave converter with  $R$  load. 8

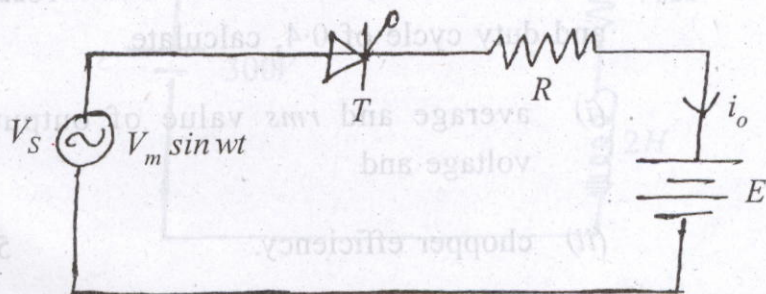(b) A d.c. battery is charged through a resistor  $R$  as shown in the figure below. Derive an expression for the average value of charging current in terms of  $V_m$ ,  $E$ ,  $R$ , firing angle delay  $\alpha$  etc.

For an ac source voltage of  $230V$ ,  $50Hz$ , find the value of average charging current for  $R=10\Omega$ ,  $E=110V$  and for firing angle delay  $\alpha=30^\circ$ .



(c) A single-phase transformer, with secondary voltage of  $230V$ ,  $50Hz$ , delivers power to load  $R=10\Omega$  through a half-wave controlled rectifier circuit. For a firing-angle delay of  $60^\circ$ , determine

- (i) The Rectification efficiency
- (ii) Form Factor
- (iii) Voltage ripple factor
- (iv) Transformer utilization factor and
- (v) P/V of thyristor.



4. (a) For a three phase half-wave converter, derive an expression for the average value of output voltage for firing angle  $\alpha$  when

(i)  $\alpha$  is less than  $30^\circ$  and

(ii)  $\alpha$  is greater than  $30^\circ$ . 6


(b) For a type-A chopper with  $dc$  source voltage =  $230V$ , load resistance =  $10\Omega$  and duty cycle of  $0.4$ , calculate

(i) average and  $rms$  value of output voltage and

(ii) chopper efficiency. 5

(c) Explain the operation of type D chopper with relevant waveforms. 5

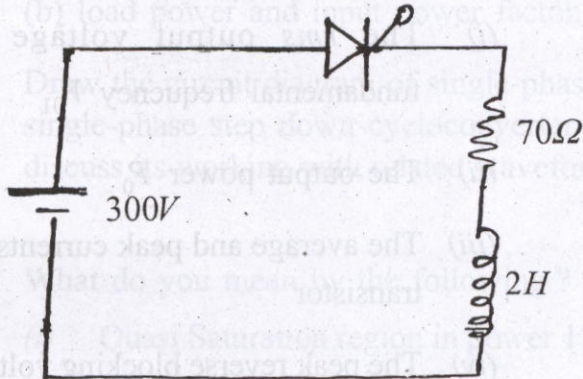- (d) In the circuit below, the thyristor is gated with a pulse width of 40 *microsec*. The latching current of thyristor is 36mA. For a load of  $70\Omega$  and  $2H$ , will the thyristor get turned on? 2



- (e) For a thyristor, maximum junction temperature is  $125^{\circ}\text{C}$ . The thermal resistances for the thyristor-sink combination are  $\theta_{jc} = 0.16$  and  $\theta_{cs} = 0.08^{\circ}\text{C}/\text{W}$ . For a heat-sink temperature of  $70^{\circ}\text{C}$ , compute the total average power loss in the thyristor-sink combination. 2

5. (a) Draw the circuit diagram of single phase inverter and explain its operation. 4
- (b) The single-phase full-bridge inverter has a resistive load of  $R = 2.4\Omega$  and the  $dc$  input voltage is  $V_S = 48V$ . Determine
- (i) The *rms* output voltage at the fundamental frequency  $V_{01}$
  - (ii) The output power  $P_0$
  - (iii) The average and peak currents of each transistor
  - (iv) The peak reverse blocking voltage  $V_{BR}$  of each transistor
  - (v) The THD. 6
- (c) Discuss the principle of working of a three-phase bridge inverter with an appropriate circuit diagram. Draw phase and line voltage waveforms on the assumption that each thyristor conducts for  $180^\circ$  and the resistive load is star-connected. 10



6. (a) A single phase full wave *ac* voltage controller feeds a load of  $R = 20\Omega$  with an input voltage of  $230V, 50Hz$ .

Firing angle for both the thyristors is  $45^\circ$ . Calculate (a) *rms* value of output voltage  
(b) load power and input power factor. 5

(b) Draw the circuit diagram of single-phase to single-phase step down cycloconverter and discuss its working with related waveforms. 6

(c) What do you mean by the following? 3

(i) Quasi Saturation region in power IGBT.

(ii) Inversion Layer in Power MOSFET.

(iii) Drift region in power devices.

(d) Draw the gate drive circuit for Power BJT and Power MOSFET. Discuss how these circuits work. 6

7. (a) Write short notes on *any two* :  $5 \times 2 = 10$

(i) Current Inverter

(ii) UPS

(iii) Microprocessor/Microcontroller control of power devices.

(b) Draw the block diagram of buck converter.

Deduce the relations for  $\Delta I$  and  $\Delta V$  in a buck converter. 6

(c) Draw the circuit diagram for bidirectional and resonant power supplies. 4