

Total number of printed pages-5

53 (IT 303) DGEL

2014

DIGITAL ELECTRONICS

Paper : IT 303

Full Marks : 100

Pass Marks : 30

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. (a) Convert the following : 1×5=5

(i) $(1F2A)_{16} = (\text{---})_2$

(ii) $(11001)_2 = (\text{---})_{16}$

(iii) $(155)_{10} = (\text{---})_8$

(iv) $(0.32)_{10} = (\text{---})_2$

(v) $(11000101)_2 = (\text{---})_8$

Contd.

(b) Perform binary arithmetic operation on the following : $2 \times 4 = 8$

(i) 110×111

(ii) $1100 \div 10$

(iii) $10110 - 101$

(iv) $11110 + 10111$

(c) Subtract $11011 - 01110$ using 2's complement method. 3

(d) Draw the logic diagram of $y = a'b + b'cd + ef$ using basic gates only. 4

2. (a) Simplify the following using boolean algebra. $2 + 3 + 3 = 8$

(i) $xyz + x'y + xyz'$

(ii) $A'C' + ABC + AC' + AB'$

(iii) $ABCD + A'BD + ABC'D + A'D$

(b) Using k -map simplify the below functions. 6×2=12

(i) $F = \sum m(0,1,2,4,5,9,10,11,13)$

(ii) $F = \sum m(2,3,4,9,10,14)$ with don't care conditions $d(1,11,15)$

3. (a) Use only NAND Gate to implement the below boolean function 5

$$F = ab' + ac + bd'$$

(b) Design a 4 : 1 multiplexer. 7

(c) Write down the truth table of a seven segment decoder. 5

(d) Draw the block diagram of a 4 bit ripple carry adder. 3

4. (a) Explain the operation of a basic S-R latch. 5

(b) Discuss the difference between a positive and a negative edge-triggered flip flop. 4

(c) Design a Full Subtractor. 7

- (d) (i) An asynchronous counters are known as _____.
- (ii) A circuit with many inputs but only one output is named as _____.
- (iii) A 4 bit binary counter has a maximum modules of _____.
- (iv) $A + A'B =$ _____. $1 \times 4 = 4$
5. (a) Explain the truth table of a J-K flipflop. 5
- (b) Describe the operation of Master-slave D-flipflop. 5
- (c) Describe the operation of a 2 bit asynchronous binary counter and develop counter timing diagram. 10
6. (a) Develop and analyze timing diagram for serial in serial out shift registers. 10
- (b) Describe a PLA and compare with PAL. $6 + 4 = 10$

7. (a) Describe a 2 bit magnitude comparator. 5
- (b) Differentiate between multiplexer & Demultiplexer. 3
- (c) What are the main differences between synchronous and asynchronous logic ? 3
- (d) What is excitation table ? 2
- (e) Write down the state synthesis table for SR to JK flip flop conversion. 5
- (f) Write down how excitation table is different from truth table. 2