

Total number of printed pages-5

53 (IT 303) DGEL

2017

**DIGITAL ELECTRONICS**

Paper : IT 303 (Back)

Full Marks : 100

Time : Three hours

**The figures in the margin indicate full marks for the questions.**

Answer **any five** questions.

1. (a) Convert the following into binary : 3

(i)  $(10F)_{16}$

(ii)  $(24)_{10}$

(iii)  $(321)_8$

(b) Convert the following into decimal : 3

(i)  $(10111)_2$

Contd.

(ii)  $(F1)_{16}$

(iii)  $(21)_8$

(c) Find out the Ex-3 code and BCD code of 23. 2

(d) Draw the logic circuit represented by each expression :  $3+3=6$

(i)  $AB + \bar{A}\bar{B} + \bar{A}BC$

(ii)  $A + B [C + D (B + \bar{C})]$

(e) Construct a truth table for each of the following Boolean expressions :  $2+3=5$

(i)  $(A + B)C$

(ii)  $(AB + C)\bar{B}$

(f) What is Gray Code ? 1

2. (a) Using Boolean algebra, simplify each expression :  $3+1+1+1+2+1=9$

(i)  $AB + (\bar{A} + \bar{B})C + AB$

(ii)  $BC + \bar{B}C$

(iii)  $A(A+B)$

(iv)  $A(\bar{A}+AB)$

(v)  $(B+BC)(B+\bar{B}C)(B+D)$



(vi)  $A(A+\bar{A}B)$

(b) Convert the following expressions to sum of product (SOP) forms :  $1+2=3$

(i)  $(A+\bar{B}C)C$

(ii)  $(A+C)(AB+AC)$

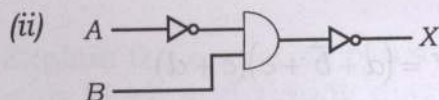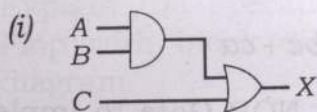(c) Write the Boolean expression for each of the logic circuits  $1+1=2$



(d) Convert into canonical SOP form :  $3+3=6$

(i)  $a' + bc$

(ii)  $xy + x'z$

3. (a) Use Karnaugh map to simplify each expression to a minimum SOP form :  
4+5+6=15

(i)  $\bar{A}\bar{B}\bar{C} + \bar{A}BC + \bar{A}BC + ABC\bar{C}$

(ii)  $\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + ABCD + ABC\bar{D}$

(iii)  $f(w, x, y, z) = \sum m(0, 1, 2, 3, 4, 11, 13, 14) + d(5, 6)$

(b) Draw a 4-variable Karnaugh map and label each cell according to its binary value. 5

4. (a) Use only NAND Gate to implement : 3

$$Y = ab + bc + ca$$

(b) Use only NOR Gate to implement : 3

$$Y = (a + \bar{b} + c)(c + d)$$

(c) State and prove De-Morgan's theorem. 2+5=7

(d) Design a 2 to 4 Decoder. 5

(e) Write down the truth table of a X-NOR Gate. 2

5. (a) Design a 8:1 Multiplexer. 5
- (b) Describe the operation of a S-R latch with circuit diagram and Function table. 6
- (c) Write down the truth table of a J-K latch. 3
- (d) Draw the Block diagram of a 3 bit ripple carry adder. 3
- (e) Write down the truth table of a 4 to 2 encoder. 2
- (f) Define Logic Gate. 1
6. (a) Design a Mod-7 Counter. 13
- (b) Explain the operation of a M-S Flip Flop with block diagram and timing diagram. 7
7. (a) Explain the operation of a 4 bit register with block and timing diagram. 10
- (b) Draw the block diagram of a 2 bit asynchronous counter and explain its counting operation with timing diagram. 10