

Total number of printed pages-4

53 (IT 303) DGLD

2016

DIGITAL LOGIC DESIGN

Paper : IE 303

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

1. (a) Write down BCD & Ex-3 code of 562. 2
- (b) Convert $(1011\cdot01)_2$ to Decimal. 1
- (c) State De-Morgan's Law. 2
- (d) Define Minterm. 2
- (e) Why NAND, NOR Gates are called universal gate ? 2
- (f) Use only NOR Gate to realize AND function. 2
- (g) Use K-map method to simplify
 $f(w,x,y,z) = \sum m(0,1,3,5,9,10,11,12,13)$ 5

Contd.

(h) Prove that $a + bc = (a + b)(a + c)$ 4

2. (a) Simplify using Boolean algebra

$$Y = f(x, y, z) = x'yz + xy'z' + x'y'z + xyz + x'y'z'$$

3

(b) Use basic gates to realize
 $Y = (a + b')cd + a'bc'$ 2

(c) Design a Full Subtractor. 5

(d) Convert $(F23E \cdot E1)_{16}$ to Binary. 1

(e) Draw block diagram of a 2 bit ripple carry adder and explain its addition operation. $2+3=5$

(f) Use NAND Gate only to implement
 $Y = a' + b'c$ 3

(g) Convert $(F20 \cdot I)_{16}$ to Decimal. 1

3. (a) Design a 8:1 Multiplexer. 5

(b) Distinguish between Decoder and Encoder. 2

(c) How many control lines are needed to design a 16:1 Multiplexer ? 1

- (d) Convert $(71)_8$ to decimal. 1
- (e) Use K-map method to simplify into product of sum form
 $f(w, x, y, z) = \pi M(0, 2, 3, 4, 9, 10)$ 5
- (f) Draw the circuit diagram of a S-R latch and explain its truth table. 4
- (g) Draw the block diagram of 2 bit counter. 2

4. (a) Simplify using Boolean algebra
 $Y = (a + b + c') (a + b + c) \overline{(a + b)}$ 3
- (b) What do you mean by don't care conditions and how don't care conditions help to simplify Boolean function using K-map method ? 1+2=3
- (c) Explain the truth table of J-K latch. 4
- (d) What are the main differences between sequential and combinational logic ? 3
- (e) Perform subtraction using 2's complement method $1011 - 1100$. 2
- (f) What is race around condition ? 2
- (g) Perform addition and division 1.5×2=3
- (i) $1111 + 1111$
- (ii) $101010 \div 10$

5. (a) Design a Mod-5 Counter. 10
- (b) Explain the operation of a 3 bit register with its block diagram. 6
- (c) Define Quad and Octet. 2
- (d) State commutative law of Boolean algebra. 2
6. (a) Design a 4 bit Binary to Gray converter. 5
- (b) Describe the operation of a 2 bit synchronous counter with timing diagram. 8
- (c) Simplify using Boolean algebra.

$$Y = xy + \overline{xyz} + \overline{xy}$$
 2
- (d) Explain the operation of M-S D-Flip Flop. 5
7. (a) Design a BCD adder. 12
- (b) Write down the Excitation tables for J-K Flip Flop, D Flip Flop, S-R Flip Flop. 6
- (c) Draw the circuit diagram of D-latch. 2