

Total number of printed pages-3

53 (IT 303) DGLG

2021

**DIGITAL LOGIC DESIGN**

Paper : IT 303

Full Marks : 100

Time : Three hours

**The figures in the margin indicate full marks for the questions.**

Answer **any five** questions.

1. (a) Convert the following:  $2 \times 5 = 10$

(i)  $(186)_{10} = (?)_8$

(ii)  $(1111.01)_2 = (?)_{10}$

(iii)  $(12FBA)_{16} = (?)_2$

(iv)  $(21.8)_8 = (?)_{10}$

(v)  $(01111011011010)_2 = (?)_{16}$

Contd.

(b) Verify the following using truth table method: 10

(i)  $\overline{(AB + \bar{B} + A\bar{B})} = 0$

(ii)  $(\bar{A} + B)(A + \bar{B}) = AB + \bar{A}\bar{B}$

2. (a) Expand  $(\bar{A} + \bar{B})$  to Minterm and Maxterms. 10

(b) State and prove both the laws of De Morgan's theorem. 10

3. Using K-map, simplify the following functions: 5×4=20

(i)  $F(A, B, C) = \sum m(5, 7, 2, 3)$

(ii)  $F(A, B, C, D) = \sum m(0, 2, 5, 9, 15) + d(6, 3, 10, 13)$

(iii)  $F(A, B, C, D) = \Pi M(2, 3, 9, 10, 11)$

(iv)  $F(A, B, C, D) = \sum m(4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15)$

4. (a) Draw the logic circuit of the Boolean functions given below using basic gates: 5+5=10

(i)  $Y = \bar{a}b\bar{c} + c\bar{d}$

(ii)  $Y = a + \bar{a}\bar{b} + (a + \bar{b})cd$



- 
- (b) Explain the full-adder circuit with the help of function table. 10
5. Explain various types of flip-flop in details with the help of diagrams. 20
6. (a) Explain 4 : 1 multiplexer and 1 : 4 Demultiplexer in details. 10  
(b) Explain 8×3 Encoder and 3×8 Decoder in details. 10
7. Write short notes on: **(any four)** 5×4=20
- (a) Universal Gates
- (b) Minterm and Maxterm
- (c) SOP and POS form
- (d) Sequential and Combinational circuit
- (e) RAM and ROM
- (f) Primary and Secondary memory.

