

Total number of printed pages-5

53 (IT 303) DLDG

2017

DIGITAL LOGIC DESIGN

Paper : IT 303

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

1. (a) Convert the following : 6

(i) $(110.1)_2 = (?)_{10}$

(ii) $(FOF)_{16} = (?)_2$

(iii) $(1F.1)_{16} = (?)_{10}$

(iv) $(49.125)_{10} = (?)_2$

(v) $(21.7)_8 = (?)_2$

(vi) $(10000.0010)_2 = (?)_8$

Contd.

(b) Use Boolean algebra to simplify the following Boolean equation.

(i) $f(x, y, z) = (x + \bar{x}y) \bar{x} + \overline{xyz}$ 2

(ii) $f(A, B, C) = (A + AB) A + A + A'BC$ 2

(iii) $f(a, b, c) = \overline{(a + bc)(a + bc')} \{ (a'b'c')' + a' \}$ 2

(iv) $f(x, y, z) = xyz + x'y'z + xy'z' + x'y'z' + x'yz$ 3

(c) Prove that : 5

(i) $\overline{a + b + c} = \bar{a} \bar{b} \bar{c}$

(ii) $\overline{ab} = \bar{a} + \bar{b}$

2. (a) 1×5=5

(i) 2's complement of 101110 is _____.

(ii) $1 \oplus 1 \oplus 0 \oplus 1 =$ _____.

(iii) Excess-3 code of 121 is _____.

(iv) BCD code of 149 is _____.

(v) $0 + 1 + 1 + 1 =$ _____.

(b) Find out the logic circuit using basic gates.

$$Y = f(x, y, z) = \bar{x}(\bar{x} + \bar{y})\overline{xy} + \overline{xyz}$$

without simplifying the Boolean function above. 3

(c) Use NOR gate only to implement

$$Y = x + y + z \quad 2$$

(d) Subtract $10111 - 10000$ using 2's complement method. 2

(e) Design a Full subtractor. 8

3. (a) Define with example : $2+2=4$

(i) Minterm

(ii) Maxterm.

(b) Simplify using k -map method.

$$4 \times 2 = 8$$

(i) $\sum m(0, 1, 2, 4, 9, 11, 13, 14, 15)$

(ii) $f(A, B, C, D) = \sum m(1, 2, 9, 14) + d(0, 3, 11, 12)$

(c) Design a 8 : 1 Multiplexer. 8

4. (a) Explain the operation of a J-K latch with truth table and circuit diagram. 5
- (b) Draw the circuit diagram of a 2 bit ripple carry adder. 2
- (c) Draw the block diagram of a 3 bit asynchronous counter. 2
- (d) Distinguish between : $2 \times 3 = 6$
- (i) synchronous and asynchronous circuit
 - (ii) combinational and sequential circuit
 - (iii) truth table and state transition table.
- (e) Explain the operation of a Master-Slave D-Flip Flop. 5
5. (a) Design a Mod-5 counter using J-K flip flop. 13
- (b) Explain the 2 bit synchronous counter with timing diagram. 7
6. (a) Design a 2 bit Magnitude comparator. 7

- (b) Write down the truth of a 7 segment decoder. 4
- (c) What is race around condition? 2
- (d) Draw the circuit diagram of a T-latch. 2
- (e) Write down the truth table of a BCD adder. 5
7. (a) Design a Mod-7 synchronous counter using D-Flip Flop. 14
- (b) Design a 1 : 8 De-Multiplexer. 6
-